

SRIPC ECE

**UNIT-I
INTRODUCTION TO VLSI**

**SWATHI E R
LECTURER/ECE**


REVOLUTION THROUGH TECHNOLOGY

764 - SRIPC

Introduction

- Metal Oxide-Semiconductor (MOS) structure is created by superimposing several layers of conducting and insulating materials to form a sandwich-like structure.
- These structures are manufactured using a series of chemical processing steps involving oxidation of the silicon, selective introduction of dopants, and deposition and etching of metal wires and contacts.
- CMOS technology provides two types of transistors: an *n*-type transistor (*n*MOS) and a *p*-type transistor (*p*MOS).
- Transistor operation is controlled by electric fields so the devices are also called Metal Oxide Semiconductor Field Effect Transistors (MOSFETs)

SRIIPC ECE

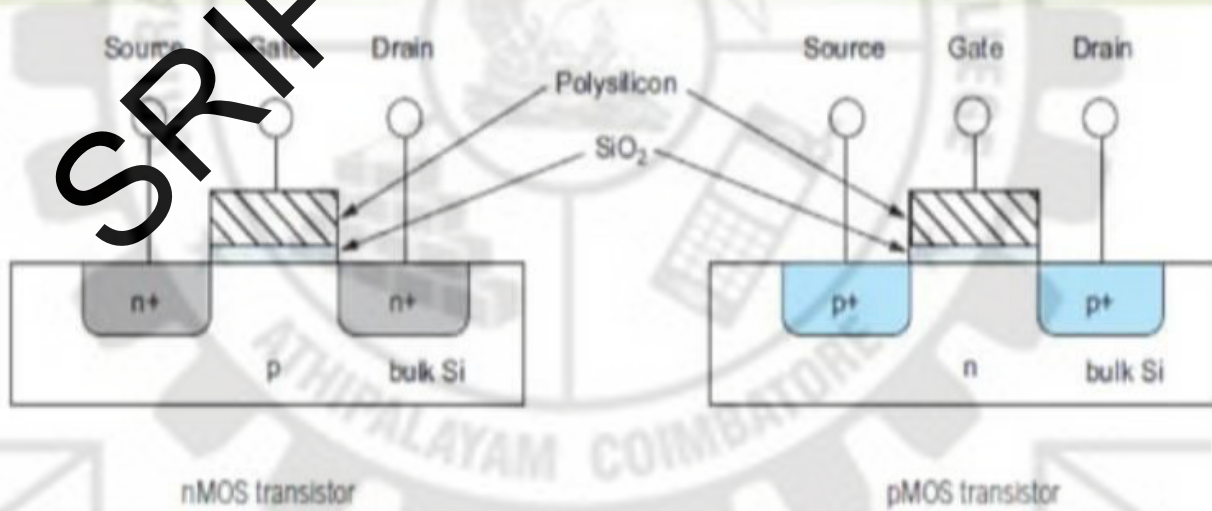

REVOLUTION THROUGH TECHNOLOGY

MOS Principle

- The gate is a control input: It affects the flow of electrical current between the source and drain.

REVOLUTION THROUGH TECHNOLOGY

764 - SRIPC

N-channel MOSFET


- Consider an nMOS transistor.
- The body is generally grounded so the p-n junctions of the source and drain to body are reverse-biased.
- If the gate is also grounded, no current flows through the reverse-biased junctions. Hence, we say the transistor is **OFF**.
- If the gate voltage is raised, it creates an electric field that starts to attract free electrons to the underside of the Si-SiO₂ interface.
- If the voltage is raised enough, the electrons outnumber the holes and a thin region under the gate called the *channel* is *inverted* to act as an n-type semiconductor.
- Hence, a conducting path of electron carriers is formed from source to drain and current can flow. We say the transistor is **ON**.

P-channel MOSFET

- For a pMOS transistor, The body is held at a positive voltage.
- When the gate is also at a positive voltage, the source and drain junctions are reverse-biased and no current flows, so the transistor is OFF.
- When the gate voltage is lowered, positive charges are attracted to the underside of the Si-SiO₂ interface.
- A sufficiently low gate voltage inverts the channel and a conducting path of positive carriers is formed from source to drain, so the transistor is ON.

MOSFET as Switch


- The gate of an MOS transistor controls the flow of current between the source and drain.
- Simplifying this to the extreme allows the MOS transistors to be viewed as simple ON/OFF switches.
- When the gate of an nMOS transistor is 1, the transistor is ON and there is a conducting path from source to drain.
- When the gate is low, the nMOS transistor is OFF and almost zero current flows from source to drain.
- A pMOS transistor is just the opposite, being ON when the gate is low and OFF when the gate is high.

 

764 - SRIPC

CMOS Inverter

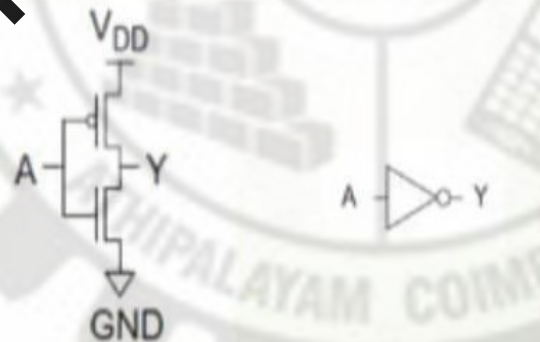- When the input A is 0, the nMOS transistor is OFF and the pMOS transistor is ON. Thus, the output Y is pulled up to 1 because it is connected to
- V_{DD} but not to GND.
- Conversely, when A is 1, the nMOS is ON, the pMOS is OFF, and Y is pulled down to 0.
- Schematic and Symbol for a CMOS inverter



★ Inverter truth table

A	Y
0	1
1	0

- The bar at the top indicates V_{DD} and the triangle at the bottom indicates GND.

CMOS NAND Gate




Gate Schematic

Symbol

764 - SRIPC

CMOS NAND Gate

- It consists of two series nMOS transistors between Y and GND and two parallel pMOS transistors between Y and VDD .
- If either input A or B is 0:
 - At least one of the nMOS transistors will be OFF, breaking the path from Y to GND .
 - But at least one of the pMOS transistors will be ON, creating a path from Y to VDD .
 - Hence, the output Y will be 1.
- If both inputs are 1,
 - both of the nMOS transistors will be ON and
 - both of the pMOS transistors will be OFF.
 - Hence, the output will be 0.

 


CMOS NAND Gate

A	B	Pull-Down Network	Pull-Up Network	Y
0	0	OFF	ON	1
0	1	OFF	ON	1
1	0	OFF	ON	1
1	1	ON	OFF	0

CMOS Logic Structure

SRIPC ECE

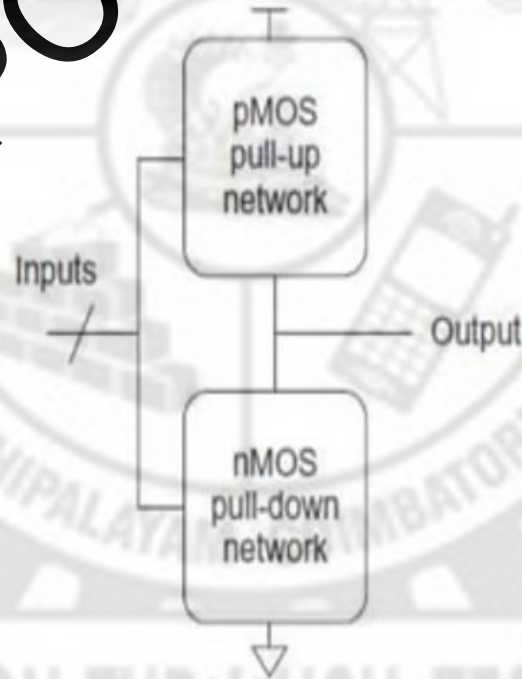


CMOS Logic Structure


- In general, a static CMOS gate has
 - ▶ an nMOS *pull-down network* to connect the output to 0 (GND) and
 - ▶ pMOS *pull-up network* to connect the output to 1 (VDD)
- In general, when we join a pull-up network to a pull-down network to form a logic gate, they both will attempt to exert a logic level at the output.
- *The networks are arranged such that one is ON and the other OFF for any input pattern.*

	pull-up OFF	pull-up ON
pull-down OFF	Z	1
pull-down ON	0	crowbarred (X)

 Connection and behaviour of series and parallel transistors




SRIPC ECE

 

764 - SRIPC

CMOS NOR Gate

 - The nMOS transistors are in parallel to pull the output low when either input is high.
- The pMOS transistors are in series to pull the output high when both inputs are low




NOR gate truth table

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

CMOS NOR Gate

 - The nMOS transistors are in parallel to pull the output low when either input is high.
- The pMOS transistors are in series to pull the output high when both inputs are low



NOR gate truth table

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0




SRIPC ECE

3 input NOR Gate??

764 - SRIPC


SRIPC ECE

 

3 input NOR Gate

764 - SRIPC

SRIPC ECE

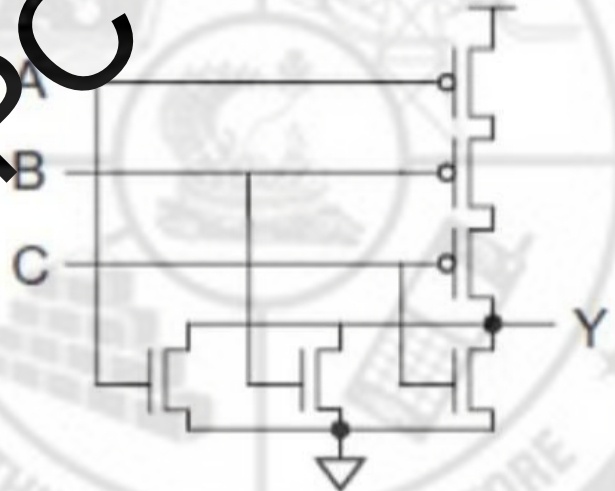

3 input NOR Gate


REVOLUTION THROUGH TECHNOLOGY

764 - SRIPC



REVOLUTION THROUGH TECHNOLOGY

764 - SRIPC

 

3 input NAND Gate

REVOLUTION THROUGH TECHNOLOGY

764 - SRIPC

Compound Gates

$$Y = \overline{(A \cdot B) + (C \cdot D)}$$

AND-OR-INVERT-22 or AOI22

764 - SRIPC

Pull Up Network

A
B

C
D

A
B

C
D

Pull Down Network

A

B

C

D


C

D

A

B

764 - SRIPC

 

REVOLUTION THROUGH TECHNOLOGY

764 - SRIPC

Compound Gates


$$Y = (A + B + C) \cdot D$$

OR-AND-INVERT-3-1 (OAI31) gate.

REVOLUTION THROUGH TECHNOLOGY

764 - SRIPC

SRIPC ECE

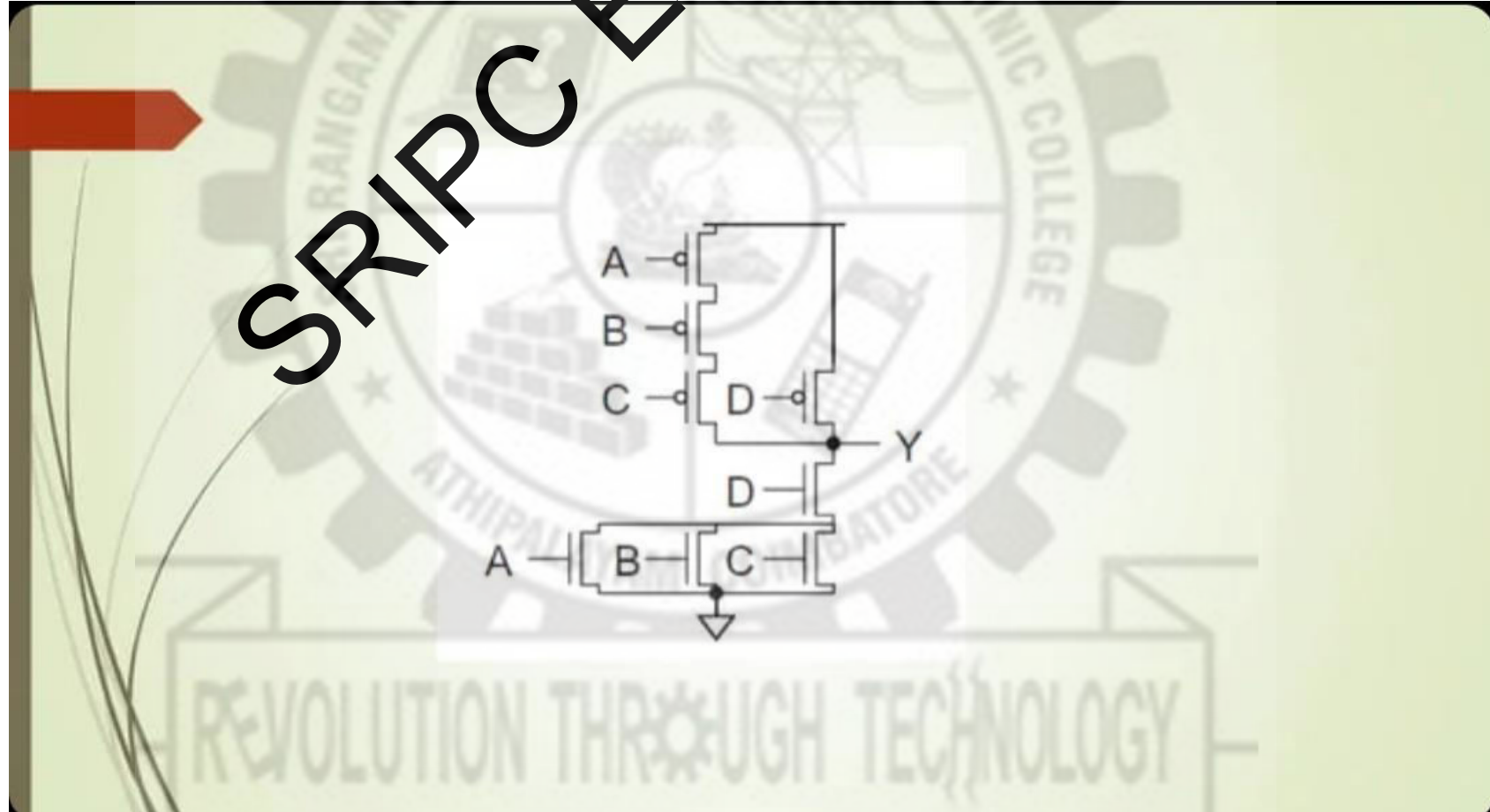

764 - SRIPC

Combinational Circuits

Sketch transistor-level schematics for the following logic functions. You may assume you have both true and complementary versions of the inputs available.

a) A 2:4 decoder defined by

$$Y_0 = \bar{A}_0 \cdot \bar{A}_1$$

$$Y_1 = \bar{A}_0 \cdot A_1$$

$$Y_2 = A_0 \cdot \bar{A}_1$$

$$Y_3 = A_0 \cdot A_1$$


b) A 3:2 priority encoder defined by

$$Y_0 = \bar{A}_0 \cdot (A_1 + \bar{A}_2)$$

$$Y_1 = \bar{A}_0 \cdot \bar{A}_1$$

Pass Transistors and Transmission Gates

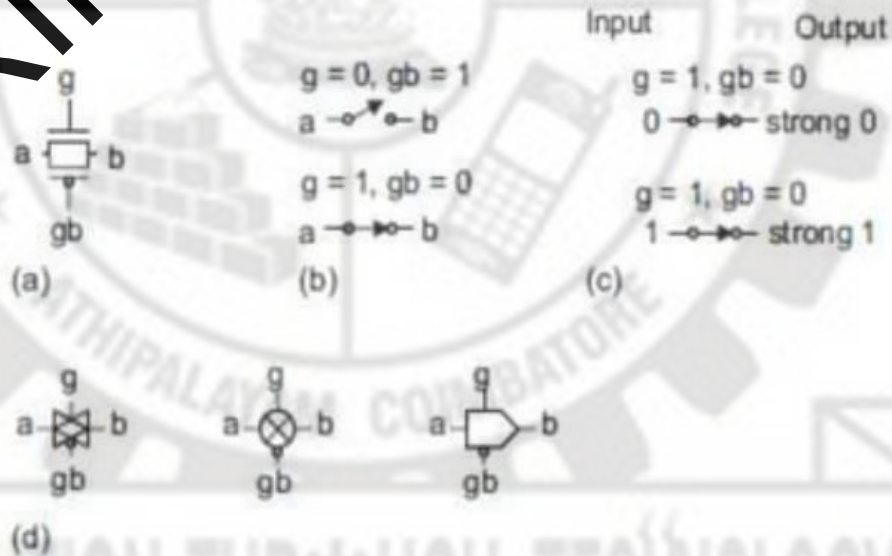- By combining an nMOS and a pMOS transistor in parallel, we obtain a switch, which 0s and 1s are both passed in an acceptable fashion.
- We term this a *transmission gate* or *pass gate*.



Pass Transistors and Transmission Gates


- The strength of a signal is measured by how closely it approximates an ideal voltage source.
- The power supplies, or rails, (VDD and GND) are the source of the strongest 1s and 0s.
- An nMOS transistor is an almost perfect switch when passing a 0 and thus we say it passes a **strong 0**. However, the nMOS transistor is imperfect at passing a 1. We say it passes a degraded or **weak 1**.
- An pMOS transistor is an almost perfect switch when passing a 1 and thus we say it passes a **strong 1**. However, the pMOS transistor is imperfect at passing a 0. We say it passes a degraded or **weak 0**.

Pass Transistors and Transmission Gates

Concept of Weak :

Consider an nMOS transistor with the Gate and Drain tied to V_{DD} .

 Imagine that the source is initially at $V_s = 0$. $V_{gs} > V_{tn}$, so the transistor is ON and current flows.




If the voltage on the source rises to $V_s = V_{DD} - V_{tn}$, V_{gs} falls to V_{tn} and the transistor cuts itself OFF.

Therefore, nMOS transistors attempting to pass a 1 never pull the source above $V_{DD} - V_{tn}$. This loss is called threshold drop.

Pass Transistors and Transmission Gates


Concept of Weak 0:

Similarly, pMOS transistors pass 1s well but 0s poorly. If the pMOS source drops below $|V_{tp}|$, the transistor cuts off.

 


Hence, pMOS transistors only pull down to within a threshold above GND.

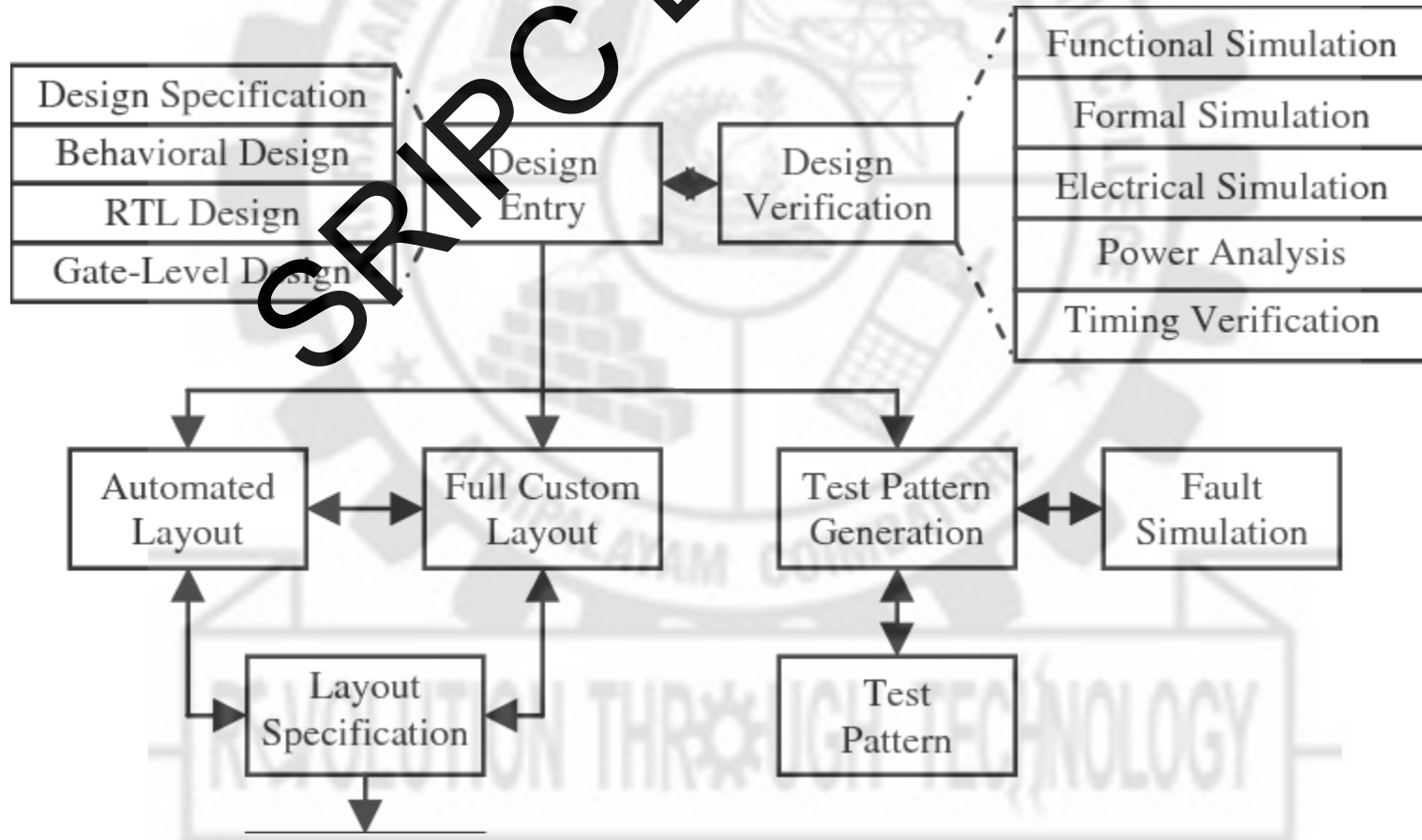DIFFERENT LEVEL OF ABSTRACTIONS IN VLSI DESIGN





STEPS INVOLVED IN VLSI DESIGN PROCESS

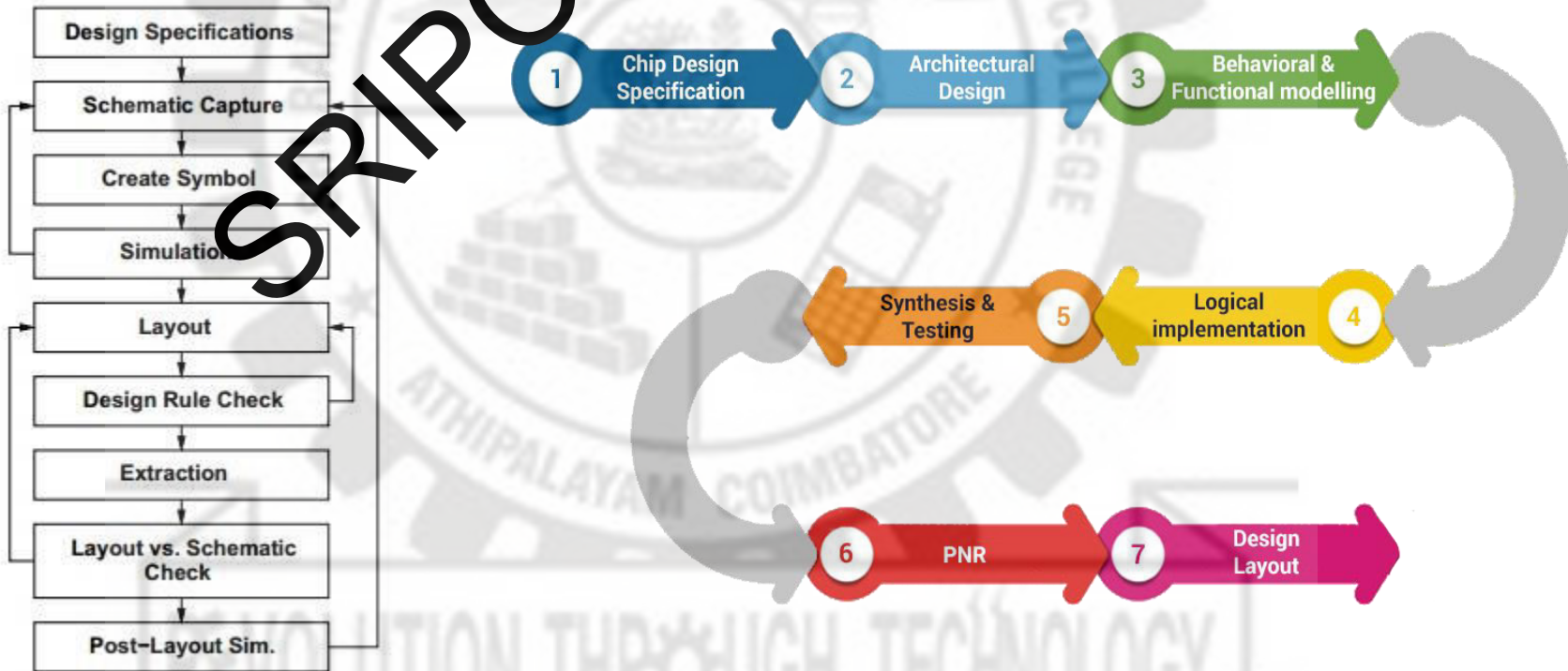



LAYOUT

SRIPC ECE

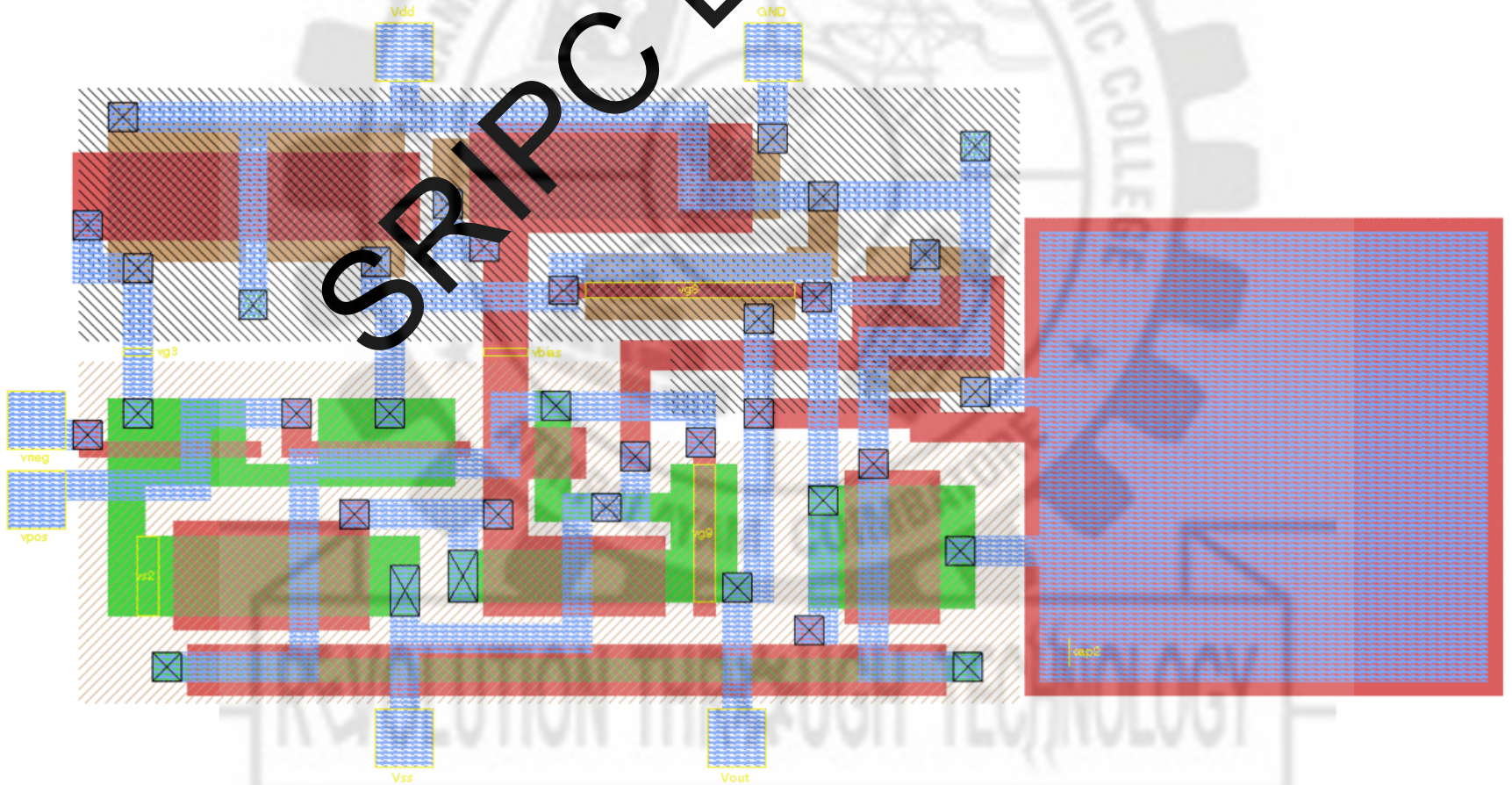

 

STICK DIAGRAM

 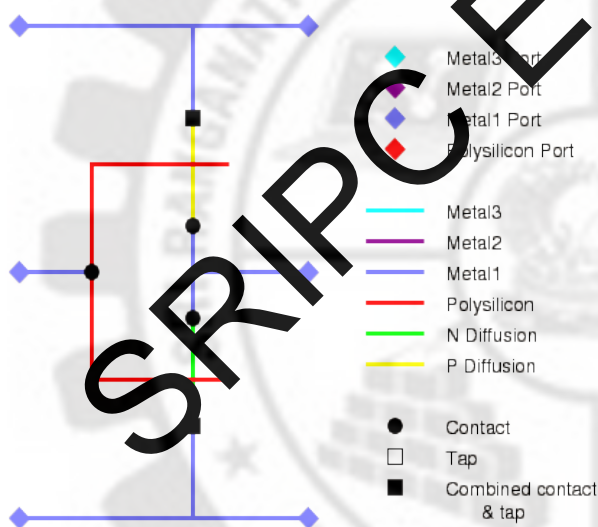

ROUTING

Standard cell row

Standard cells

Macros

SRIPC ECE
UNIT-II
INTRODUCTION TO VHDL

SWATHI E R
LECTURER/ECE

764 - SRIPC

History of VHDL

- Designed by IBM, Texas Instruments, and Intermetrics as part of the DoD funded VHSIC program
- Standardized by the IEEE in 1987: IEEE 1076-1987
- Enhanced version of the language defined in 1993: IEEE 1076-1993
- Additional standardized packages provide definitions of data types and expressions of timing data
 - IEEE 1164 (data types)
 - IEEE 1076.3 (numeric)
 - IEEE 1076.4 (timing)

Traditional vs. Hardware Description Languages

- Procedural programming languages provide the *how* or recipes
 - for computation
 - for data manipulation
 - for execution on a specific hardware model
- Hardware description languages *describe* a system
 - Systems can be described from many different points of view
 - Behavior: what does it do?
 - Structure: what is it composed of?
 - Functional properties: how do I interface to it?
 - Physical properties: how fast is it?


Usage

- Descriptions can be at different levels of abstraction
 - Switch level: model switching behavior of transistors
 - Register transfer level: model combinational and sequential logic components
 - Instruction set architecture level: functional behavior of a microprocessor
- Descriptions can be used for
 - Simulation
 - Verification, performance evaluation
 - Synthesis
 - First step in hardware design


Why do we Describe Systems?

- Design Specification
 - unambiguous definition of components and interfaces in a large design
- Design Simulation
 - verify system/subsystem/chip performance prior to design implementation
- Design Synthesis
 - automated generation of a hardware design

Digital System Design Flow

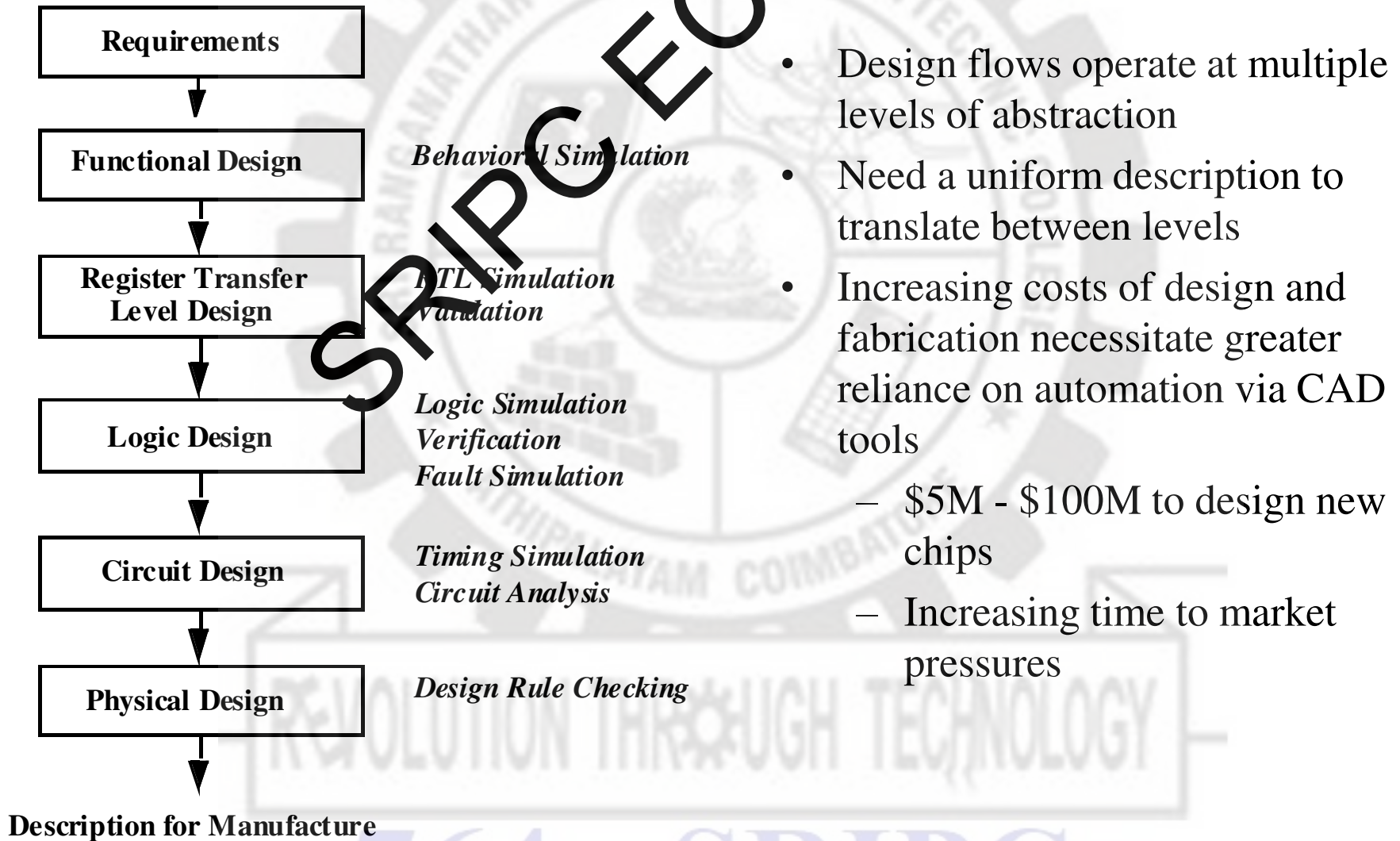


A Synthesis Design Flow

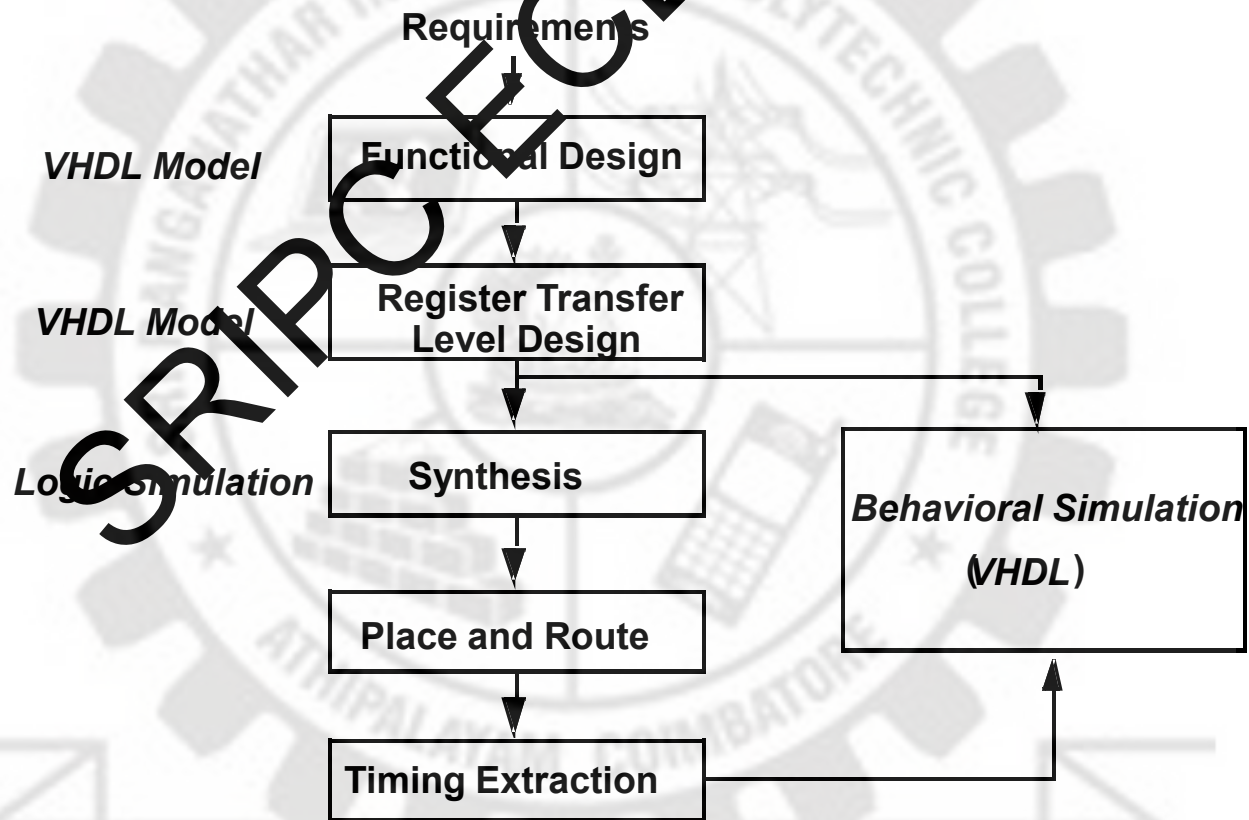

- Automation of design refinement steps
- Feedback for accurate simulation
- Example targets: ASICs, FPGAs

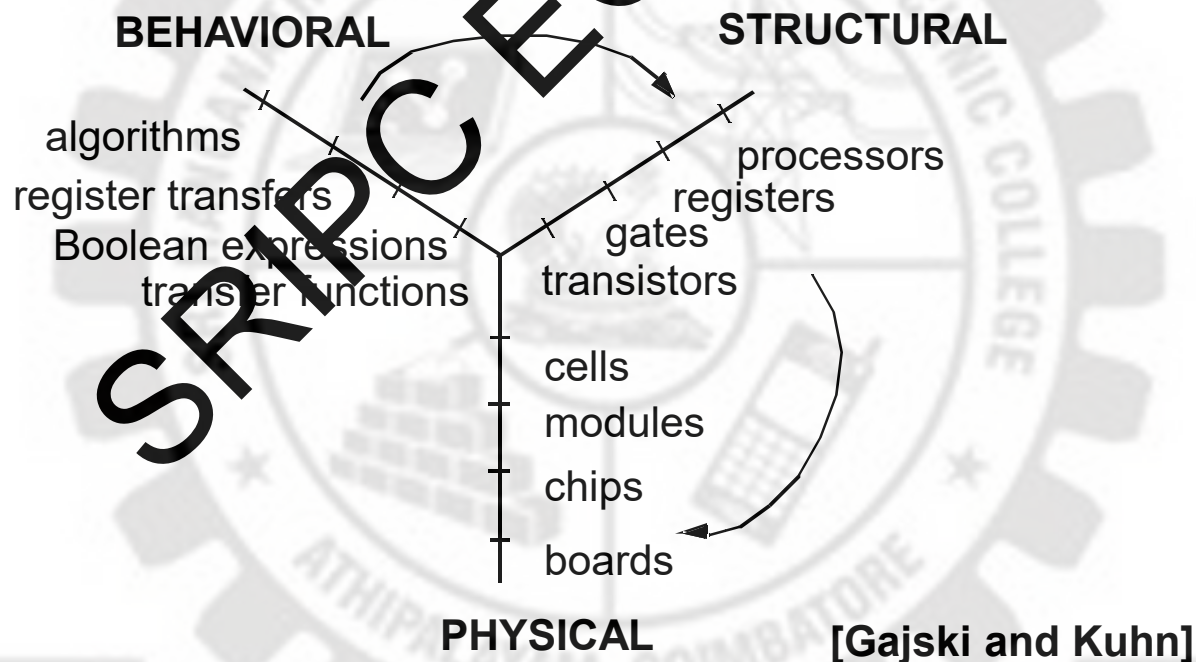The Role of Hardware Description Languages




- Design is structured around a hierarchy of representations
- HDLs can describe distinct aspects of a design at multiple levels of abstraction

Domains and Levels of Modeling

Structural

Functional

SRIPC ECE

 

high level of abstraction

low level of abstraction

Geometric

“Y-chart” due to Gajski & Kahn

Domains and Levels of Modeling

Structural

Functional

*Algorithm
(behavioral)*

*Register-Transfer
Language*

Boolean Equation


Differential Equation

Geometric

“Y-chart” due to
Gajski & Kahn

764 - SRIPC

Domains and Levels of Modeling

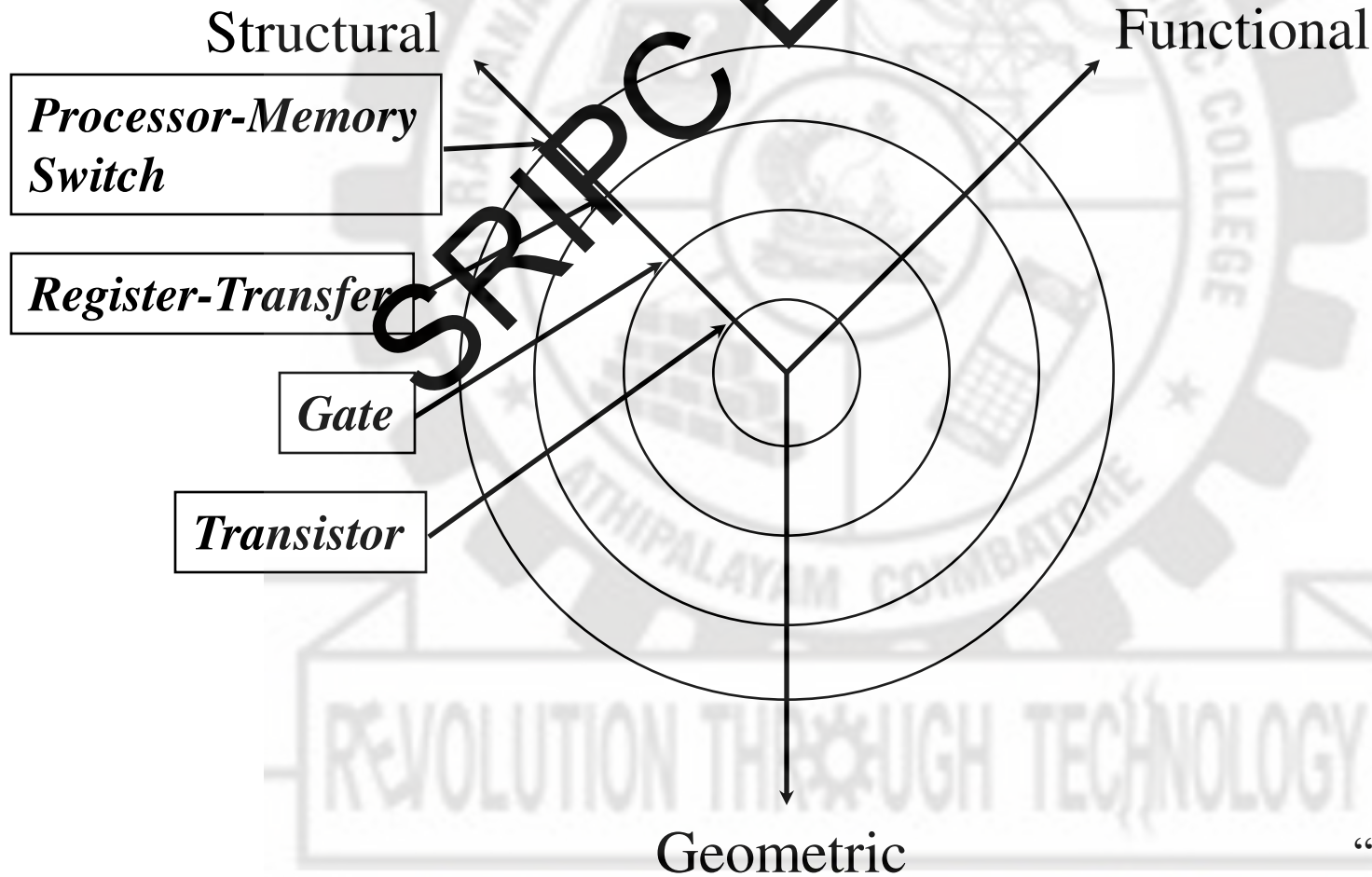


“Y-chart” due to Gajski & Kahn

Domains and Levels of Modeling

Structural

Functional

SRIPC ECE

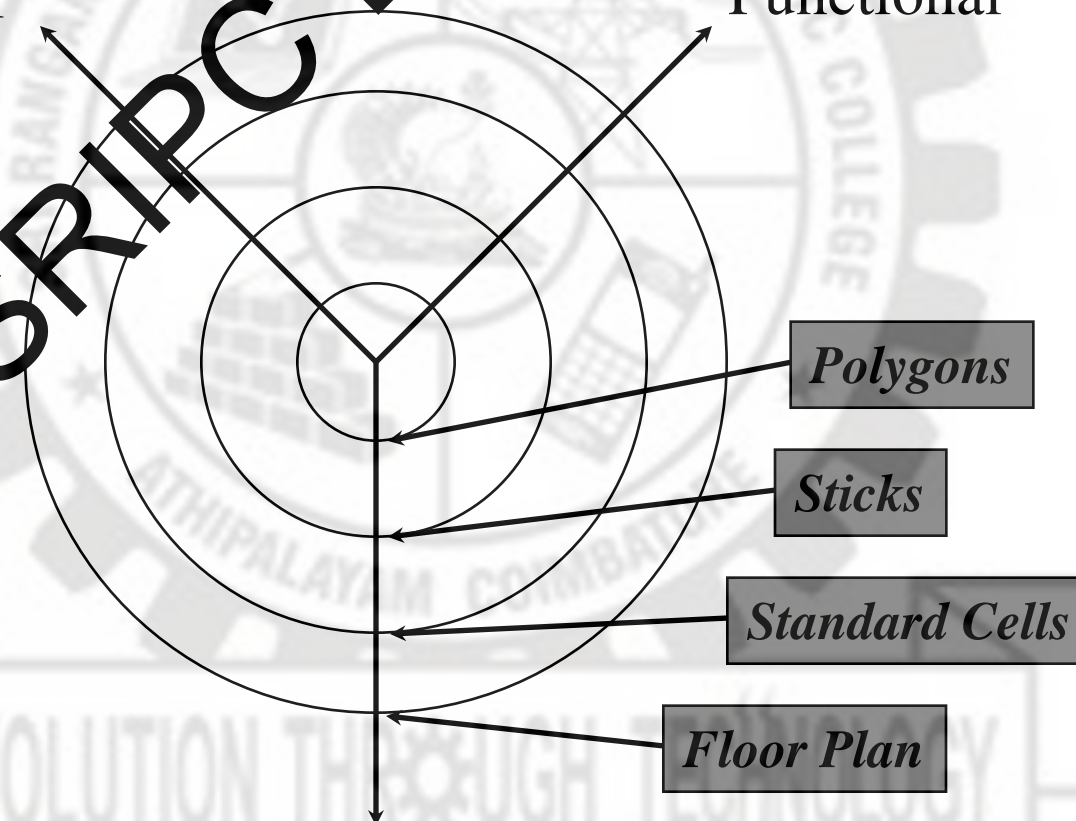

Geometric


“Y-chart” due to Gajski & Kahn

Basic VHDL Concepts

- Interfaces
- Modeling (Behavior, Dataflow, Structure)
- Test Benches
- Analysis, elaboration, simulation
- Synthesis

Basic Structure of a VHDL File

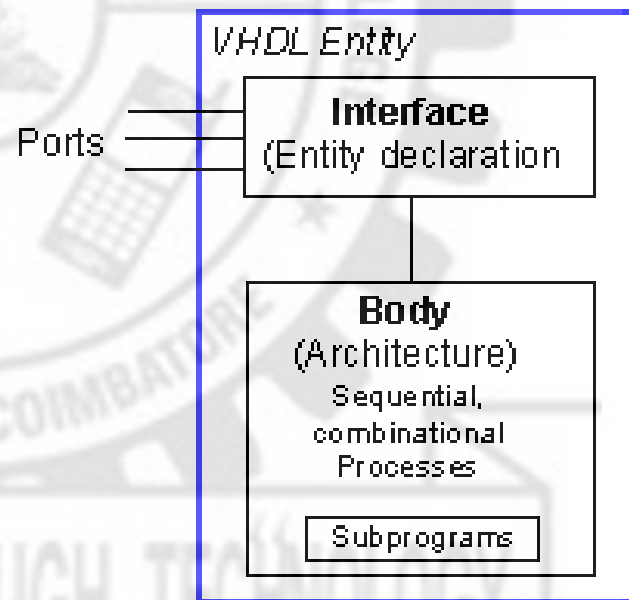- Entity
 - Entity declaration: interface to outside world; defines input and output signals
 - Architecture: describes the entity, contains processes, components operating concurrently



Entity Declaration

```

entity NAME_OF_ENTITY is
  port (signal_names: mode type;
        signal_names: mode type;
        signal_names: mode type);
end [NAME_OF_ENTITY] ;
  
```

MVL - 9			
Uninitialized	'U'	Weak 1	'H'
Don't Care	'-'	Weak 0	'L'
Forcing 1	'1'	Weak Unknown	'W'
Forcing 0	'0'	High Impedance	'Z'
Forcing Unknown	'X'		

- NAME_OF_ENTITY: user defined
- signal_names: list of signals (both input and output)
- mode: in, out, buffer, inout
- type: boolean, integer, character, std_logic

Architecture

- **Behavioral Model:**

```
architecture architecture_name of NAME_OF_ENTITY  
is
```

```
-- Declarations
```

```
.....
```

```
.....
```

```
begin
```

```
-- Statements
```

```
end architecture_name;
```

VHDL Process

- Group of Instructions that are executed sequentially

- Syntax

process

declarations;

begin

sequential statement;

sequential statement;

...


end process;

- The whole process is a concurrent statement

STATEMENTS

- An if...else statement is a **sequential statement** in VHDL which got executed depending on the value of the condition. The if condition tests each condition sequentially until the true condition is found.
- VHDL is a Hardware Description Language that is used to describe at a high level of abstraction a digital circuit in an FPGA or ASIC. **When we need to perform a choice or selection between two or more choices**, we can use the VHDL conditional statement.
- VHDL entity example. The entity syntax is **keyword “entity”**, **followed by entity name and the keyword “is” and “port”**. Then inside parenthesis there is the ports declaration. In the port declaration there are port name followed by colon, then port direction (in/out in this example) followed by port type.

Half Adder

 

```

library ieee;
use ieee.std_logic_1164.all;
entity half_adder is
port(
    x,y: in std_logic;
    sum, carry: out std_logic);
end half_adder;

```

```

architecture myadd of half_adder is
begin

```

```

    sum <= x xor y;
    carry <= x and y;

```

```

end myadd;

```

Entity Examples ...

entity half_adder is

port(

 x,y: in std_logic;

 sum,carry: out std_logic);

end half_adder;




Architecture Examples: Behavioral Description

- Entity FULLADDER is
port (
A, B, C: in std_logic;
SUM, CARRY: in std_logic);
end FULLADDER;
- Architecture CONCURRENT of FULLADDER is
begin
SUM <= A xor B xor C after 5 ns;
CARRY <= (A and B) or (B and C) or (A and C) after 3
ns;
end CONCURRENT;

Architecture Examples: Structural Description ...

- architecture **STRUCTURAL** of **FULL_ADDER** is
 signal S1, C1, C2 : bit;
 component HA
 port (I1, I2 : in bit; S, C : out bit);
 end component;
 component OR
 port (I1, I2 : in bit; X : out bit);
 end component;
 begin
 INST_HA1 : HA port map (I1 => B, I2 => C, S => S1, C => C1);
 INST_HA2 : HA port map (I1 => A, I2 => S1, S => SUM, C => C2);
 INST_OR : OR port map (I1 => C2, I2 => C1, X => CARRY);
 end **STRUCTURAL**;

 


... Architecture Examples: Structural Description

```
Entity HA is
PORT (I1, I2 : in bit; S, C : out bit);
end HA ;
Architecture behavior of HA is
begin
    S <= I1 xor I2;
    C <= I1 and I2;
end behavior;
```

```
Entity OR is
PORT (I1, I2 : in bit; X : out bit);
end OR ;
Architecture behavior of OR is
begin
    X <= I1 or I2;
end behavior;
```

One Entity Many Descriptions

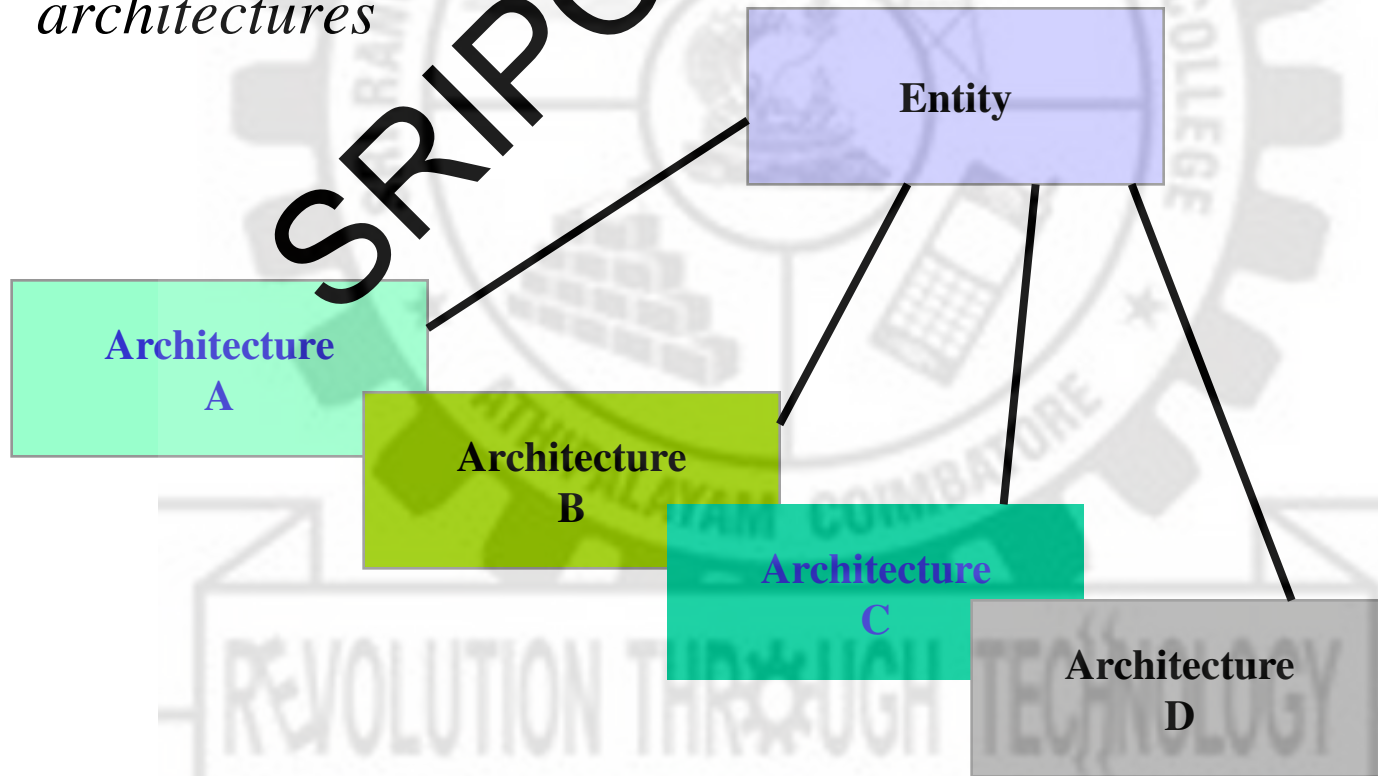- A system (an *entity*) can be specified with different *architectures*



Test Benches

- Testing a design by simulation
- Use a *test bench* model
 - an architecture body that includes an instance of the design under test
 - applies sequences of test values to inputs
 - monitors values on output signals
 - either using simulator
 - or with a process that verifies correct operation

PROGRAM

- **VHDL CODES:**
- **OR gate program**
- library IEEE;
- use IEEE.STD_LOGIC_1164.ALL; use IEEE.STD_LOGIC_ARITH.ALL;
- use IEEE.STD_LOGIC_UNSIGNED.ALL;
- entity gate is
- Port (a : in STD_LOGIC; b : in STD_LOGIC;
- c : out STD_LOGIC); end gate;
- architecture Behavioral of gate is begin
- c <= a or b;
- end Behavioral;
- **ANDgate Program**
- library IEEE;
- use IEEE.STD_LOGIC_1164.ALL; use IEEE.STD_LOGIC_ARITH.ALL;
- use IEEE.STD_LOGIC_UNSIGNED.ALL;
- entity gate is
- Port (a : in STD_LOGIC; b : in STD_LOGIC;
- c : out STD_LOGIC); end gate;
- architecture Behavioral of gate is begin
- c <= a and b; end Behavioral;

764 - SRIPC

PROGRAM

- **VHDL CODES:**
- **NOT gate program**
- library IEEE;
- use IEEE.STD_LOGIC_1164.ALL; use IEEE.STD_LOGIC_ARITH.ALL;
- use IEEE.STD_LOGIC_UNSIGNED.ALL;
- entity gate is
- Port (a : in STD_LOGIC); end gate;
- architecture Behavioral of gate is begin
- c <= a not b;
- end Behavioral;
- **NANDgate Program**
- library IEEE;
- use IEEE.STD_LOGIC_1164.ALL; use IEEE.STD_LOGIC_ARITH.ALL;
- use IEEE.STD_LOGIC_UNSIGNED.ALL;
- entity gate is
- Port (a : in STD_LOGIC; b : in STD_LOGIC;
- c : out STD_LOGIC); end gate;
- architecture Behavioral of gate is begin
- c <= a nand b; end Behavioral;

764 - SRIPC

PROGRAM

- **VHDL CODES:**
- **Nor gate Program**
- library IEEE;
- use IEEE.STD_LOGIC_1164.ALL; use IEEE.STD_LOGIC_ARITH.ALL;
- use IEEE.STD_LOGIC_UNSIGNED.ALL;
- entity gate is
- Port (a : in STD_LOGIC; b : in STD_LOGIC;
- c : out STD_LOGIC); end gate;
- architecture Behavioral of gate is begin
- c <= a nand b; end Behavioral;
- **Exor gate Program**
- library IEEE;
- use IEEE.STD_LOGIC_1164.ALL; use IEEE.STD_LOGIC_ARITH.ALL;
- use IEEE.STD_LOGIC_UNSIGNED.ALL;
- entity gate is
- Port (a : in STD_LOGIC; b : in STD_LOGIC;
- c : out STD_LOGIC); end gate;
- architecture Behavioral of gate is begin
- c <= a exor b; end Behavioral;

764 - SRIPC

SRIPC ECE
UNIT-III
COMBINATIONAL CIRCUIT DESIGN


SWATHI E R
LECTURER/ECE

764 - SRIPC

Combinational Circuits




Combinational circuits

 

- So far we've just worked with **combinational circuits**, where applying the same inputs always produces the same outputs.
- This corresponds to a mathematical function, where every input has a single, unique output.
- In programming terminology, combinational circuits are similar to "functional programs" that do not contain variables and assignments.


HALF ADDER

 

Half Adder


REVOLUTION THROUGH TECHNOLOGY

TRUTH TABLE

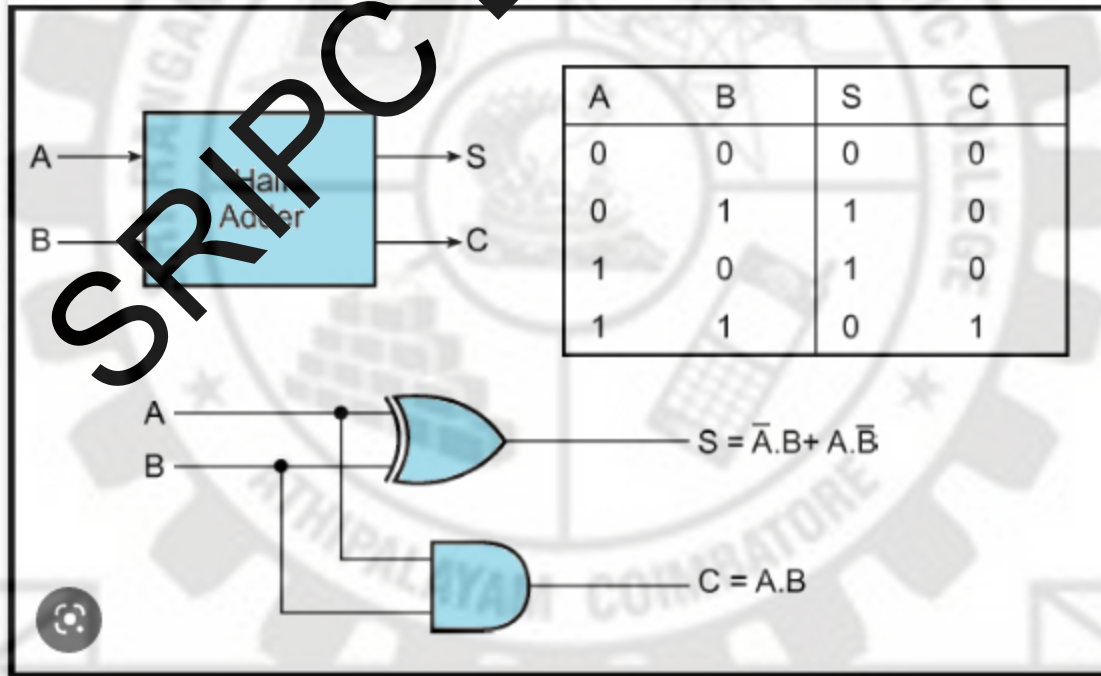


FULL ADDER

SRIPC ECE

 

764 - SRIPC

TRUTH TABLE

 

Inputs			Outputs	
A	B	C_{in}	S	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

764 - SRIPC

HALF SUBTRACTOR




TRUTH TABLE

Inputs		Outputs	
A	B	Difference	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

764 - SRIPC

FULL SUBTRACTOR

 

764 - SRIPC

TRUTH TABLE


INPUT			OUTPUT	
A	B	Bin	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

764 - SRIPC

4 TO 1 MUX


Input	S1	S0	Y
I ₀	0	0	I ₀
I ₁	0	1	I ₁
I ₂	1	0	I ₂
I ₃	1	1	I ₃
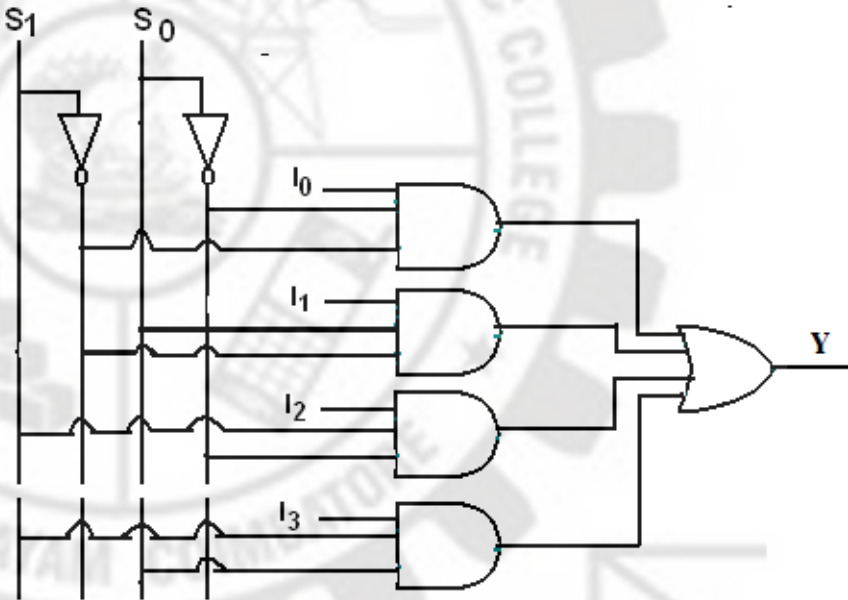
$$Y = S_1 S_0 I_3 + S_1 \bar{S}_0 I_2 + \bar{S}_1 S_0 I_1 + \bar{S}_1 \bar{S}_0 I_0$$




4 to 1 Multiplexer and its truth table


1 TO 4 DEMUX

 


4 TO 2 ENCODER

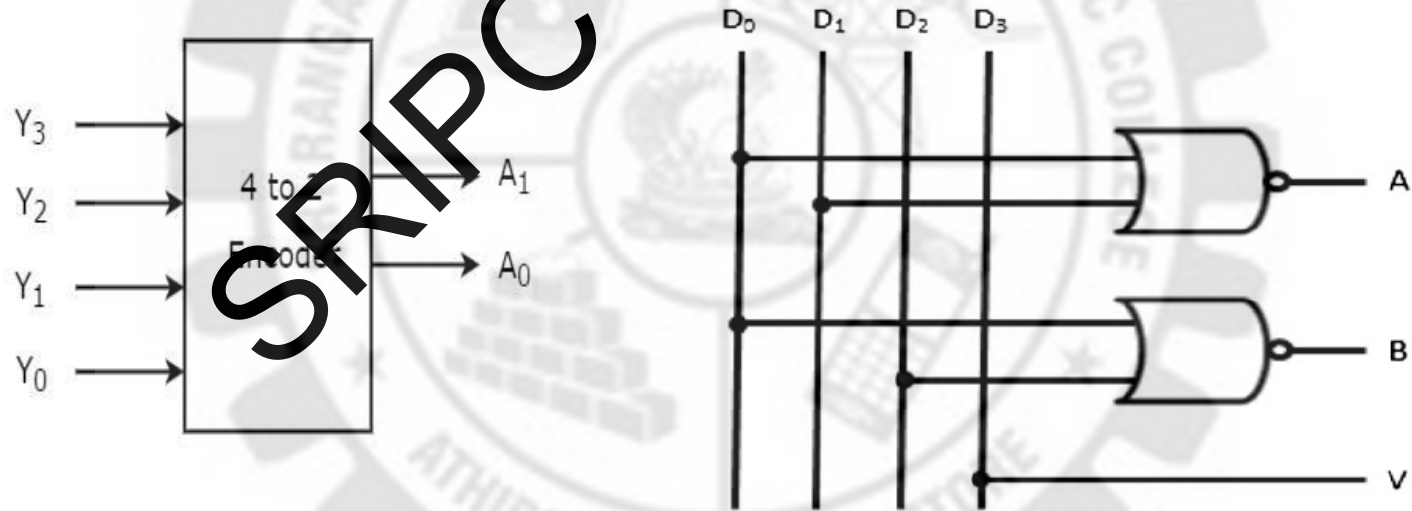

2 TO 4 DECODER

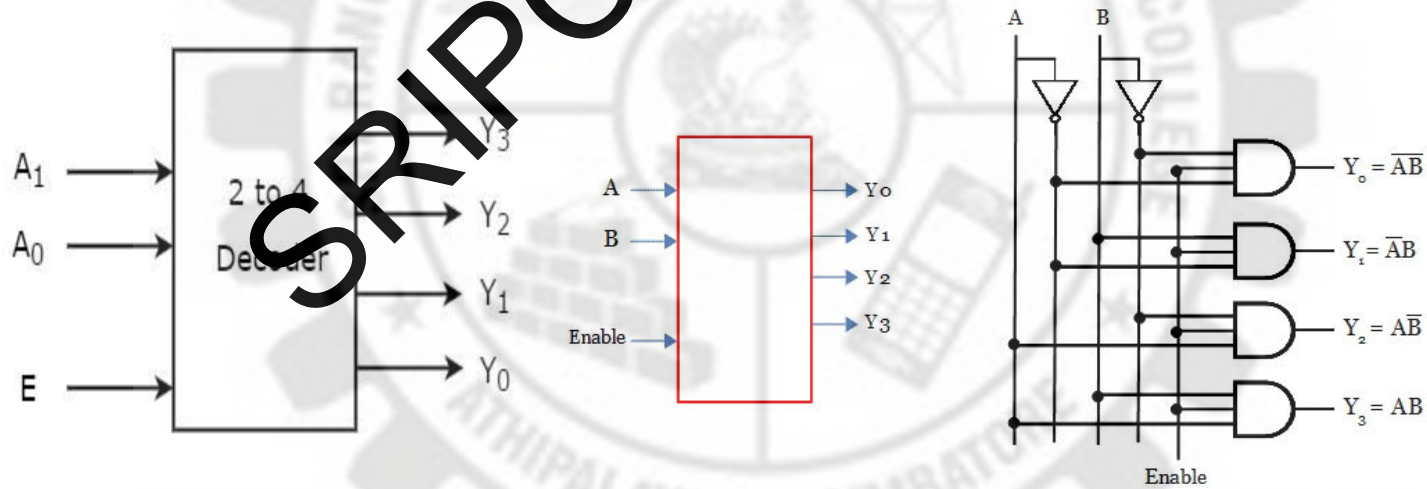


COMPARATOR

 

764 - SRIPC


4 BIT ADDER

 

REVOLUTION THROUGH TECHNOLOGY

764 - SRIPC

4 BIT SUBTRACTOR

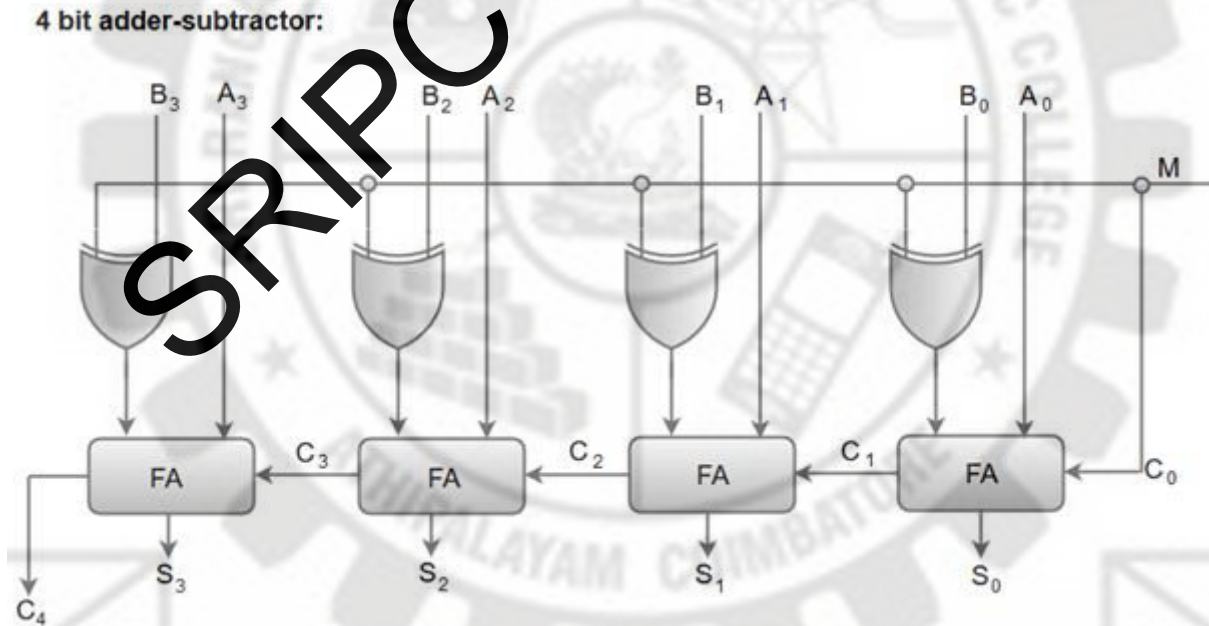

REVOLUTION THROUGH TECHNOLOGY

764 - SRIPC

VHDL PROGRAM FOR HALF ADDER

VHDL Code half adder

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity half_adder is
    port(a,b:in bit; sum,carry:out bit);
end half_adder;

architecture data of half_adder is
begin
    sum<= a xor b;
    carry <= a and b;
end data;
```

764 - SRIPC

VHDL PROGRAM FOR FULL ADDER

Full adder Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity full_adder is port
(a,b,c:in bit; sum,carry:out bit);
end full_adder;

architecture data of full_adder is
begin
    sum<= a xor b xor c;
    carry <= ((a and b) or (b and c) or (a and c));
end data;
```

764 - SRIPC

VHDL PROGRAM FOR HALF SUBTRACTOR

- library IEEE;
- use IEEE.STD_LOGIC_1164.ALL; use IEEE.STD_LOGIC_ARITH.ALL;
- use IEEE.STD_LOGIC_UNSIGNED.ALL;
-
- Library ieee;
- use ieee.std_logic_1164.all;
-
- entity half_sub is
- port (a,b : in std_logic; dif,bo: out std_logic);
- end half_sub;
-
- architecture sub_arch of half_sub is begin
- dif <= a xor b;
- bo <= (not a) and b; end sub_arch;

VHDL PROGRAM FOR FULL SUBTRACTOR

- library IEEE;
- use IEEE.STD_LOGIC_1164.ALL; use IEEE.STD_LOGIC_ARITH.ALL;
- use IEEE.STD_LOGIC_UNSIGNED.ALL;
-
- entity full_sub is
- port(a,b,c: in bit; sub, borrow:out bit); end full_sub;
- architecture data of full_sub is beginsub<= a xor b xor c;
- borrow <= ((b xor c) and (not a))or (b and c);
- end data;

VHDL PROGRAM FOR SINGLE BIT DIGITAL COMPARATOR

- library IEEE;
- use IEEE.STD_LOGIC_1164.ALL;
- entity comparator_1bit is
- Port (A,B in std_logic; G,S,E: out std_logic);
- end comparator_1bit;
- architecture comp_arch of comparator_1bit is
begin
- $G \leq A \text{ and } (\text{not } B)$; $S \leq (\text{not } A) \text{ and } B$; $E \leq A \text{ xnor } B$;
- end comp_arch;

VHDL PROGRAM FOR ENCODER

- library IEEE;
- use IEEE.STD_LOGIC_1164.ALL; use IEEE.STD_LOGIC_ARITH.ALL;
- use IEEE.STD_LOGIC_UNSIGNED.ALL;
- entity first is
- port (input : in std_logic_vector(3 downto 0); output : out std_logic_vector(1 downto 0)); end first;
- architecture Behavioral of first is begin
- process(input) begin
- case input is
- when "0001" =>output <= "00";
- when "0010" =>output <= "10";
- when "0100" =>output <= "01";
- when "1000" =>output <= "11"; when others =>null;
- end case; end process;
- end Behavioral;

VHDL PROGRAM FOR DECODER

- Library ieee;
- use ieee.std_logic_1164.all; use ieee.std_logic_arith.all; use ieee.std_logic_unsigned.all;
- entity object_co is port (clk : in std_logic;
- sw : in std_logic_vector(3 downto 0); y : out std_logic_vector(7 downto 0);
- -- sel : out std_logic_vector(5 downto 3) sel : out std_logic_vector(5 downto 0)
-);
- end object_co;

Four bit Arithmetic adder

- LIBRARY IEEE;
- USE IEEE STD_LOGIC_1164.ALL;
- USE IEEE STD_LOGIC_ARITH.ALL;
- ENTITY ADDER_4 BIT IS
- PORT(A:IN STD_LOGIC_VECTOR(3 DOWN TO 0);
(B:IN STD_LOGIC_VECTOR(3 DOWN TO 0);
- CARRY:OUT STD_LOGIC;
- S:OUT STD_LOGIC_VECTOR(3 DOWN TO 0);
- END ADDER_4 BIT;

- ARCHITECTURE ADDER_4 BIT IS
- COMPONENT FA
- PORT(X:IN STD_LOGIC;
- Y:IN STD_LOGIC;
- CI:IN STD_LOGIC;
- SUM:OUT STD_LOGIC;
- CY:OUT STD_LOGIC);
- END COMPONENT;
- SIGNAL C0,C1,C2,C3:STD_LOGIC;
- BEGIN;

- `BBAR<=NOT B;`
- `FA0:FA PORT MAP(A(0)),BBAR(0),'1',D(0)C(0);`
- `FA1:FA PORT MAP(A(1)),BBAR(0),'1',D(0)C(0);`
- `FA2:FA PORT MAP(A(2)),BBAR(0),'1',D(0)C(0);`
- `FA3:FA PORT MAP(A(3)),BBAR(0),'1',D(0)C(0);`
- `CARRY<=C3;`
- `END ARCH_4;`

Four bit Arithmetic SUBTRACTOR

- LIBRARY IEEE;
- USE IEEE STD_LOGIC_1164.ALL;
- USE IEEE STD_LOGIC_ARITH.ALL;
- ENTITY SUB_4 BIT IS
- PORT(A:IN STD_LOGIC_VECTOR(3 DOWN TO 0);
(B:IN STD_LOGIC_VECTOR(3 DOWN TO 0);
- D:OUT STD_LOGIC;
- OV:OUT STD_LOGIC_VECTOR(3 DOWN TO 0);
- END SUB_4 BIT;

- ARCHITECTURE SUB_ARC OF ADDER_4 BIT IS
- COMPONENT FA
- PORT(X:IN STD_LOGIC;
- Y:IN STD_LOGIC;
- CI:IN STD LOGIC;
- SUM:OUT STD_LOGIC;
- CY:OUT STD_LOGIC);
- END COMPONENT;
- SIGNAL C0,C1,C2,C3:STD_LKOGIC;
- BEGIN;

- `BBAR<=NOT B;`
- `FA0:FA PORT MAP(A(0)),BBAR(0),'1',D(0)C(0);`
- `FA1:FA PORT MAP(A(1)),BBAR(0),'1',D(0)C(0);`
- `FA2:FA PORT MAP(A(2)),BBAR(0),'1',D(0)C(0);`
- `FA3:FA PORT MAP(A(3)),BBAR(0),'1',D(0)C(0);`
- `OV<=C2 XOR C3;`
- `END SUB_4;`

SRIPC ECE


UNIT-IV

SEQUENTIAL CIRCUIT DESIGN

SWATHI E R
LECTURER/ECE


764 - SRIPC

SEQUENTIAL CIRCUIT DESIGN

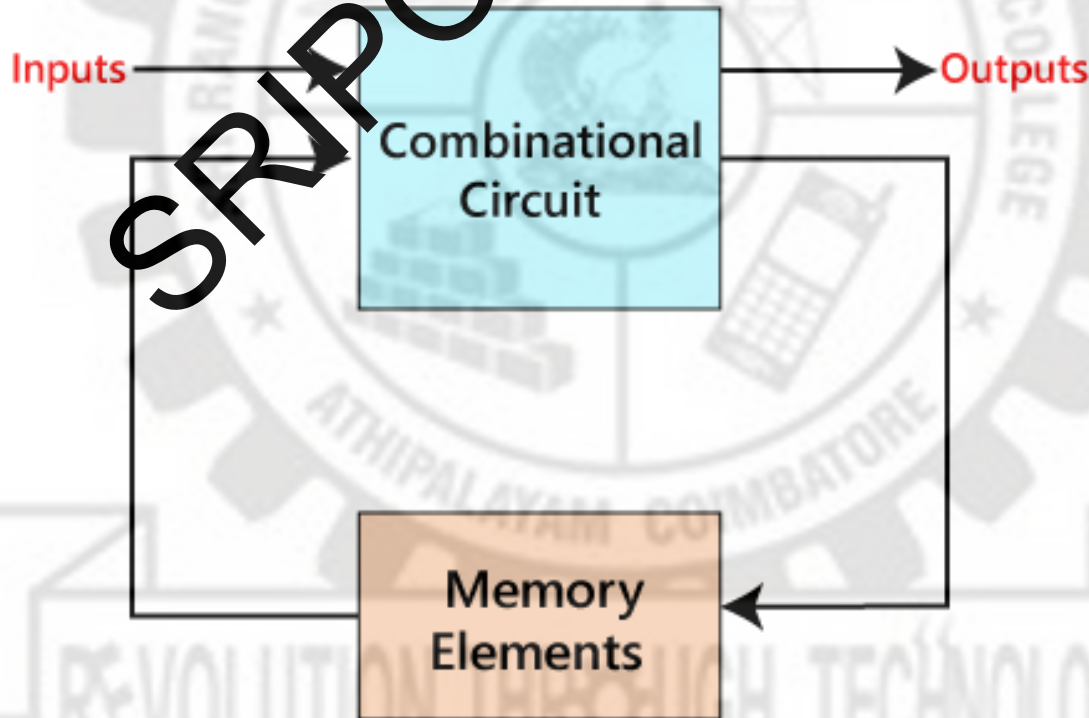

JK FLIP-FLOPS

JK Flip-Flop Symbol

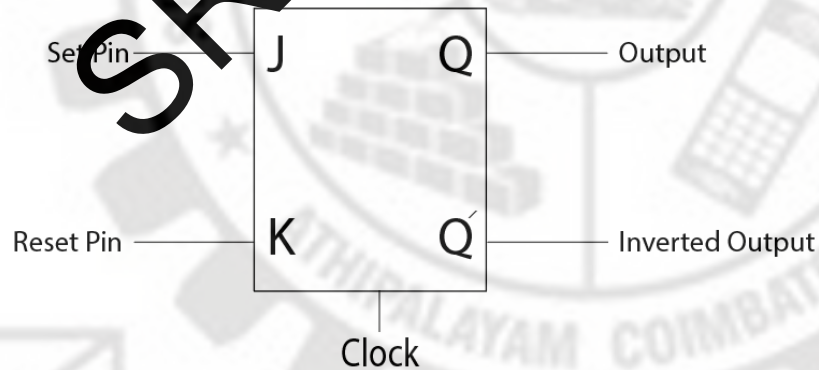


JK Flip-Flop Logic Table


C	J	K	Q	Q'
HIGH	0	0	Latch	Latch
HIGH	0	1	0	1
HIGH	1	0	1	0
HIGH	1	1	Toggle	Toggle
LOW	0	0	Latch	Latch
LOW	0	1	Latch	Latch
LOW	1	0	Latch	Latch
LOW	1	1	Latch	Latch

Introduction to JK Flip Flop


D FLIPFLOPS

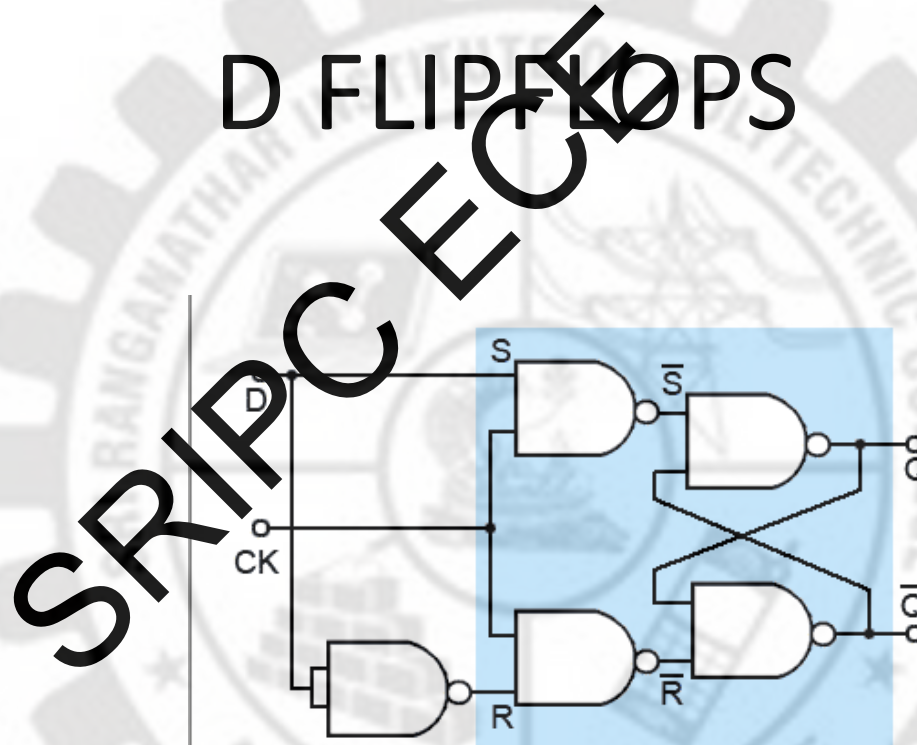

Inputs		Outputs	
CK	D	Q	\bar{Q}
0	X	No change	
1	0	0	1
1	1	1	0

 


T FLIPFLOPS

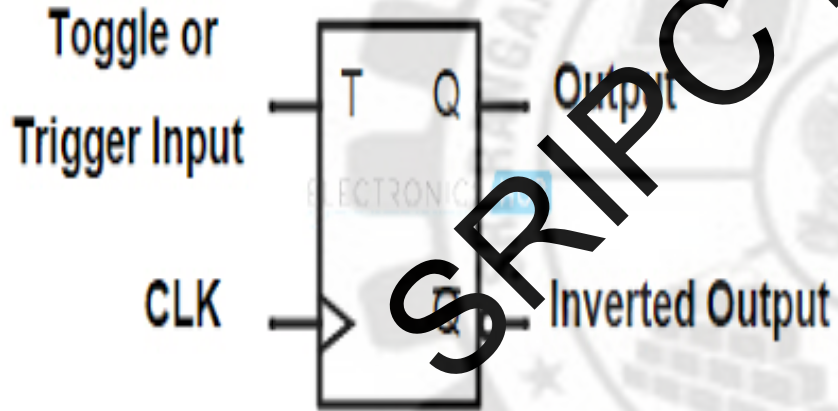

T	Q _n	Q _{n+1}	J	K
0	0	0	0	x
0	1	1	x	0
1	0	1	1	x
1	1	0	x	1


3 BIT SYNCHRONOUS UP COUNTER

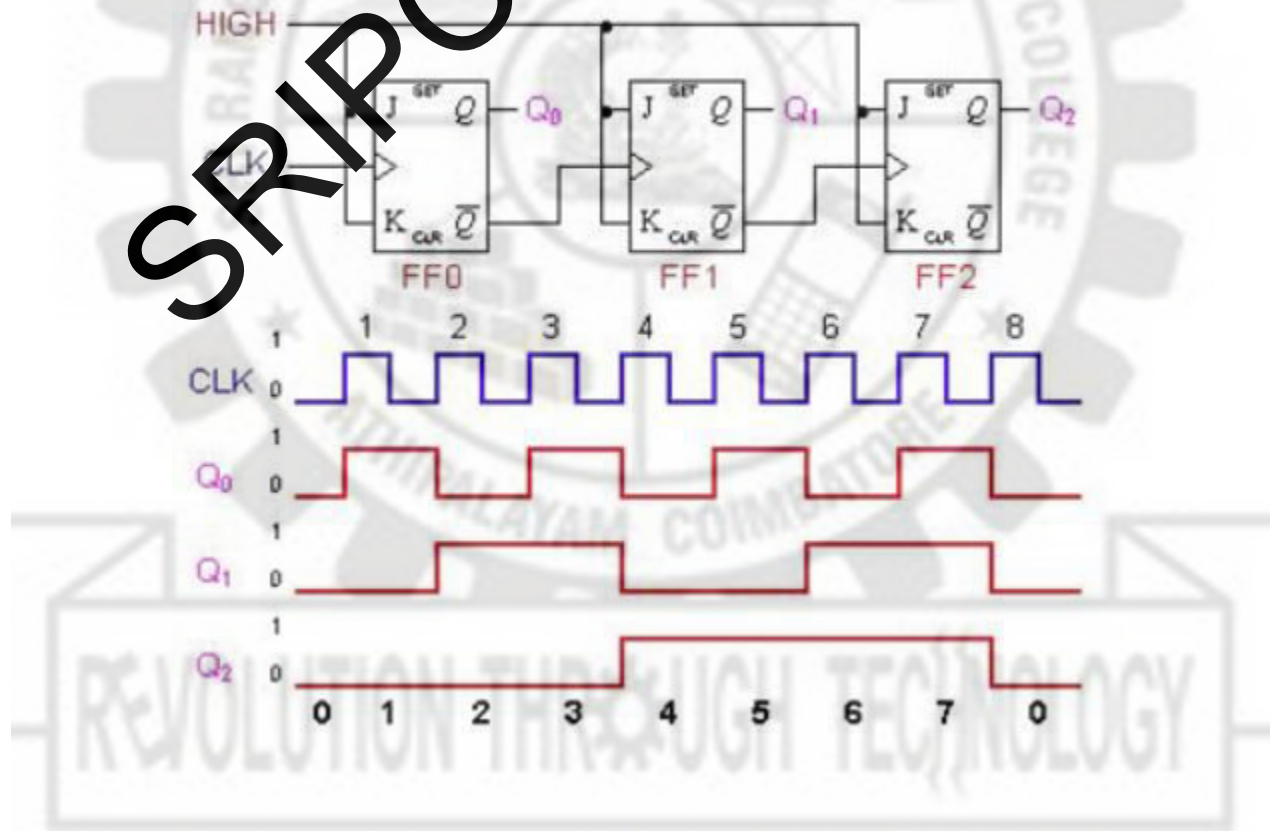

764 - SRIPC


3 BIT SYNCHRONOUS DOWN COUNTER

Logic Diagram for 3-bit Down Counter:

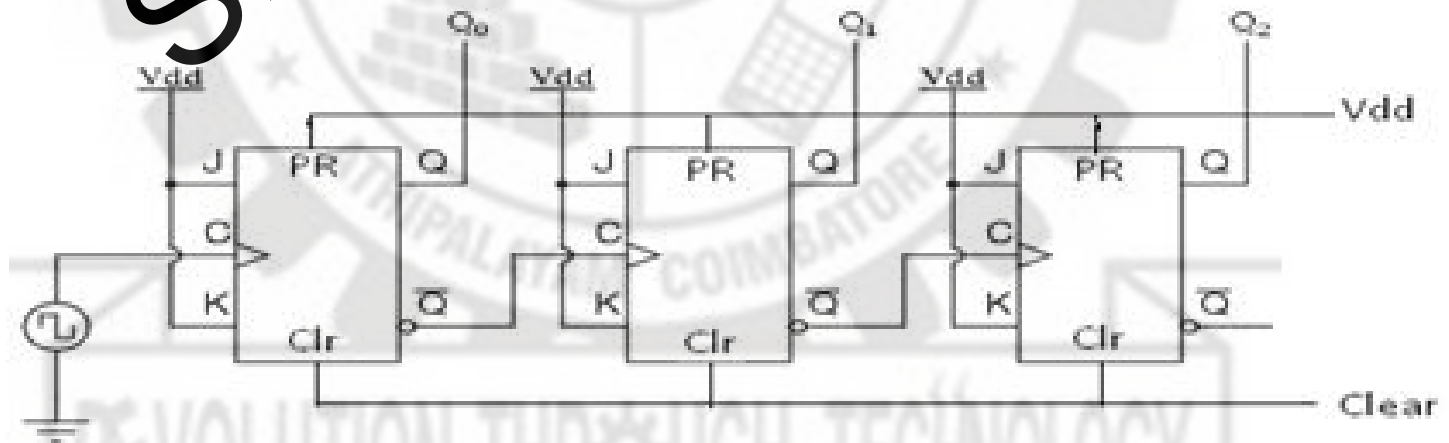


764 - SRIPC

3 BIT SYNCHRONOUS UP/DOWN

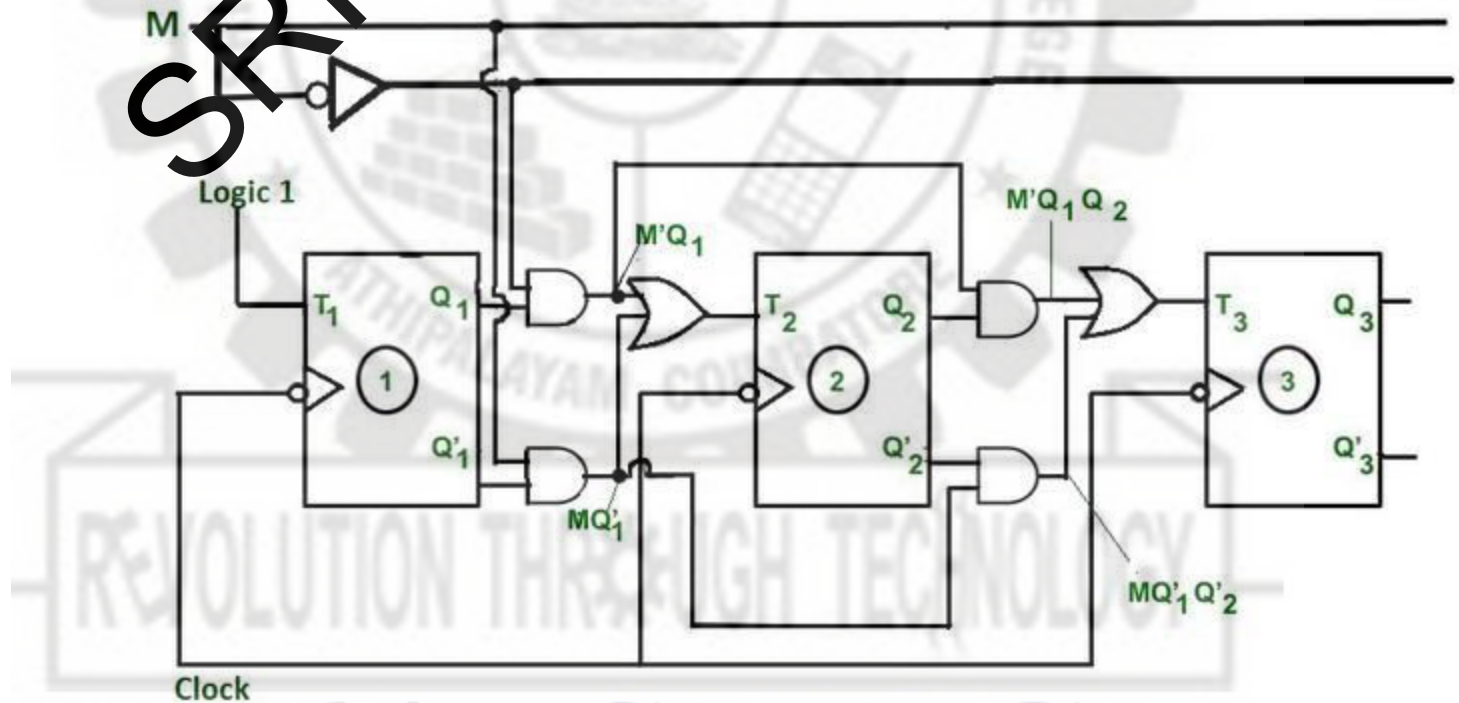


764 - SRIPC

3 BIT ASYNCHRONOUS UP COUNTER

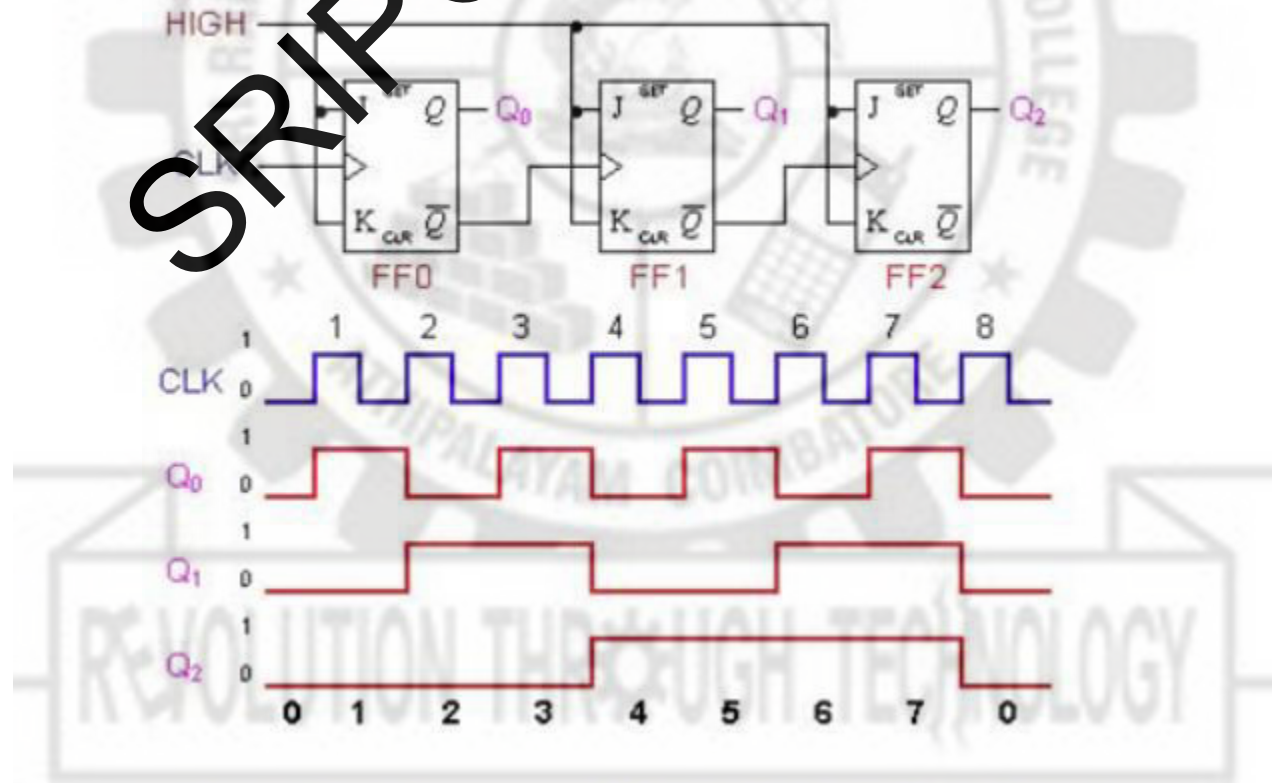


764 - SRIPC

3 BIT ASYNCHRONOUS DOWN COUNTER

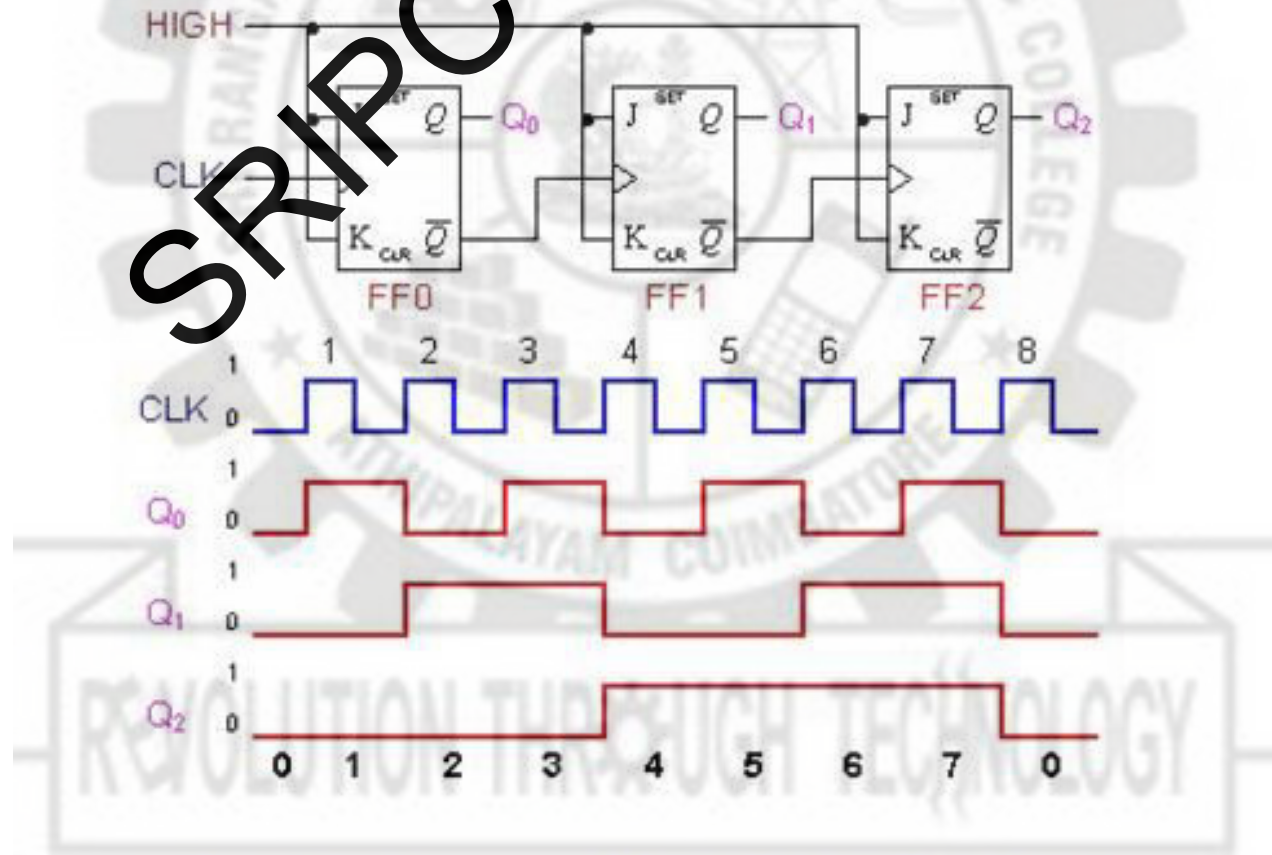


764 - SRIPC

3 BIT ASYNCHRONOUS UP/DOWN COUNTER

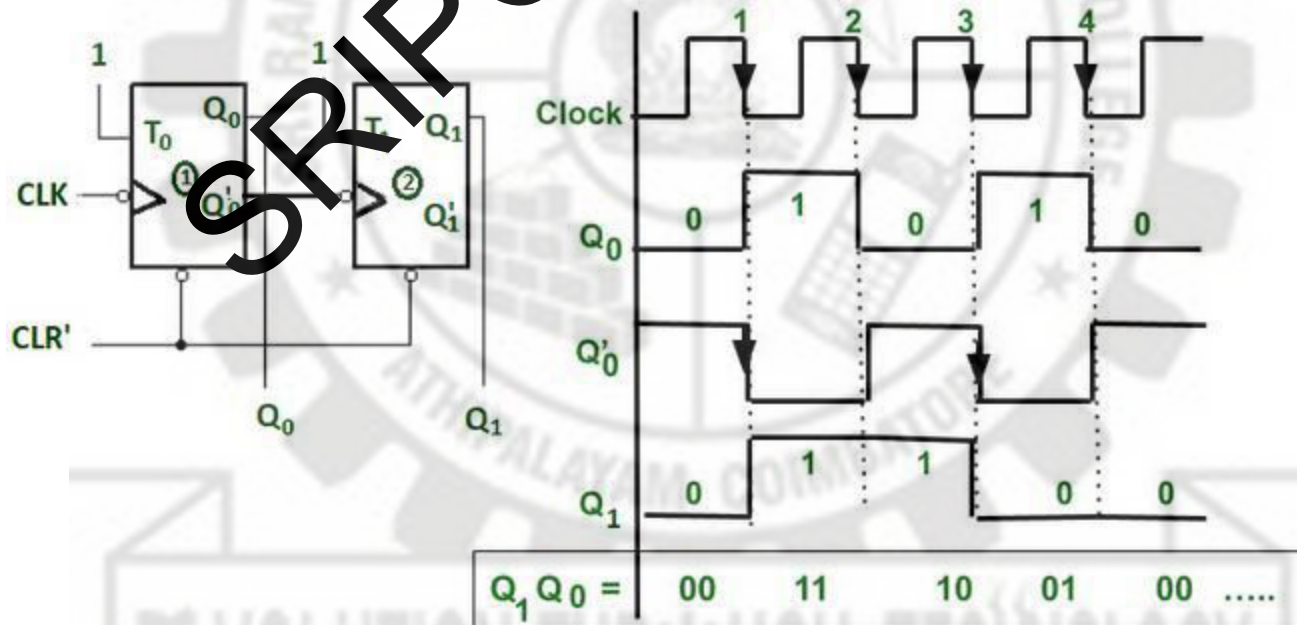

Decade counter

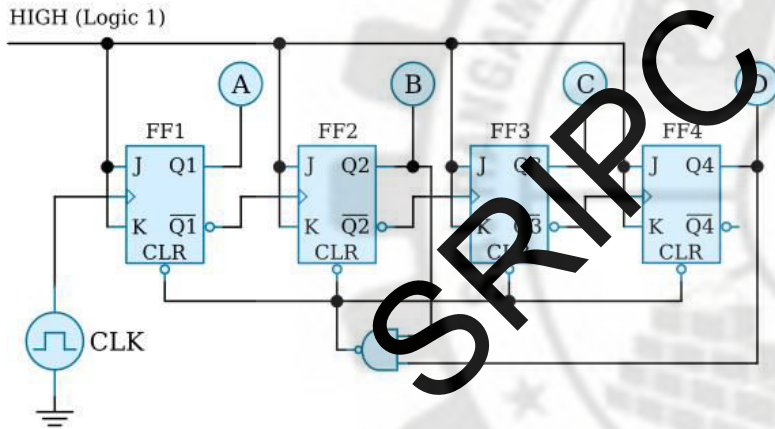


Input Pulses	D	C	B	A
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
0	0	0	0	0 (resets)


REVOLUTION THROUGH TECHNOLOGY

764 - SRIPC


RING COUNTER

 

CLK	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆
1	1	0	0	0	0	0
2	0	1	0	0	0	0
3	0	0	1	0	0	0
4	0	0	0	1	0	0
5	0	0	0	0	1	0
6	0	0	0	0	0	1

 

What is Johnson Counter?

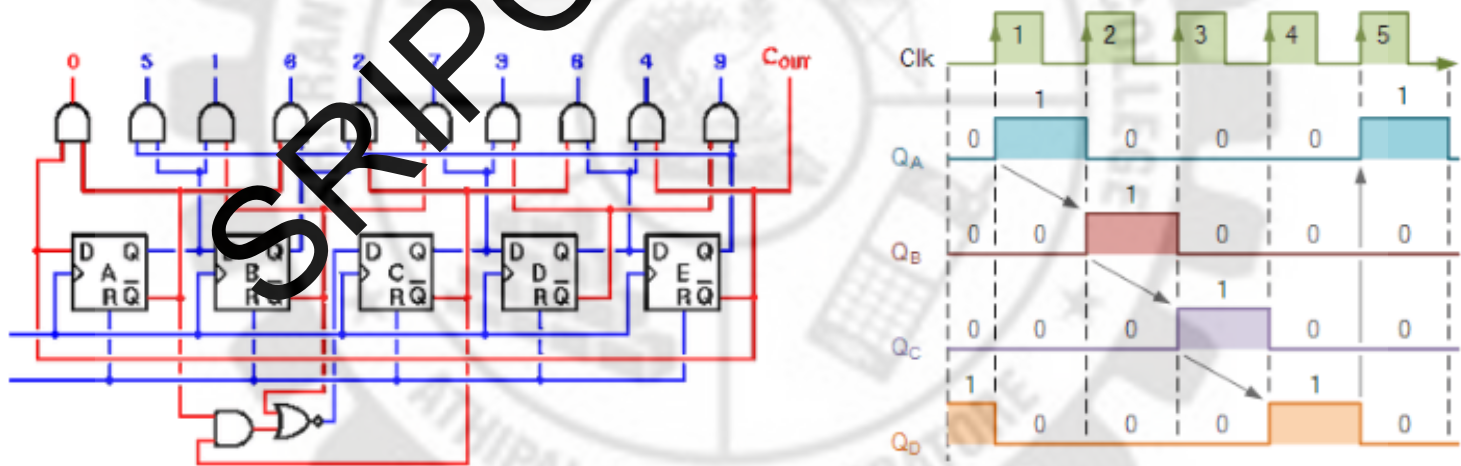

764 - SRIPC

D FLIP FLOP

```
Library IEEE;
USE IEEE.Std_logic_1164.all;
entity RisingEdge_DFlipFlop is
port( Q : out std_logic; Clk : in std_logic;
      D : in std_logic );
end RisingEdge_DFlipFlop;
architecture Behavioral of RisingEdge_DFlipFlop is
begin
  process(Clk)
begin if(rising_edge(Clk))
then Q <= D;
end if;
end process;
end Behavioral;
```

D FLIPFLOP with RESET

```
Library IEEE;
USE IEEE.Std_logic_1164.all;
entity RisingEdge_DFlipFlop is
port( reset,Q : out std_logic; clk :in std_logic;
      D :in std_logic );
end RisingEdge_DFlipFlop;
architecture Behavioral of RisingEdge_DFlipFlop is
begin
  process(Clk)
    Reset="1 then temp='0';"
begin if(rising_edge(Clk))
then Q <= D;
end if;
end process;
end Behavioral;
```

T FLIP FLOPS

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity T_FF is
port( T: in std_logic;
Clock: in std_logic;
Q: out std_logic);
end T_FF;
architecture Behavioral of T_FF is
signal tmp: std_logic;
begin
process (Clock)
begin
if Clock'event and Clock='1' then
if T='0' then
tmp <= tmp;
elsif T='1' then
tmp <= not (tmp);
end if;
end if;
end process;
Q <= tmp;
end Behavioral;
```

T FLIP FLOPS with RESET

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity T_FF is
port( reset,T: in std_logic;
Clock: in std_logic;
Q: out std_logic);
end T_FF;
architecture Behavioral of T_FF is
signal tmp: std_logic;
begin
process (Clock)
begin
if Clock'event and Clock='1' then
Reset="1 then tmp='0';"
if T='0' then
tmp <= tmp;
elsif T='1' then
tmp <= not (tmp);
end if;
end if;
end process;
Q <= tmp;
end Behavioral;
```

764 - SRIPC

J K FLIP FLOPS

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;
entity JK_FF is
PORT(J,K,CLOCK: in std_logic;
Q, QB: out std_logic);
end JK_FF;
Architecture behavioral of JK_FF is
begin
PROCESS(CLOCK)
variable TMP: std_logic;
begin
if(CLOCK='1' and CLOCK'EVENT) then
if(J='0' and K='0')then
TMP:=TMP;
elsif(J='1' and K='1')then
TMP:= not TMP;
elsif(J='0' and K='1')then
TMP:='0';
else
TMP:='1';
end if;
end if;
Q<=TMP;
Q <=not TMP;
end PROCESS;
end behavioral;
```

SRIPC ECE

764 - SRIPC

J K FLIP FLOPS with RESET

```
library ieee;
use ieee. std_logic_1164.all;
use ieee. std_logic_arith.all;
use ieee. std_logic_unsigned.all;
entity JK_FF is
PORT(reset J,K,CLOCK: in std_logic;
Q, QB: out std_logic);
end JK_FF;
Architecture behavioral of JK_FF is
begin
PROCESS(CLOCK)
variable TMP: std_logic;
begin
if(CLOCK='1' and CLOCK'EVENT) then
Reset="1 then temp='0';"
if(J='0' and K='0')then
TMP:=TMP;
elsif(J='1' and K='1')then
TMP:= not TMP;
elsif(J='0' and K='1')then
TMP:='0';
else
TMP:='1';
end if;
end if;
Q<=TMP;
Q <=not TMP;
end PROCESS;
```

SRIPC ECE

764 - SRIPC

VHDL code for synchronous up-counter

```
library IEEE;
  use IEEE.STD_LOGIC_1164.ALL;
  use IEEE.STD_LOGIC_ARITH.ALL;
  ; use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity SOURCE is
  Port ( CLK,RST : in STD_LOGIC;
        COUNT : in out STD_LOGIC_VECTOR (3 downto 0));
end SOURCE;
architecture Behavioral of SOURCE is
begin
  process (CLK,RST)
  begin if (RST = '1')
  then COUNT <= "0000";
  elsif(rising_edge(CLK))
  then COUNT <= COUNT+1;
  end if;
  end process;
end Behavioral;
```

VHDL code for synchronous down-counter

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity is
  Port ( clk,rst : in STD_LOGIC;
        count : out STD_LOGIC_VECTOR (3 downto 0));
end;
architecture Behavioral of down_count is
  signal temp:std_logic_vector(3 downto 0);
begin process(clk,rst)
  begin if(rst='1')
  then temp<="1111";
  elsif(rising_edge(clk))
  then temp<=temp-1;
  end if;
end process;
  count<=temp;
end Behavioral;
```

VHDL code for synchronous updown-counter

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity updown_count is
    Port ( clk,rst,updown : in STD_LOGIC;
          count : out STD_LOGIC_VECTOR (7 downto 0));
end updown_count;
architecture Behavioral of updown_count is
    signal temp:std_logic_vector(3 downto 0):="0000";
Begin
    process(clk,rst)
    begin if(rst='1')
    then temp<="0000"
    ; elsif(rising_edge(clk))
    then if(updown='0')
    then temp<=temp+1;
    else temp<=temp-1;
    end if; end if;
    end process;
    count<=temp;
end Behavioral;
```

VHDL CODE FOR DECADE COUNTER

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity decade is
  Port ( CLOCK : in  STD_LOGIC;
        RESET : in  STD_LOGIC;
        Q : out STD_LOGIC_VECTOR (3 downto 0));
end decade;
architecture Behavioral of decade is
  signal q_tmp: std_logic_vector(3 downto 0):= "0000";
begin
  process(CLOCK,RESET)
  begin
    if RESET = '1' then
      count <= "0000";
    Else if clock'event AND clock='1' then
      If count<count+'1';
    Else
      count <= "0000";
    end if
    Q <= count;
  end process;
end Behavioral;
```

VHDL CODE FOR RING COUNTER

```
• library IEEE;
• use IEEE.STD_LOGIC_1164.ALL;
•
• entity Ring_counter is
•   Port ( CLOCK : in STD_LOGIC;
•         RESET : in STD_LOGIC;
•         Q : out STD_LOGIC_VECTOR (3 downto 0));
• end Ring_counter;
•
• architecture Behavioral of Ring_counter is
•   signal q_tmp: std_logic_vector(3 downto 0):= "0000";
•   begin
•   process(CLOCK,RESET)
•   begin
•   if RESET = '1' then
•     q_tmp <= "0001";
•   elsif Rising_edge(CLOCK) then
•     q_tmp(1) <= q_tmp(0);
•     q_tmp(2) <= q_tmp(1);
•     q_tmp(3) <= q_tmp(2);
•     q_tmp(0) <= q_tmp(3);
•   end if;
•   end process;
•   Q <= q_tmp;
• end Behavioral;
```

VHDL CODE FOR JOHNSON COUNTER

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Johnson_counter is
Port ( clk : in STD_LOGIC;
rst : in STD_LOGIC;
Q : out STD_LOGIC_VECTOR (3 downto 0));
end Johnson_counter;

architecture Behavioral of Johnson_counter is
signal temp: std_logic_vector(3 downto 0) := "0000";
begin
process(clk,rst)
begin
if rst = '1' then
temp <= "0000";
elsif Rising_edge(clk) then
temp(1) <= temp(0);
temp(2) <= temp(1);
temp(3) <= temp(2);
temp(0) <= not temp(3);
end if;
end process;
Q <= temp;
end Behavioral;
```


UNIT-V PROGRAMMABLE LOGIC DEVICES

SRIPC


BY
SWATHI E R
LECTURER
ECE

REVOLUTION THROUGH TECHNOLOGY

764 - SRIPC

PROM

 PROM chips have several different applications, including **cell phones, video game consoles, RFID tags, medical devices, and other electronics**. They provide a simple means of programming electronic devices. Standard PROM can only be programmed once.



764 - SRIPC

PAL

Programmable Array Logic (PAL) is a type of semiconductor used to implement logic functions in digital circuits. PAL is a type of programmable logic device, which is a term for an integrated circuit that can be programmed in a laboratory to perform complex functions



COMPARE PROM, PAL, PLA

Ans :

P(ROM)	PAL	PLA
1. AND array is fixed, OR array is programmable.	1. OR array is fixed, AND is array programmable.	1. Both arrays are programmable.
2. Only SSOP type Boolean function or expression can be implement.	2. Any SOP type Boolean expression can be implement.	2. Any SOP type expression can be implement.
3. Cost is low.	3. Cost is low.	3. Costlier.
4. Simple to construct.	4. Simple to construct.	4. Complex to construct.

- Available choice for digital designer
- FPGA – A detailed look
- Interconnection Framework
 - FPGAs and CPLDs
- Field programmability and programming technologies
 - SRAM, Anti-fuse, EPROM and EEPROM

Designer's Choice

- Digital designer has various options
 - SSI (small scale integrated circuits) or MSI (medium scale integrated circuits) components
 - Difficulties arise as design size increases
 - Interconnections grow with complexity resulting in a prolonged testing phase
 - Simple programmable logic devices
 - PALs (programmable array logic)
 - PLAs (programmable logic array)
 - Architecture not scalable; Power consumption and delays play an important role in extending the architecture to complex designs
 - Implementation of larger designs leads to same difficulty as that of discrete components

Designer's Choice

- Quest for high capacity; Two choices available
 - MPGA (Masked Programmable Logic Devices)
 - Customized during fabrication
 - Low volume expensive
 - Prolonged time-to-market and high financial risk
 - FPGA (Field Programmable Logic Devices)
 - Customized by end user
 - Implements multi-level logic function
 - Fast time to market and low risk

FPGA – A Quick Look

- Two dimensional array of customizable logic block placed in an interconnect array
- Like PLDs programmable at users site
- Like MPGAs implements thousands of gates of logic in a single device
 - Employs logic and interconnect structure capable of implementing multi-level logic
 - Scalable in proportion with logic removing many of the size limitations of PLD derived two level architecture
- FPGAs offer the benefit of both MPGAs and PLDs!


FPGA – A Detailed Look

- Based on the principle of functional completeness
- FPGA: Functionally complete elements (Logic Blocks) placed in an interconnect framework
- Interconnection framework comprises of wire segments and switches; Provide a means to interconnect logic blocks
- Circuits are partitioned to logic block size, mapped and routed


A Fictitious FPGA Architecture

(With Multiplexer As Functionally Complete Cell)


- Basic building block

 


(A) Mux with 3 select inputs

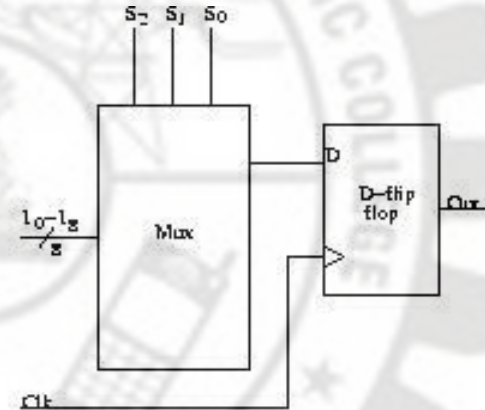

(B) Mux with output driving D-flip flop

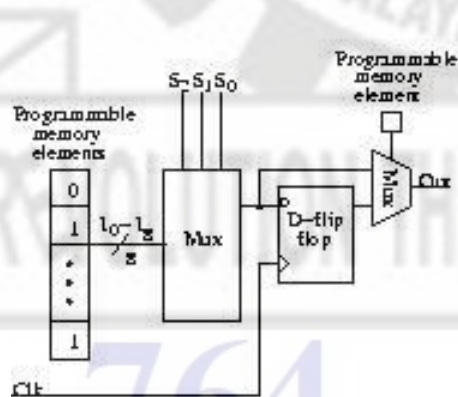

 (C) Selection of combinational or sequential output




(D) Shorthand image of basic building block

Interconnection Framework

- Granularity and interconnection structure has caused a split in the industry

FPGA

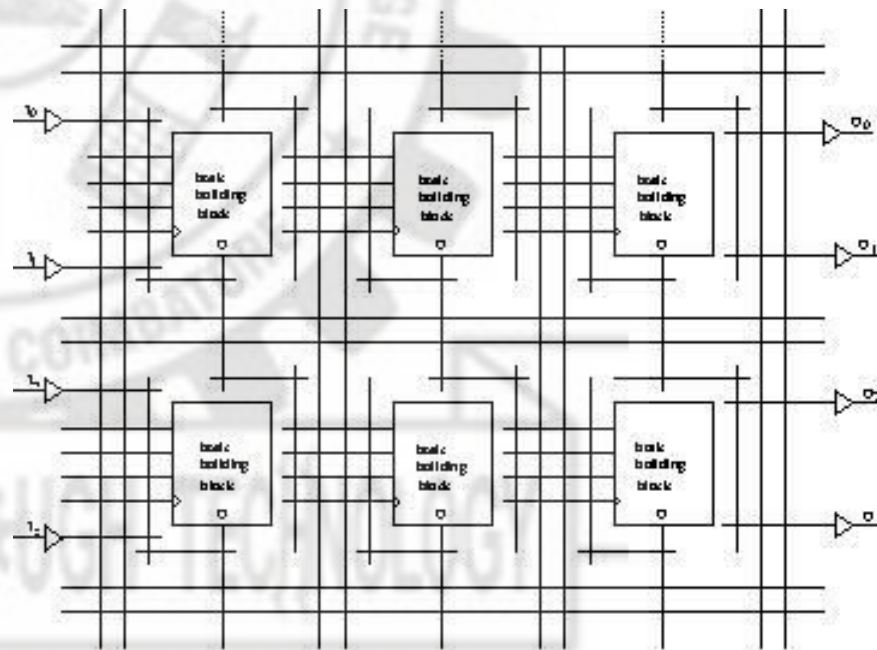- Fine grained
- Variable length interconnect segments
- Timing in general is not predictable; Timing extracted after placement and route




* Closed frame as a response to the neighboring logic blocks which are not shown.

Interconnection Framework

- CPLD

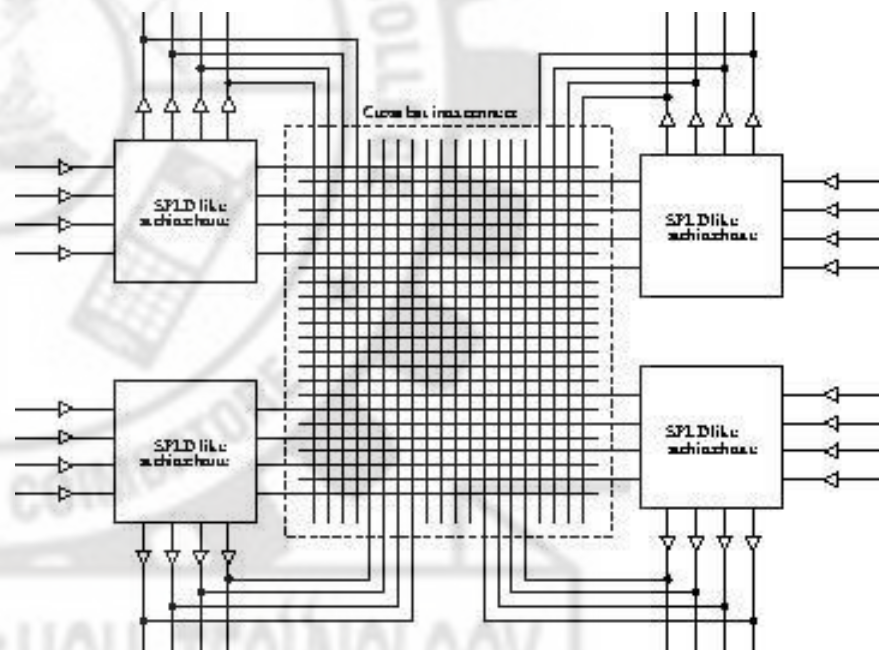- Coarse grained (SPLD like blocks)
- Programmable crossbar interconnect structure
- Interconnect structure uses continuous metal lines
- The switch matrix may or may not be fully populated
- Timing predictable if fully populated
- Architecture does not scale well



Field Programmability


- Field programmability is achieved through switches (Transistors controlled by memory elements or fuses)
- Switches control the following aspects
 - Intercornection among wire segments
 - Configuration of logic blocks
- Distributed memory elements controlling the switches and configuration of logic blocks are together called “Configuration Memory”

Technology of Programmable Elements


- Vary from vendor to vendor. All share the common property: Configurable in one of the two positions – ‘ON’ or ‘OFF’
- Can be classified into three categories:
 - SRAM based
 - Fuse based
 - EPROM/EEPROM/Flash based
- Desired properties:
 - Minimum area consumption
 - Low on resistance; High off resistance
 - Low parasitic capacitance to the attached wire
 - Reliability in volume production

SRAM Programming Technology

 - Employs SRAM (Static Random Access Memory) cells to control pass transistors and/or transmission gates
- SRAM cells control the configuration of logic block as well
- Volatile
 - Needs an external storage
 - Needs a power-on configuration mechanism
 - In-circuit re-programmable
- Lesser configuration time
- Occupies relatively larger area




(A) pass transistor

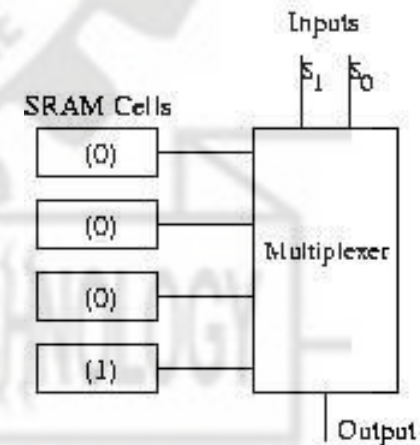

(B) Multiplexer

Anti-fuse Programming Technology

 


- Though implementation differ, all anti-fuse programming elements share common property
 - Uses materials which normally resides in high impedance state
 - But can be fused irreversibly into low impedance state by applying high voltage

Anti-fuse Programming Technology

- Very low ON Resistance (Faster implementation of circuits)
- Limited size of anti-fuse elements; Interconnects occupy relatively lesser area
 - Offset : Larger transistors needed for programming
- One Time Programmable
 - Cannot be re-programmed
 - (Design changes are not possible)
 - Retain configuration after power off

 
EPROM, EEPROM or Flash Based Programming Technology



- EPROM Programming Technology

- Two gates: Floating and Select
- Normal mode:
 - No charge on floating gate
 - Transistor behaves as normal n-channel transistor
- Floating gate charged by applying high voltage
 - Threshold of transistor (as seen by gate) increases
 - Transistor turned off permanently
- Re-programmable by exposing to UV radiation

EPRM Programming Technology

 

- Used as pull-down devices
- Consumes static power

Select gate Floating gate


EPROM Programming Technology

- No external storage mechanism
- Re-programmable (Not all!)
- Not in-system re-programmable
- Re-programming is a time consuming task

EEPROM Programming Technology

- Two gates: Floating and Select
- Functionally equivalent to EPROM; Construction and structure differ
- Electrically Erasable: Re-programmable by applying high voltage
(No UV radiation expose!)
- When un-programmed, the threshold (as seen by select gate) is negative!

EEPROM Programming Technology

 



764 - SRIPC

EEPROM Programming Technology

- Re-programmable, In general, in-system re-programmable
- Re-programming consumes lesser time compared to EPROM technology
- Multiple voltage sources may be required
- Area occupied is twice that of EPROM!

An Example

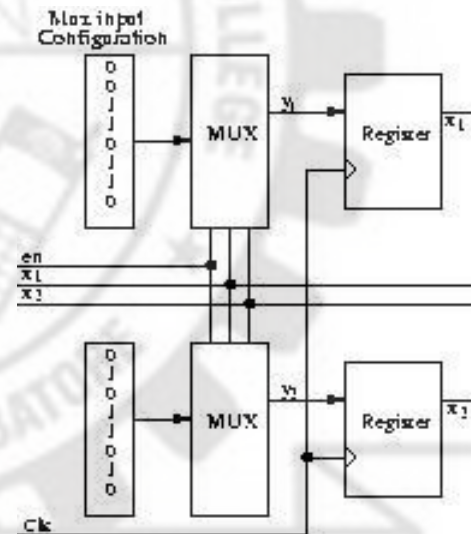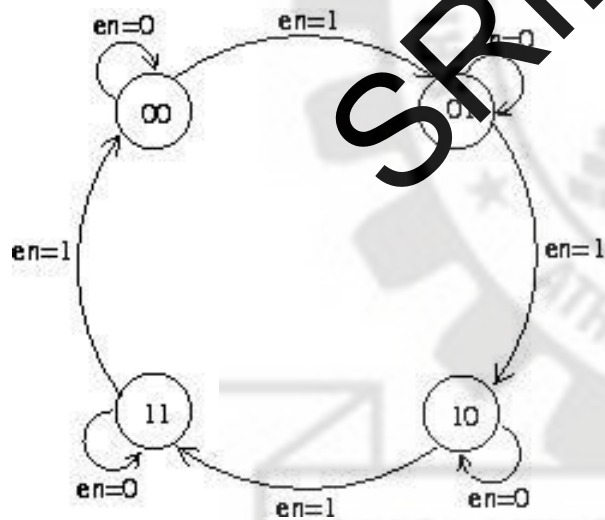
- Modulo-4 counter: Specification
- Modulo-4 counter: Logic Implementation




en	PS	Next State	Y1	Y2
	X1	X2		
0	0	0	0	0
0	0	1	0	J
0	1	0	J	0
0	1	1	J	J
1	0	0	0	J
1	0	1	J	0
1	1	0	J	J
1	1	1	0	0

* PS - Present State

FPGA Implementation of Modulo-4 Counter

 

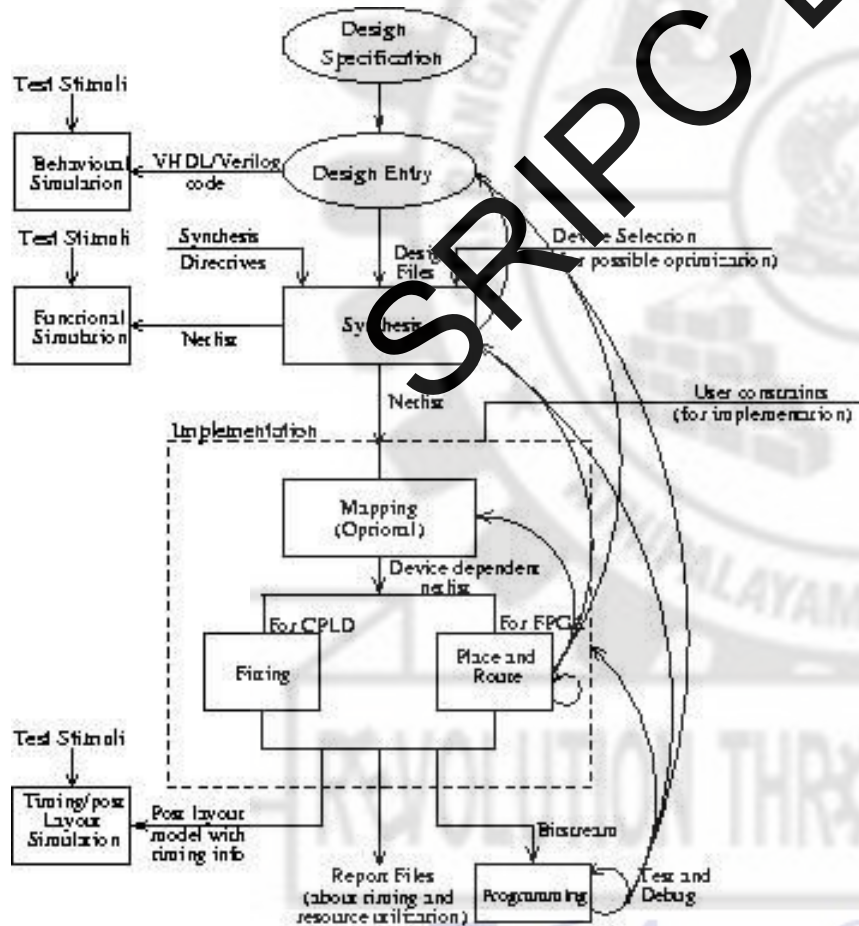Design Steps Involved in Designing With FPGAs




- Understand and define design requirements
- Design description
- Behavioural simulation (Source code interpretation)
- Synthesis
- Functional or Gate level simulation
- Implementation
 - Fitting
 - Place and Route
- Timing or Post layout simulation
- Programming, Test and Debug

Commercially Available Devices

- Architecture differs from vendor to vendor
- Characterized by
 - Structure and content of logic block
 - Structure and content of routing resources
- To examine, look at some of available devices
 - FPGA: Xilinx (XC4000)
 - CPLD: Altera (MAX 5K)

ALTERA CPLDS

➤ Altera generic architecture

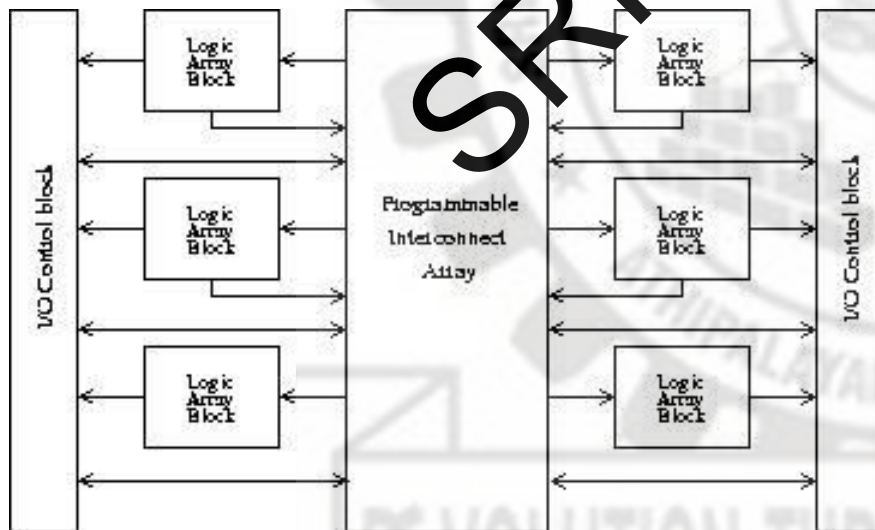

- Hierarchical PLD structure
 - First level: LABs (Functional blocks); LAB is similar to SPLDs
 - Second Level: Interconnections among LABs
- LAB consists of
 - Product term array
 - Product term distribution
 - Macro-cells
 - Expander product terms
- Interconnection region: PIA
- EPROM/EEPROM based
- Example: MAX5K, MAX7K

SRAM FPGA -- EEPROM FPGA

- An FPGA is similar to several other types of devices which have been around for quite a while, the difference being that an FPGA is simply much more expandable and versatile. The devices which FPGAs get compared to most often are CPLDs (Complex Programmable Logic Devices), which are similar in function but typically have way less logic gates inside them; Customizable CPU design is much more feasible with an FPGA. Once upon a time, CPLDs also had the distinct advantage of retaining their configuration even

SRAM FPGA -- EEPROM FPGA

- when turned off; When FPGAs first came out, they used simple SRAM to hold their configuration, which of course would be lost when the device lost power. Back then, the FPGA had to be programmed from scratch every time it was turned on, usually from a separate serial ROM chip. But today, FPGAs come in Flash, EPROM, and EEPROM variants, which will retain configuration, and which can also be re-programmed. (Fuse and anti-fuse FPGAs also exist, which act like PROMs in that they are one-time programmable, and cannot be reprogrammed)

SRAM FPGA -- EEPROM FPGA

- afterward.) Despite this, however, most FPGAs still use SRAM for reasons of simplicity (when you need to reprogram it, it's easier to re-encode a small ROM chip than to reprogram a large FPGA chip), so count on having to use a separate boot ROM for the FPGA.
- Use of an FPGA is broadly divided into two main stages: The first is "configuration mode", the mode in which the FPGA is when you first power it up. Configuration mode is, as you may have guessed, where you configure the FPGA; That is,

SRAM FPGA -- EEPROM FPGA

- this is when you load your code into it, dictating how the pins behave. Once configuration is complete, the FPGA goes into "user mode", its main mode of operation, where the programmed circuit actually starts functioning.

Product – FPGA vs ASIC


Comparison:

- **FPGA benefits vs ASICs:**
 - Design time: 9 month design cycle vs 2-3 years
 - Cost: No \$3-5 M upfront (NRE) design cost.
No \$100-500K mask-set cost
 - Volume: High initial ASIC cost recovered only in very high volume products
- **Due to Moore's law, many ASIC market requirements now met by FPGAs**
 - Eg. Virtex II Pro has 4 processors, 10 Mb memory, IO

Resulting Market Shift:


- **Dramatic decline in number of ASIC design starts:**
 - 11,000 in '97
 - 1,500 in '02
- **FPGAs as a % of Logic market:**
 - Increase from 10 to 22% in past 3-4 years
- **FPGAs (or programmable logic) is the fastest growing segment of the semiconductor industry!!**

FPGA/ASIC Crossover Changes

 

Taxonomy of FPGAs

SRIPC ECE

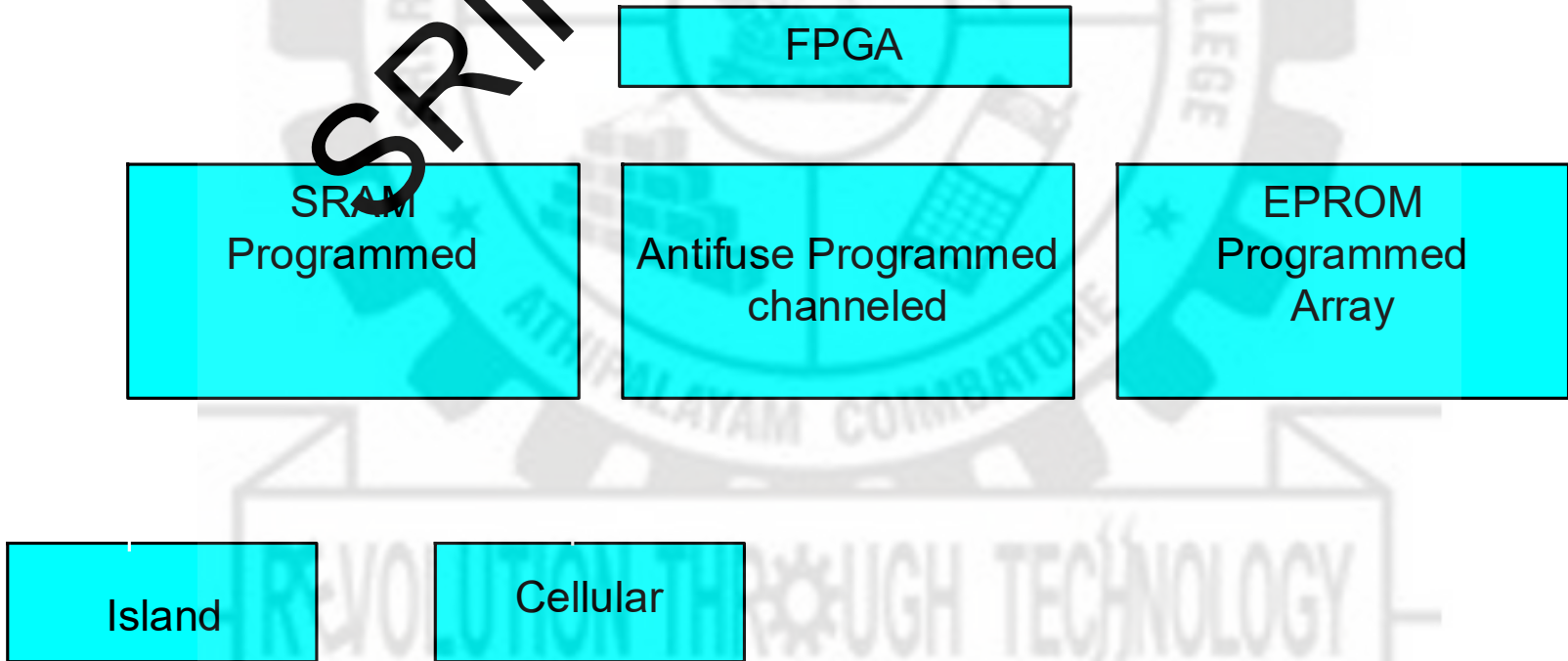

ASICs

- An ASIC (application-specific integrated circuit) is a **microchip** designed for a special application, such as a particular kind of transmission protocol or a hand-held computer. You might contrast it with general integrated circuits, such as the microprocessor and the random access memory chips in your PC. ASICs are used in a wide-range of applications, including auto emission control, environmental monitoring, and personal digital assistants (**PDA**s).