

SUBJECT- ELECTRICAL CIRCUIT THEORY

SUBJECT CODE-4030320

CONTENT

1. NOTES OF LESSON INDEX PAGE
2. NOTES OF LESSON (VIDEO LINK, PPT LINK ATTACHED IN THE INDEX PAGE)

PREPARED BY
N SRIRAM,
LECTURER/EEE.

REVOLUTION THROUGH TECHNOLOGY

764 - SRIPC



NOTES OF LESSON – INDEX PAGE

YEAR	SECOND YEAR	SEMESTER	IV SEMESTER
CT/SUBJECT CODE	ELECTRICAL CIRCUIT THEORY 4030320	SCHEME	N-SCHEME

UNIT-I- DC CIRCUITS

TOPIC	REFER TEXT BOOK NAME	VIDEO PRESENTATION	PPT	ANY OTHER
Basic Concepts of Current,	"Circuits and Networks Analysis and Synthesis" AUTHORS A Sudhakar Shyammohan S Palli PUBLISHER Tata McGraw Hill Education Private "Electric Circuits" AUTHORS Mahamood Nahvi Joseph A Edminister PUBLISHER Schaum Publishing Company, Newyork	https://www.youtube.com/watch?v=W6WAfcYKrdA https://www.youtube.com/watch?v=HsLLq6Rm5tU https://www.youtube.com/watch?v=u3cfW5RmKuw https://www.youtube.com/watch?v=u3cfW5RmKuw https://www.youtube.com/watch?v=IP2R52diLqg https://www.youtube.com/watch?v=Q79ztk0o5Jk https://www.youtube.com/watch?v=yNa4oray8_8	NIL	E-BOOK
EMF,				
Potential Difference,				
Resistance and Resistivity				
Ohm's Law –				
Work, Power, Energy				
Resistance in Series, Parallel and Series				
Parallel Circuits				
Kirchhoff's Laws				
Concept of Capacitance				
Capacitors in Series and in Parallel				
Problems in the above Topics.				


UNIT-II- CIRCUIT THEOREMS

TOPIC	REFER TEXT BOOK NAME	VIDEO PRESENTATION	PPT	ANY OTHER
Definitions of Node	"Circuits and Networks Analysis and Synthesis" AUTHORS A Sudhakar Shyammohan S Palli PUBLISHER Tata McGraw Hill Education Private "Electric Circuits" AUTHORS Mahamood Nahvi Joseph A Edminister PUBLISHER Schaum Publishing Company, Newyork	https://www.youtube.com/watch?v=JpNQ-9_VEKA	NIL	E-BOOK
Branch and Network				
Mesh Equations		https://www.youtube.com/watch?v=S0GsrzjVkd4		
Nodal Equations				
Star / Delta Transformations		https://www.youtube.com/watch?v=8udwPc5pCoA		
Superposition Theorem				
Thevenin's Theorem		https://www.youtube.com/watch?v=DdLA8rntWEY		
Norton's Theorem				
Maximum Power Transfer Theorem		https://www.youtube.com/watch?v=RbII8o49Hys		
Problems in DC Circuits only				

UNIT-III- SINGLE PHASE CIRCUITS

TOPIC	REFER TEXT BOOK NAME	VIDEO PRESENTATION	PPT	ANY OTHER
Definitions of Sinusoidal Voltage and Current Instantaneous, Peak, Average and Effective Values	“Circuits and Networks Analysis and Synthesis” AUTHORS A Sudhakar Shyammohan S Palli PUBLISHER Tata McGraw Hill Education Private	NIL	PPT	E-BOOK
Form Factor and Peak Factor (Derivation for Sine Wave)				
Pure Resistive, Inductive and Capacitive Circuits RL, RC, RLC Series Circuits – Impedance – Phase Angle				
Use of „J” Notations– Rectangular and Polar Coordinates - Phasor Diagram				
Power and Power Factor Power Triangle				
Apparent Power, Active and Reactive Power	“Electric Circuits” AUTHORS Mahamood Nahvi Joseph A Edminister PUBLISHER Schaum Publishing Company, Newyork		PPT	
Parallel Circuits (Two Branches Only)				
Conductance, Susceptance and Admittance				
Problems in all above topics.				
Concept of Series Resonance				
Parallel Resonance (R, L & C)				
Applications (No Problems)				

UNIT-IV- THREE PHASE AC CIRCUITS

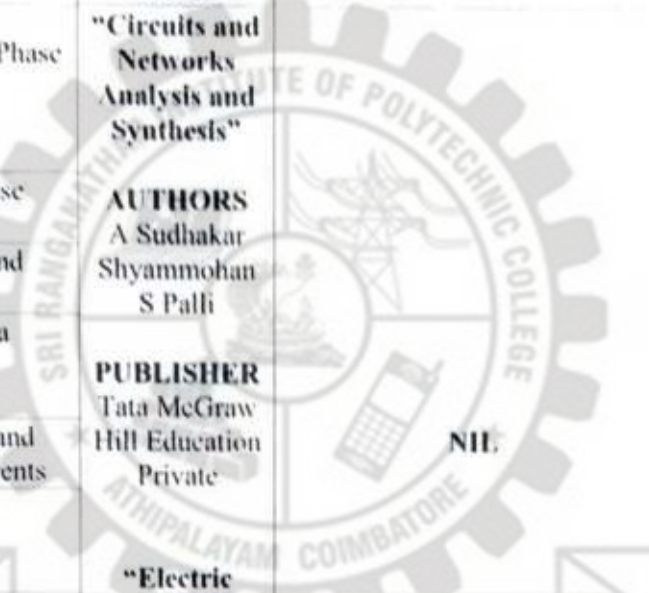TOPIC	REFER TEXT BOOK NAME	VIDEO PRESENTATION	PPT	ANY OTHER
Three Phase AC Systems-Phase Sequence	"Circuits and Networks Analysis and Synthesis"			
Necessity of Three Phase System	AUTHORS A Sudhakar Shyammohan S Palli			
Concept of Balanced and Unbalanced Load				
Balanced Star & Delta Connected Loads				
Relation between Line and Phase Voltages and Currents Phasor Diagram Three Phase Power	PUBLISHER Tata McGraw Hill Education Private	* NIL	PPT	E-BOOK
Power Factor	"Electric Circuits"			
Three Phase Power and Power Factor Measurement by Single Wattmeter and Two Wattmeter Methods	AUTHORS Mahamood Nahvi Joseph A Edminister	* NIL		
Problems in all Topics	PUBLISHER Schaum Publishing Company, Newyork			

UNIT-V- STORAGE BATTERIES

TOPIC	REFER TEXT BOOK NAME	VIDEO PRESENTATION	PPT	ANY OTHER
Classification of cells	<p>"Circuits and Networks Analysis and Synthesis"</p> <p>AUTHORS A Sudhakar Shyamamohan S Palli</p> <p>PUBLISHER Tata McGraw Hill Education Private</p> <p>"Electric Circuits"</p> <p>AUTHORS Mahamood Nahvi Joseph A Edminister</p> <p>PUBLISHER Schaum Publishing Company, Newyork</p>	https://www.youtube.com/watch?v=Q0VSVy-IIM	NIL	<p>Ohp Lead Acid BATTERY</p> <p>E-BOOK NICKEL Iron BATTERY</p>
Construction, Chemical action and physical changes during charging and discharging of Lead Acid, Nickel Iron and Nickel Cadmium Cells		https://www.youtube.com/watch?v=HhxtfULIO7c		
Advantages and Disadvantages of Nickel Ion and Nickel Cadmium Cells over Lead Acid Cell		https://www.youtube.com/watch?v=w7gmrcjRABY		
indication of fully charged and discharged battery		https://www.youtube.com/watch?v=kz9fErCL6Bk		
defects and their remedies		https://www.youtube.com/watch?v=YFd0kb9Nwt0		
capacity				
AH efficiency and WH efficiency (no problems)		https://www.youtube.com/watch?v=B9X1buyq9As		
methods of charging				
care and maintenance		https://www.youtube.com/watch?v=Ie3Vmf1Geyk		
applications – maintenance free batteries				
Lithium Cells, Lithium -Ion Cells and Mercury Cells	https://www.youtube.com/watch?v=Sh7DPjNiu9U			
Concept of Recharged Cell	https://www.youtube.com/watch?v=3KX_KuS6FPI			

Law of Resistance

The resistance of a conductor (R)

1. Is directly proportional to its length (l)
2. Is inversely proportional to its area of cross section (A)
3. Depends upon the nature of material.
4. Depends on its temperature.

I conductor or resistance (R) என்பது

1. Length (l) க்கு நேர விகிதத்தில் இருக்கும்.
2. Area of cross section (A) க்கு நேர் விகிதத்தில் இருக்கும்.
3. Material or nature (குணம்) ன்வு மூலக்கூறு இருக்கும்.
4. Temperature ன்வு மூலக்கூறு இருக்கும்.

$$R \propto l$$

$$R \propto \frac{1}{a}$$

$$R \propto \frac{l}{a}$$

$$R = \frac{l}{a}$$

$$R = \rho \frac{l}{a}$$

where ρ - (rho) constant
 l - length of conductor
 a - area of cross section

Specific resistance (or) resistivity

1. It is defined as the resistance between the opposite face of a cube material.
 The unit is ohm-m.

ஒரு மீட்டர் கியூபு மீட்டர் மீட்டர் - opposite இடங்களை
 Resistance இது அளக்கிறது.

$$R = \rho \frac{l}{a}$$

REVOLUTION THROUGH TECHNOLOGY

Power

764 - SRIPC

$$P = UI \text{ watts}$$

$$P = I^2 R \text{ watts}$$

$$P = \frac{V^2}{R} \text{ watts}$$

Energy Sources

1. Ideal Voltage source
2. Ideal current source

1. Ideal Voltage source




Where

$V_s \rightarrow$ Voltage source

$I_s \rightarrow$ current source

$R \rightarrow$ Resistance

2. Ideal current source

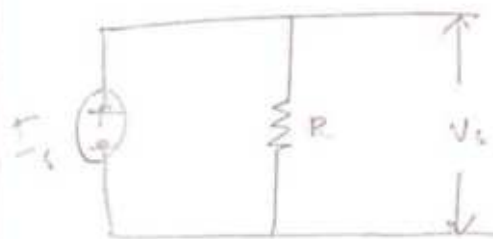

V_s - Voltage source

I_s - current source

R - Resistance

Q) If an electric bulb has a Voltage of 230 V with current of 5 Amp. The resistance of bulb is 18Ω . Draw the Ideal Voltage source and Ideal current source.

Given,

$$V = 230 \text{ Volts}$$

$$I = 5 \text{ A}$$


$$R = 18 \Omega$$

To find,


1. Ideal Voltage source
2. Ideal current source

Solution

1. Ideal voltage source

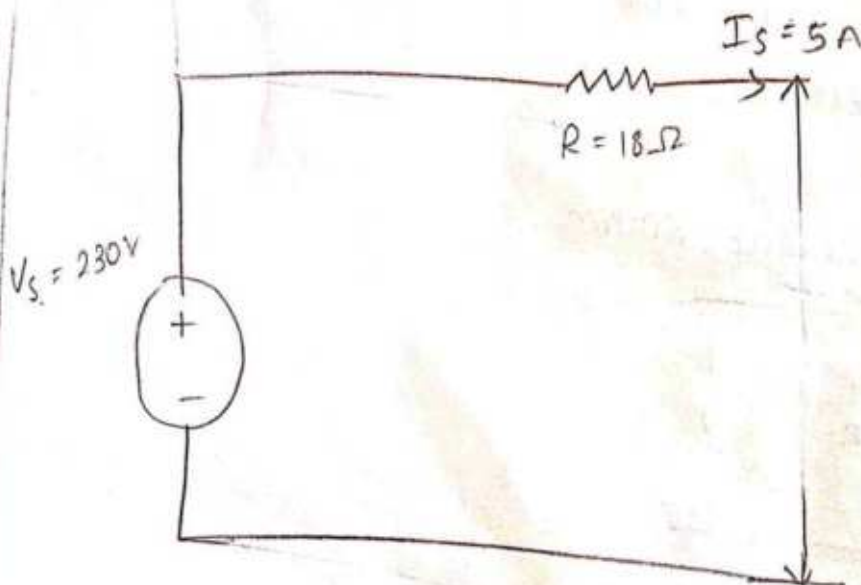

2. Ideal current source

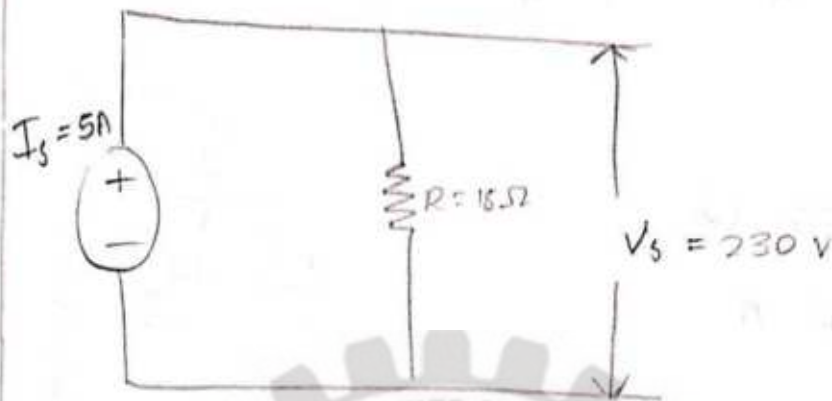

1. Calculate the voltage of a circuit. If the value of current is $10A$ and resistance is 25Ω

Given data

(Current) $I = 10A$

(Resistance) $R = 25\Omega$

(Voltage) $V = ?$

To find the voltage

$$V = IR$$

$$V = 10 \times 25$$

$$V = 250$$


$$V = 250V$$

- 2) Calculate the voltage of a circuit if the value of current is 40 A and $R = 250\ \Omega$

Given data

(Resistance) $R = 250\ \Omega$

(Current) $I = 40\text{ A}$

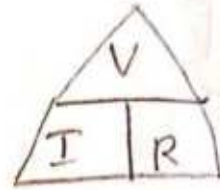

To find Voltage $V = ?$

Solution

$$V = IR$$

$$V = 40 \times 250$$

$$V = 10,000\text{ V}$$

3. Calculate the resistance of a circuit if value of current is 10 A and voltage is 230 V

Given data

$$\text{Current } (I) = 10\text{ A}$$

$$\text{Voltage } (V) = 230\text{ V}$$

To find

$$\text{Resistance } (R) = ?$$

Solution

$$R = \frac{V}{I}$$

$$R = \frac{230}{10}$$

$$R = 23 \Omega$$

4. Calculate the resistance of a circuit if the value of current is 15 A and voltage 210 V

Given data

$$\text{Current (I)} = 15 \text{ A}$$

$$\text{Voltage (V)} = 210 \text{ V}$$

To find

$$\text{Resistance (R)} = ?$$

Solution

$$R = \frac{V}{I}$$

$$R = \frac{210}{15}$$

$$R = 16 \Omega$$

5. Calculate the current of a circuit if the value of voltage is 230 V and Resistance is 10 Ω

Given data

$$\text{Voltage (V)} = 230 \text{ V}$$

$$\text{Resistance} = 10 \Omega$$

To find

$$I \text{ (current)} = ?$$

Solution

$$I = \frac{V}{R}$$

$$I = \frac{230}{10}$$

$$I = 23 \text{ A}$$

- 6) Calculate the current of a circuit if the value of voltage 245V and Resistance 8.6 Ω

Given data

$$\text{Voltage (V)} = 245 \text{ V}$$

$$\text{Resistance (R)} = 8.6 \Omega$$

To find

$$\text{Current (I)} = ?$$

Solution

$$I = \frac{V}{R}$$

$$I = \frac{245}{8.6}$$

$$I = 28.48 \text{ A}$$

② calculate the current and resistance of a 100W, 200V electric bulb.

Given data

$$\text{Power (P)} = 100 \text{ W}$$

$$\text{Voltage (V)} = 200 \text{ V}$$

To find

$$\text{Current (I)} = ?$$

$$\text{Resistance (R)} = ?$$

Solution

To find current :

$$P = VI$$

$$I = \frac{P}{V}$$

$$I = \frac{100}{200}$$

$$I = 0.50 \text{ A}$$

To find resistance :

$$R = \frac{V}{I}$$

$$R = \frac{200}{0.50}$$

$$R = 400 \Omega$$

8.

Calculate the current and resistance of a 150 W
230 V electric bulb.

Given data

$$\text{Voltage (V)} = 230 \text{ V}$$

$$\text{Power (P)} = 150 \text{ W}$$

To find

(I) current = ?

Resistance R = ?

Solution

To find current:

$$P = \frac{V^2}{R} \quad P = VI$$

$$I = \frac{P}{V}$$

$$I = \frac{150}{230}$$

$$I = 0.65 \text{ A}$$

To find resistance:

$$R = \frac{V}{I}$$

$$R = \frac{230}{0.65}$$

$$R = 353.84 \Omega$$

9.

Calculate the power rating of a heater coil used on 220V taking a supply of 5 Amps.

Given data

$$\text{Voltage} = 220 \text{ V}$$

$$\text{Current (I)} = 5 \text{ A}$$

To find

(P) Power = ?

Solution

$$P = VI$$

$$P = 220 \times 5$$

$$P = 1100 \text{ Watts}$$

10.

The resistance of an incandescent lamp when cold is 25Ω . Its hot value after operating voltage of 125V is 250Ω

i) Movement of switching ON

ii) Normal working current

Given data

$$\text{Resistance (R}_1\text{)} = 25 \Omega$$

$$\text{Resistance (R}_2\text{)} = 250 \Omega$$

$$\text{Voltage (V)} = 125 \text{ V}$$

To find

~~Resistance~~ Current (I) = ?

Solution

i) To find movement & switching on

$$I = \frac{V}{R_1}$$

$$I = \frac{125}{25}$$

$$I = 5 \text{ A}$$

ii) Normal working current

$$I = \frac{V}{R_2}$$

$$I = \frac{125}{250}$$

$$I = 0.50 \text{ A}$$

conversion

06.08.22
Saturday

1. To convert km into m \Rightarrow Value $\times 10^3 \text{ m}$
2. To convert cm^2 into $\text{m}^2 \Rightarrow$ Value $\times 10^{-4} \text{ m}^2$

① find the resistance of copper wire of 0.75 km long, having cross sectional area of 0.01 cm^2 . Take $\rho = 1.72 \times 10^{-8}$

$$R = \frac{\rho l}{a}$$

Given data

$$\rho (\text{rho}) = 1.72 \times 10^{-8}$$

$$l (\text{length}) = 0.75 \text{ km}$$

$$a (\text{area}) = 0.01 \text{ cm}^2$$

To find

resistance (R) = ?

Solution

$$R = \frac{\rho l}{a}$$

$$\text{length } l = 0.75 \times 10^3 \text{ m}$$

$$\text{cross section } (a) = 0.01 \times 10^{-4} \text{ m}^2$$

$$(\text{Rho}) \rho = 1.72 \times 10^{-8}$$

$$R =$$

$$R = \frac{(1.72 \times 10^{-8}) \times (0.75 \times 10^3)}{(0.01 \times 10^{-4})}$$

$$R = \frac{(1.29 \times 10^{-5})}{(0.01 \times 10^{-4})}$$

$$R = 12.9 \Omega$$

- ② find the resistance of a copper wire of 0.95 km long, having cross section area of 0.04 cm². Take $\rho = 1.54 \times 10^{-6}$

Given data

$$\text{length } (l) = 0.95 \text{ km}$$

$$0.95 \times 10^3 \text{ m}$$

$$\text{area } (a) = 0.04 \text{ cm}^2$$

$$0.04 \times 10^{-4} \text{ m}^2$$

$$\rho = 1.54 \times 10^{-6}$$

To find

$$\text{Resistance } (R) = ?$$

Solution

$$R = \frac{\rho l}{a}$$

$$R = \frac{(1.54 \times 10^{-6}) \times (0.95 \times 10^3)}{(0.04 \times 10^{-4})}$$


$$(0.04 \times 10^{-4})$$

08.08.21
Monday ☺

Connections of resistance

1. Series connection
2. Parallel connection
3. Series - parallel connection

1. Series connection

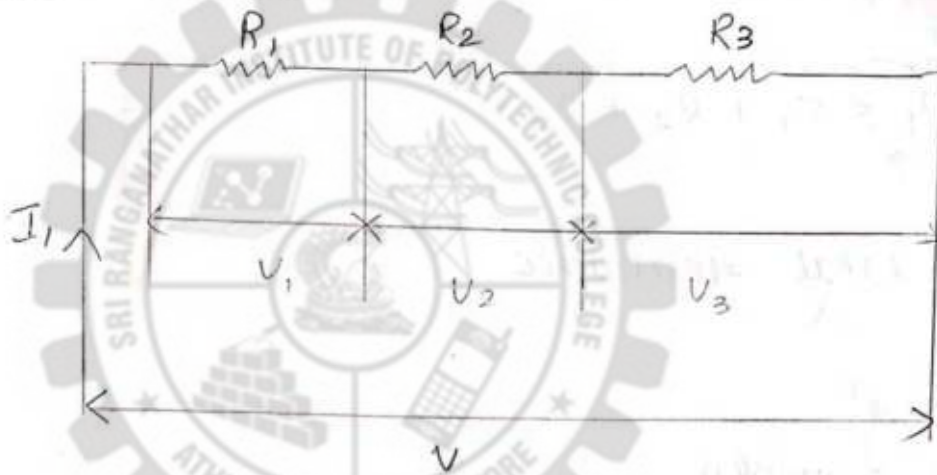

Where,

V = Voltage

I = Current

R_1, R_2, R_3 = Resistance

V_1 = Voltage drop across R_1

V_2 = Voltage drop across R_2

V_3 = Voltage drop across R_3

$$\therefore \text{Total Voltage } V = V_1 + V_2 + V_3 \rightarrow \textcircled{1}$$

We know that $V_1 = IR_1$, $V_2 = IR_2$, $V_3 = IR_3$

Substitute equ $\textcircled{2}$ in $\textcircled{1}$ we get

$$V = V_1 + V_2 + V_3 \longrightarrow \textcircled{1}$$

$$V = (IR_1) + (IR_2) + (IR_3)$$

$$V = I [R_1 + R_2 + R_3]$$

$$V/I = R_1 + R_2 + R_3$$


$$\frac{V}{I} = R$$

$$R = R_1 + R_2 + R_3 \quad \left[\text{since } R = \frac{V}{I} \right]$$

$$R_T = R_1 + R_2 + R_3$$

R_T = Total resistance

Parallel connection

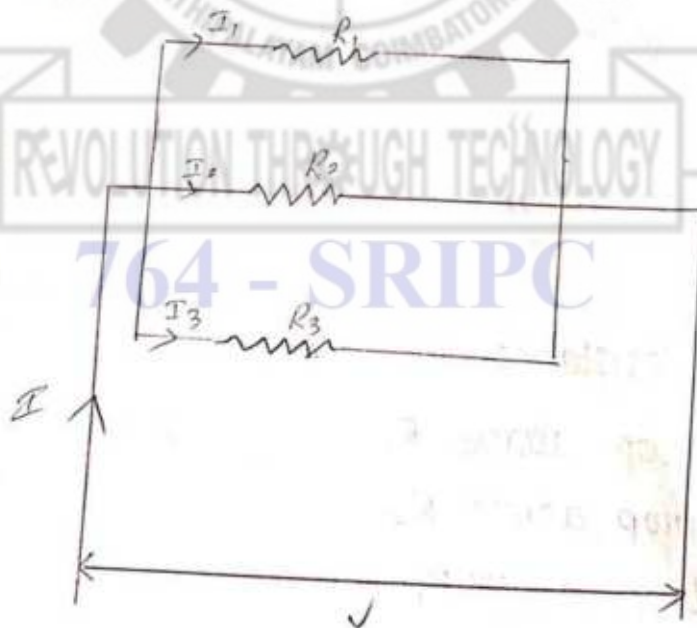

V - voltage

I - current

I_1 - current through resistance R_1

I_2 - current through resistance R_2

I_3 - current through resistance R_3

$$\therefore \text{Total current } I = I_1 + I_2 + I_3 \rightarrow (1)$$

$$\text{By Ohm's law } I = V/R$$

$$\text{So, } I_1 = V/R_1, I_2 = V/R_2, I_3 = V/R_3 \rightarrow (2)$$

Sub equ (2) in (1) we get

$$I = I_1 + I_2 + I_3 \rightarrow (1)$$

$$I = \left(\frac{V}{R_1} \right) + \left(\frac{V}{R_2} \right) + \left(\frac{V}{R_3} \right)$$

$$I = V \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right]$$

$$I/V = \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right]$$


$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\left[\begin{array}{l} \text{Since } R = V/I \\ \text{So } \frac{1}{R} = \frac{I}{V} \end{array} \right]$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$\frac{1}{R_T}$ = Total resistance

Series - parallel connection

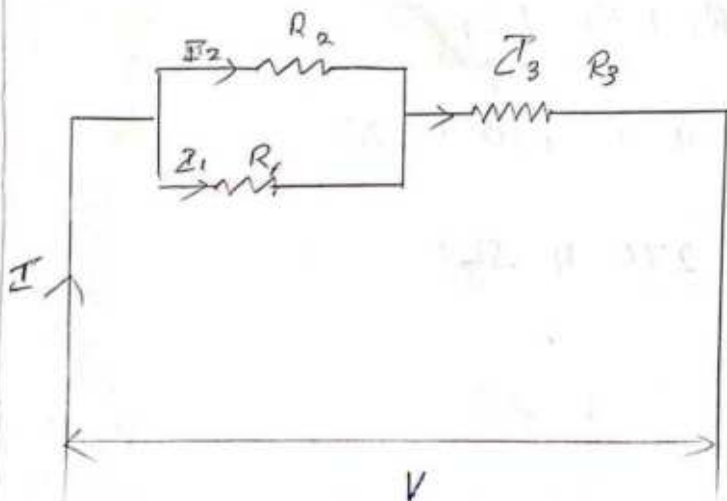

I - current

V - voltage

I_1 - current through R_1

I_2 - current through R_2

I_3 - current through R_3

$$\therefore \text{Total current } \mathcal{I} = I_1 + I_2 + I_3 \rightarrow \textcircled{1}$$

$$\text{By Ohm's law } \mathcal{I} = V/R$$

$$\text{So, } I_1 = V/R_1, I_2 = V/R_2, I_3 = V/R_3 \rightarrow \textcircled{2}$$

Sub equ (2) in (1) we get

$$\mathcal{I} = I_1 + I_2 + I_3 \rightarrow \textcircled{1}$$

$$\mathcal{I} = \left(\frac{V}{R_1} \right) + \left(\frac{V}{R_2} \right) + \left(\frac{V}{R_3} \right)$$

$$\mathcal{I} = V \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right]$$

$$\mathcal{I}/V = \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right]$$


$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\left[\begin{array}{l} \text{Since } R = V/I \\ \text{So } \frac{1}{R} = \mathcal{I}/V \end{array} \right]$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$\frac{1}{R_T}$ = Total resistance

Series - parallel connection

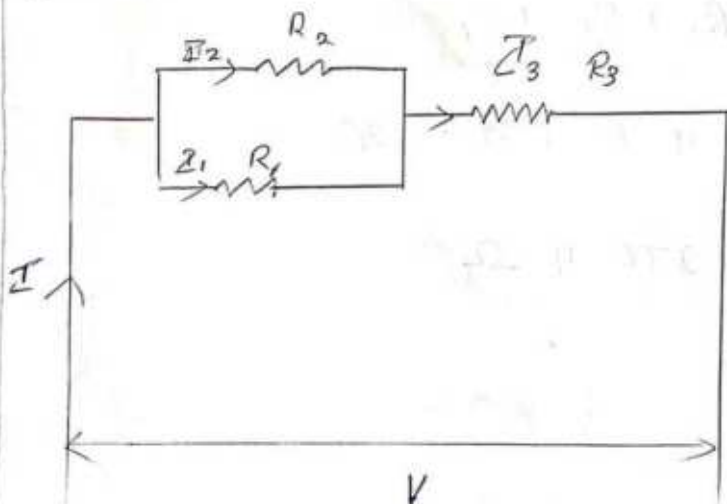

\mathcal{I} - current

V - voltage


I_1 - current through R_1

I_2 - current through R_2

I_3 - current through R_3

① A circuit is made of 0.4Ω wire, a 150Ω bulb and 120Ω Rheostat which are connected in series. Determine total resistance.

Series

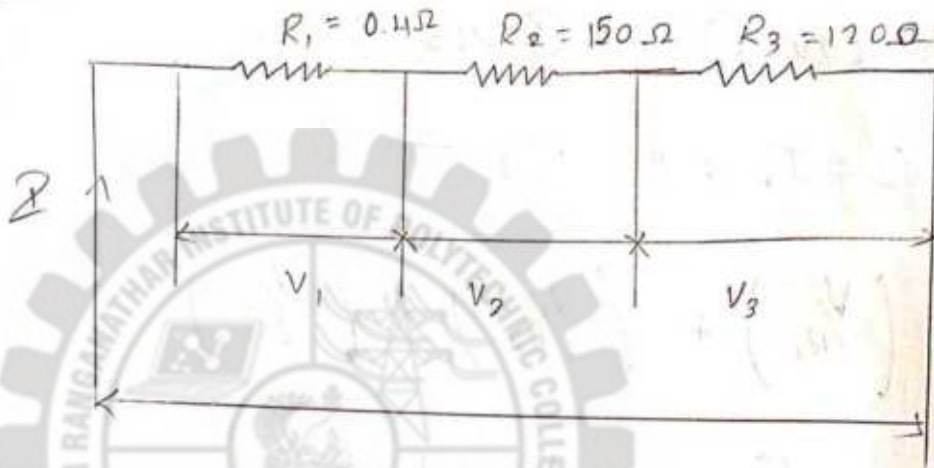

Given data

$$R_1 = 0.4 \Omega$$

$$R_2 = 150 \Omega$$

$$R_3 = 120 \Omega$$

To find

Total resistance = ?


Solution

$$R_T = R_1 + R_2 + R_3$$

$$R_T = 0.4 + 150 + 120$$

$$R_T = 270.4 \Omega$$

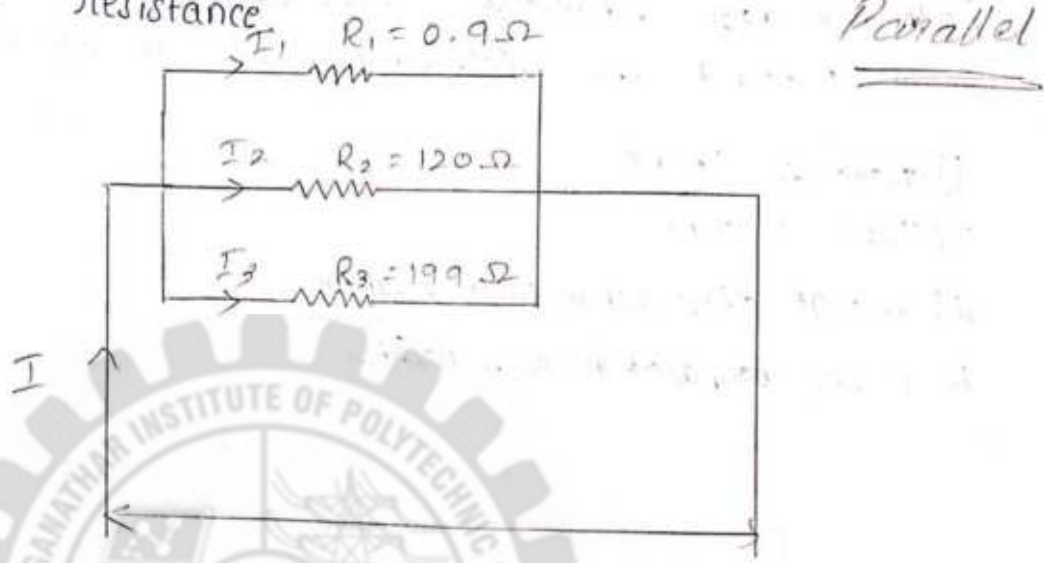② A circuit is made of 0.9Ω wire, a 120Ω bulb and 199Ω Rheostat which are connected in parallel connection. Determine the total resistance



Given data

$$R_1 = 0.9 \Omega$$

$$R_2 = 120 \Omega$$

$$R_3 = 199 \Omega$$

To find **74 - SRIPC**

Total resistance = ?

Soln.


$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_T} = \left[\frac{1}{0.9} \right] + \left[\frac{1}{120} \right] + \left[\frac{1}{199} \right]$$

$$\frac{1}{R_T} = 1.12 \Omega \quad R_T = \frac{1}{1.12} = 0.89 \Omega$$

1. A circuit is made of 1.9Ω wire, a 142Ω bulb and 99Ω Rheostat which are connected in series. Determine the following. with voltage 240 volts

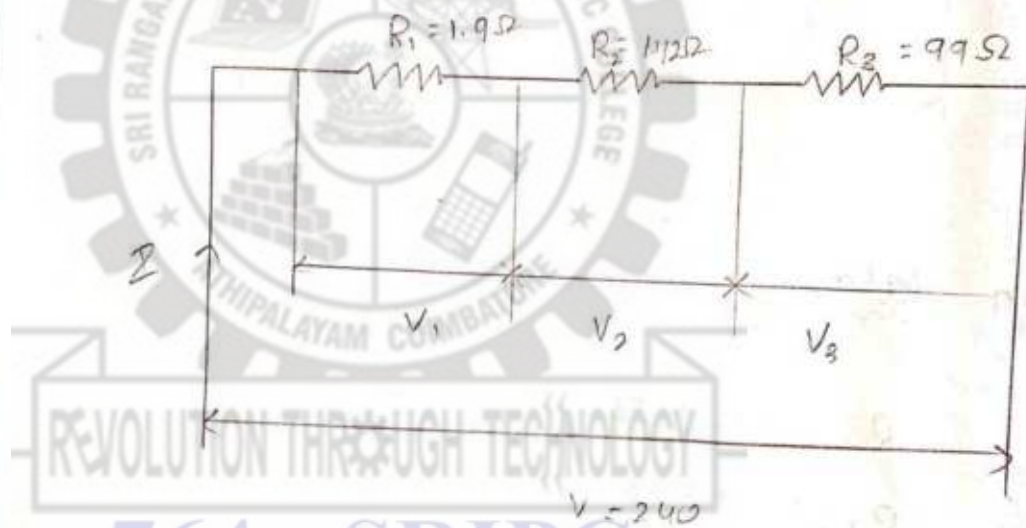- i) Total resistance
- ii) Total current
- iii) voltage drop across each resistor.
- iv) power dissipated in each resistor.



Given data.

$$\text{Resistance } (R_1) = 1.9 \Omega$$

$$\text{Resistance } (R_2) = 142 \Omega$$

$$\text{Resistance } (R_3) = 99 \Omega$$

$$\text{Voltage } (V) = 240$$

To find

$$\text{Total resistance} = ?$$

$$\text{Total current} = ?$$

$$\text{Voltage drop across each resistor} = ?$$

$$\text{Power dissipated in each other} = ?$$

Solution:

i) Total resistance

$$R_T = R_1 + R_2 + R_3$$

$$R_T = 1.9 + 142 + 99$$

$$R_T = 242.9 \Omega$$

ii) Total current

$$I = \frac{V}{R_T}$$

$$I = \frac{240}{242.9}$$

$$I = 0.98 \text{ amps}$$

iii) Voltage drop across each resistor

$$V_1 = I R_1$$

$$V_1 = 0.98 \times 1.9$$

$$V_1 = 1.86 \text{ volts}$$

$$V_2 = I R_2$$

$$V_2 = 0.98 \times 142$$

$$V_2 = 139.16$$

$$V_2 = 139.16 \text{ volts}$$

$$V_3 = 0.98 \times 99$$

$$V_3 = 97.02 \text{ volts}$$

iv) power dissipated in each resistor

$$P_1 = I^2 R_1$$

$$P_1 = 0.98^2 \times 1.9$$

$$P_1 = 1.82 \text{ watts}$$

$$P_2 = I^2 R_2$$

$$P_2 = 0.98^2 \times 142$$

$$P_2 = 136.6$$

$$P_2 = 136.37 \text{ watts}$$

$$P_3 = I^2 R_3$$


$$P_3 = 0.98 \times 99$$

$$P_3 = 95.07 \text{ watts}$$

② A circuit is made of 2.3Ω wire, a 136Ω bulb and 69Ω Rheostat which are connected in parallel. Determine the following with voltage $240V$

1. Total resistance
2. Total current
3. Voltage drop across each resistor
4. Power dissipated in each resistor.

Parallel

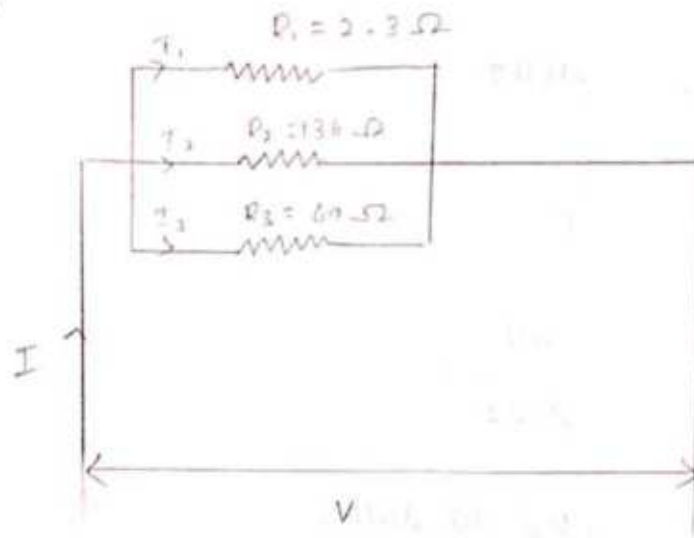

Given data

$$R_1 \text{ (Resistance)} = 2.3 \Omega$$

$$R_2 \text{ (Resistance)} = 136 \Omega$$

$$R_3 \text{ (Resistance)} = 69 \Omega$$

$$\text{Voltage (V)} = 240$$

To find

Total resistance = ?

Total current = ?

Voltage drop across each other ?

Power dissipated in each resistor = ?

10/6/22

1. Total resistance

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_T} = \left[\frac{1}{2.3} \right] + \left[\frac{1}{136} \right] + \left[\frac{1}{69} \right]$$

$$\frac{1}{R_T} = 0.45 \Omega$$

$$R_T = \frac{1}{0.45}$$

$$R_T = 2.22 \Omega$$

ii) Total current

$$I = \frac{V}{R_T}$$

$$I = \frac{240}{2.22}$$

$$I = 108.10 \text{ amps}$$

iii) Voltage drop across each resistor

$$V_1 = I R_1$$

$$V_1 = 108.10 \times 2.3$$

$$V_1 = 248.63 \text{ volts}$$

$$V_2 = I R_2$$

$$V_2 = 108.10 \times 136$$

$$V_2 = 1470.16 \text{ volts}$$

$$V_3 = I R_3$$

$$V_3 = 108.10 \times 69$$

$$V_3 = 7458.9 \text{ volts}$$

iv) Power dissipated in each resistor :

$$P_1 = I^2 R_1$$

$$P_1 = (108.10)^2 \times 2.3$$

$$P_1 = 26876.90 \text{ watts}$$

$$P_2 = I^2 R_2$$

$$P_2 = (108 \cdot 10)^2 \times 136$$

$$P_2 = 1589242.96 \text{ watts}$$

$$P_3 = I^2 R_3$$


$$P_3 = (108 \cdot 10)^2 \times 69$$

$$P_3 = 806307.09 \text{ watts}$$

11. 08. 2022
Thursday ☺

① A Resistance of R ohm is connected in series with a parallel circuit comprising of two resistance 12 ohms and 8 ohms respectively. The total power dissipated in the circuit is 70 watts. when the applied voltage is 20 v. calculate the value R ;

764 - SRIPC

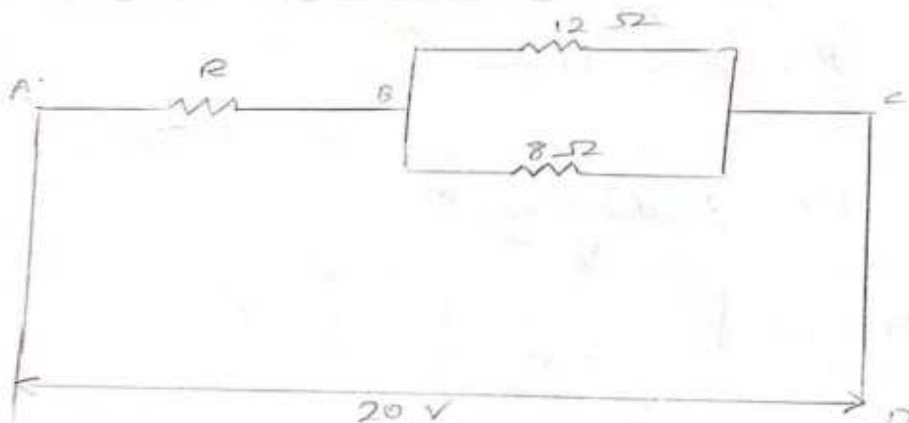

Given data..

$$\text{Resistance } R_1 = R$$

$$\text{Resistance } R_2 = 12 \Omega$$

$$\text{Resistance } R_3 = 8 \Omega$$

$$\text{Total power (P)} = 70 \text{ W}$$

$$\text{Voltage (V)} = 20 \text{ V}$$

To find

Unknown resistance $R = ?$

Solution

To find Unknown resistance

$$R_T = R_{AB} + R_{BC}$$

$$R_{AB} = R_T - R_{BC} \rightarrow \textcircled{1}$$

S-1

To find R_T ?


$$\text{Total resistance } R_T = \frac{V^2}{P}$$

$$R_T = \frac{20^2}{70}$$

$$R_T = 5.71 \Omega$$

S-2

To find R_{BC} ?

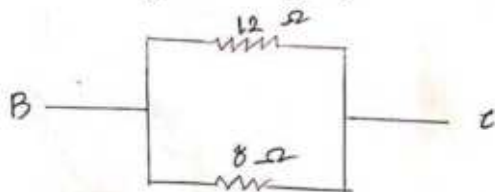

Resistance in parallel

$$\frac{1}{R_{BC}} = \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_{BC}} = \left(\frac{1}{10} \right) + \left(\frac{1}{8} \right)$$

$$\frac{1}{R_{BC}} = 0.20$$

$$R_{BC} = \frac{1}{0.20}$$

$$R_{BC} = 4.8 \Omega$$

Q-3

Sub R_T and R_{BC} value in equ (1), so we get


$$R_{AB} = R_T - R_{BC} \quad \text{--- (1)}$$

$$R_{AB} = 5.71 - 4.8$$

$$R_{AB} = 0.914 \Omega$$

unknown resistance $R_{AB} = 0.914 \Omega = R$

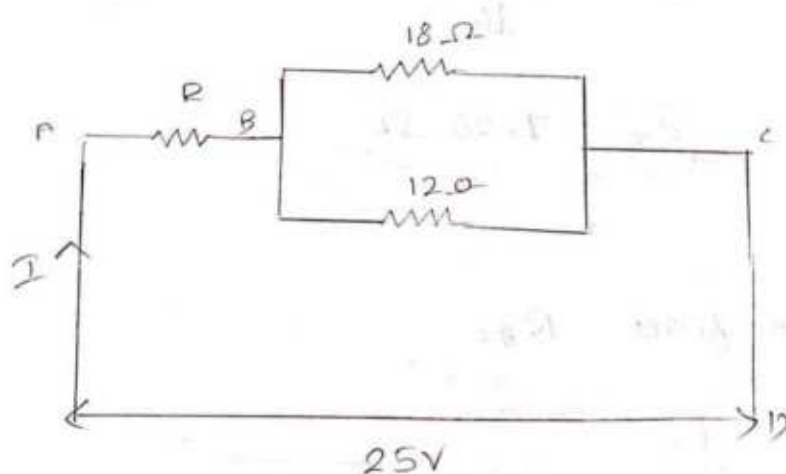A resistance of R ohm is connected in series with a parallel circuit comprising of two resistances 18 ohm and 12 ohm respectively. The total power dissipated in the circuit is 86 watts. when the applied voltage is 25V. Calculate the value of ' R '.



Given data

$$\text{Resistance } (R_1) = R$$

$$\text{Resistance } (R_2) = 18 \Omega$$

$$\text{Resistance } (R_3) = 12 \Omega$$

$$\text{Total power } (P) = 86 \text{ watts}$$

$$\text{voltage } (V) = 25 \text{ V}$$

To find ?

Unknown resistance $R = ?$

Solution

To find unknown resistance

$$R_T = R_{AB} + R_{BC}$$

$$R_{AB} = R_T - R_{BC} \rightarrow \textcircled{1}$$

Step 1 - SRIPC

To find R_T


$$\text{Total resistance } R_T = \frac{V^2}{P}$$

$$R_T = \frac{25^2}{86}$$

$$R_T = 7.26 \Omega$$

Step 2

To find R_{BC}

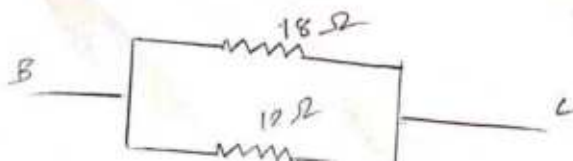

Total resistance in parallel

$$\frac{1}{R_{BC}} = \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_{BC}} = \left(\frac{1}{18}\right) + \left(\frac{1}{12}\right)$$

$$\frac{1}{R_{BC}} = 0.138$$

$$R_{BC} = \frac{1}{0.138}$$

$$R_{BC} = 7.24 \Omega$$

Step 3

Sub R_T and R_{BC} in eqn (1)

$$R_{AB} = R_T - R_{BC} \quad \text{--- (1)}$$

$$R_{AB} = 7.26 - 7.24$$

$$R_{AB} = 0.02 \Omega$$

Total resistance

$$\text{Unknown resistance } R_{AB} = 0.02 \Omega = R$$

Conditions for Kirchoff's law

for battery

நீளம் எடுக்கும் மின்சுற்றில் உண்மையில் battery ஓர் மிகுந்த உணர்வு positive terminal ல் இருந்து negative terminal லை செல்வதற்கு இருக்காது அதன் EMF லை Negative sign லில் குறிப்பிட்டு எழுதப்படும்.

1. In a circuit, the value of the battery goes from positive terminal to negative terminal means, that EMF should be mentioned in "negative sign."

2. If the battery goes from negative terminal to positive terminal means that EMF should be mentioned in positive sign for current.

for current

1. In a circuit the direction of current

and direction of current in resistance are in same direction means that voltage drop must be mentioned in negative sign.

2. If the both currents are in opposite direction means the voltage drop must be mentioned in positive sign.

Conditions for Kirchoff's law

for battery

நீளம் எடுக்கும் மின்சுற்றில் உண் battery ஓர் மிகுந்த உணர் positive terminal ல் இடத்து Negative terminal லை செல்வதற்கு இடத்து எந்த EMF லை Negative sign லை குறிக்க வேண்டும்

1. In a circuit, the value of the battery goes from positive terminal to negative terminal means, that EMF should be mentioned in "negative sign."

2. If the battery goes from negative terminal to positive terminal means that EMF should be mentioned in positive sign for current

for current


1. In a circuit the direction of current

and direction of current in resistance are in same direction means that voltage drop must be mentioned in negative sign.

2. If the both currents are in opposite direction means the voltage drop must be mentioned in positive sign.



Illustration of Kirchhoff's law

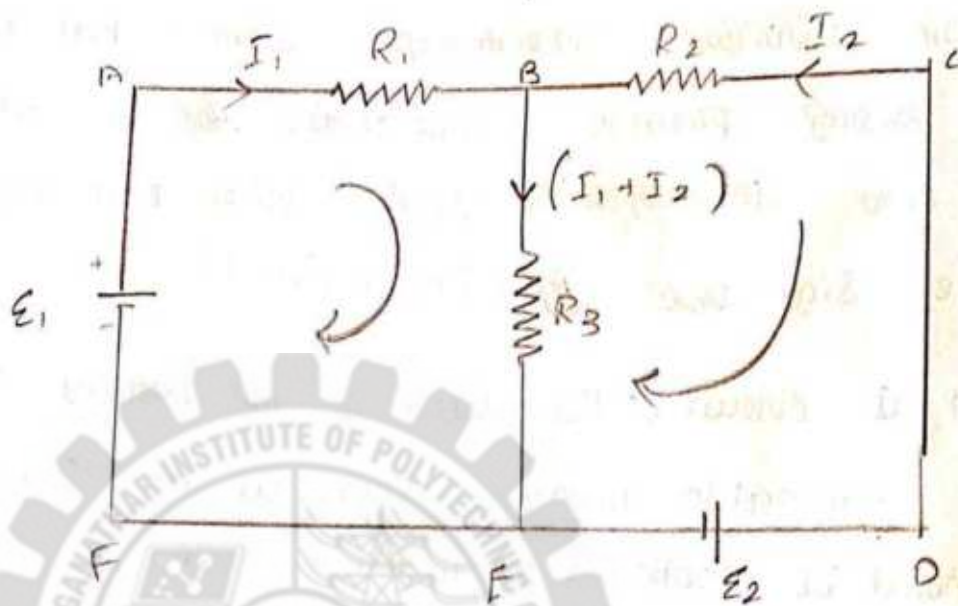

In closed loop ABCEA

$$-I_1 R_1 - (I_1 + I_2) R_3 + E_1 = 0$$

$$-I_1 R_1 - (I_1 + I_2) R_3 = -E_1$$

In closed loop BCDEF

$$I_2 R_2 - E_2 + (I_1 + I_2) R_3 = 0$$


$$I_2 R_2 + (I_1 + I_2) R_3 = E_2$$

In closed loop ABCDEFA

$$-I_1 R_1 + I_2 R_2 - E_2 + E_1 = 0$$

$$-I_1 R_1 + I_2 R_2 = E_2 - E_1$$

① find the current in 4Ω resistor

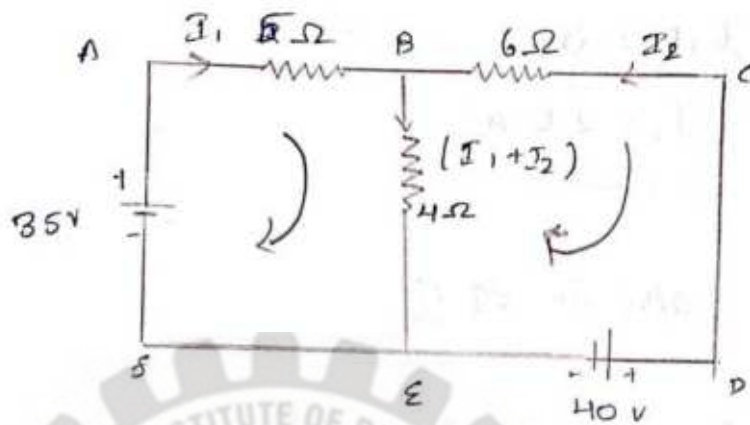

In closed loop ABFEFA

$$-5I_1 - 4(I_1 + I_2) + 35 = 0$$

$$-9I_1 - 4(I_1 + I_2) + 35 = 0$$

$$-9I_1 - 4I_2 = -35 \rightarrow \textcircled{1}$$

In closed loop ABCDEF

$$-5I_1 + 6I_2 - 40 + 35 = 0$$

$$-5I_1 + 6I_2 - 5 = 0 \rightarrow \textcircled{2}$$

Eq are

$$-9I_1 - 4I_2 = -35 \rightarrow \textcircled{1}$$

$$-5I_1 + 6I_2 = 5 \rightarrow \textcircled{2}$$

∴ find I_1 and I_2

$$\text{Multiply eq 1} \times 3 \Rightarrow -27I_1 + 12I_2 = -105$$

$$-10I_1 + 12I_2 = 10$$

$$\text{Multiply eq 2} \times 2$$

$$\underline{-37I_1 = -95}$$

$$+ I_1 = -95 / -37$$

$$I_1 = 2.6$$

$$I_1 = 2.6 \text{ A}$$

Sub I_1 Value in eq ①

$$-9I_1 - 4I_2 = -35 \rightarrow \text{①}$$

$$-9(2.6) - 4I_2 = -35$$

$$-23.4 - 4I_2 = -35$$

$$4I_2 = -35 + 23.4$$

$$-4I_2 = 11.6$$

764 - SRIPC

$$I_2 = \frac{-11.6}{-4}$$

$$I_2 = 2.9 \text{ A}$$


current through 4Ω resistance

$$I = I_1 + I_2$$

$$I = 2.6 + 2.9$$

$$I = 5.5 \text{ Amps}$$

find the current in 2Ω resistor

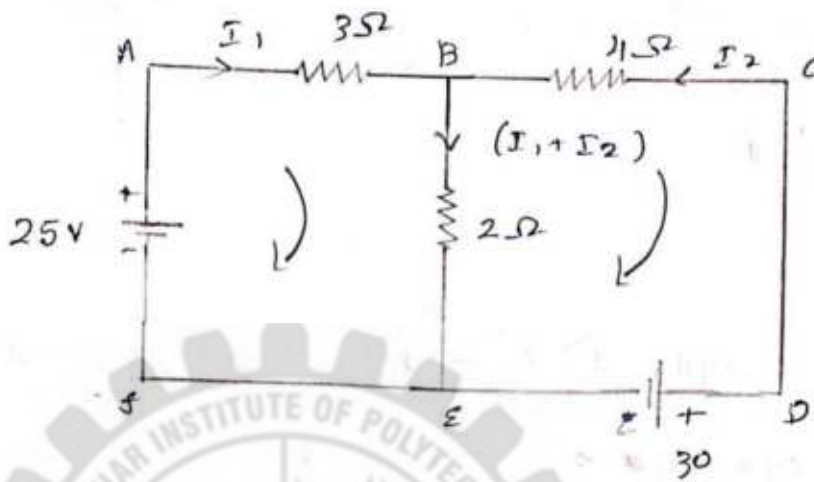

The closed loop ABCEFA

$$-3I_1 - 2(I_1 + I_2) + 25 = 0$$

~~$$\begin{aligned} -3I_1 - 2(I_1 + I_2) &= -25 \\ -5I_1 - 2I_2 &= -25 \end{aligned}$$~~

→ ①

~~The closed loop ABCDEF~~

763I - SRIPC

~~$$-3I_1 - 2I_1 - 2I_2 + 25 = 0$$~~

~~$$-5I_1 - 2I_2 = -25 \rightarrow \text{①}$$~~

$$-4(5+2)$$

$$-20 - 8$$

The closed loop ABCDEF

$$-3I_1 + 4I_2 - 30 + 25 = 0$$

$$-3I_1 + 4I_2 - 5 = 0$$

$$-3I_1 + 4I_2 = 5 \rightarrow \text{②}$$

Equations

$$1. -5I_1 - 2I_2 = -25 \rightarrow \textcircled{1}$$

$$2. -3I_1 + 4I_2 = 5 \rightarrow \textcircled{2}$$

To find

$$\text{equ } \textcircled{1} \times 2 \quad -10I_1 - 4I_2 = -50$$

$$\text{equ } \textcircled{2} \times 2 \quad -6I_1 + 8I_2 = 10$$

$$\text{equ } \textcircled{1} \times 2 \quad -10I_1 - 4I_2 = -50$$

$$\text{equ } \textcircled{2} \quad -3I_1 + 4I_2 = 5$$

$$-13I_1 = -45$$

$$764 - 3RIP \quad -13I_1 = -45$$

$$I_1 = \frac{-45}{-13}$$

$$I_1 = 3.46 \text{ A}$$

Sub I_1 in the 2nd equ

$$-3(3.46) + 4I_2 = 5$$

$$-10.38 + 4I_2 = 5$$

$$+4I_2 = 5 + 10 \cdot 38$$

$$+4I_2 = 15.38$$

$$I_2 = \frac{15.38}{4}$$

$$I_2 = 3.84 \text{ A}$$

Current through

$$I = I_1 + I_2$$

$$I = 3.4 + 3.8$$

$$I = 7.2 \text{ Amps}$$

REVOLUTION THROUGH TECHNOLOGY

764 - SRIPC

17.08.2022

Capacitors

1. any two conducting surface separated by an insulating medium exhibit the property of the capacitor.
2. A capacitor stores energy in the form of an electric field that is established by the opposite charges on the ^{two} electrodes.

capacitance

The ability of a capacitor to store electricity is known as its capacitance.

$$Q \propto V$$

(or)

$Q =$ charge


$V =$ Voltage

$C =$ capacitance

$$C = \frac{Q}{V}$$

The unit is "faraday" (F)

Capacitor in Series

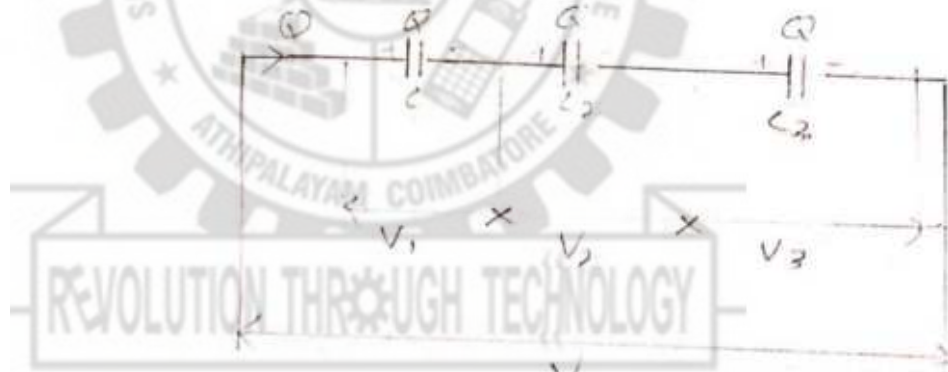

764 - SRIPC

Total Voltage $V = V_1 + V_2 + V_3$

[We know that $C = \frac{Q}{V}$, so $V = \frac{Q}{C}$]

sub V in equ (1),


$$V = V_1 + V_2 + V_3 \rightarrow (1)$$

$$\frac{Q}{C} = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3}$$

$$\frac{Q}{C} = Q \left[\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right]$$

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$
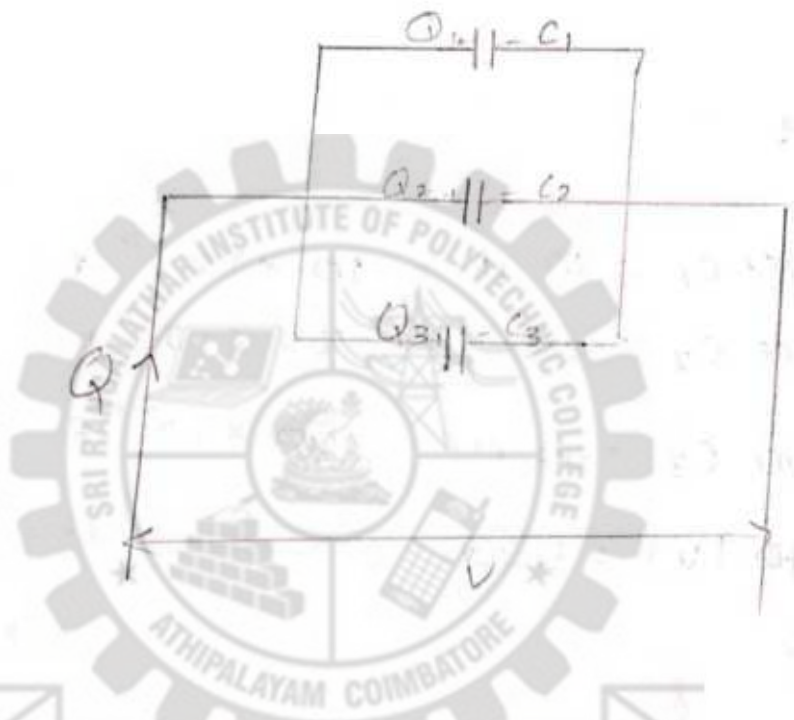
$$\left[\begin{array}{l} C = Q/V \\ \frac{1}{C} = \frac{1}{Q/V} \\ \frac{1}{C} = \frac{V}{Q} \\ \frac{Q}{V} = C \end{array} \right]$$



Total charge $Q = Q_1 + Q_2 + Q_3 \rightarrow$ (1)

[we know that $C = Q/V$, so $Q = CV$]

sub Q in equ (1)

$$CV = C_1V + C_2V + C_3V$$

$$CV = V [C_1 + C_2 + C_3]$$

$$C = C_1 + C_2 + C_3$$

18.08.2022
Thursday

11.12



Three capacitors 10MF, 25MF and 50MF are connected in a) Series b) parallel find the equivalent capacitance in each of the cases (a) and (b) when they connected across 500V supply.

Given data:

capacitance $C_1 = 10 \mu F = 10 \times 10^{-6} F$

capacitance $C_2 = 25 \mu F = 25 \times 10^{-6} F$

capacitance $C_3 = 50 \mu F = 50 \times 10^{-6} F$


Voltage (V) = 500V

To find

Total capacitance in series $1/C_T = ?$

Total capacitance in parallel $C_T = ?$

i) Series

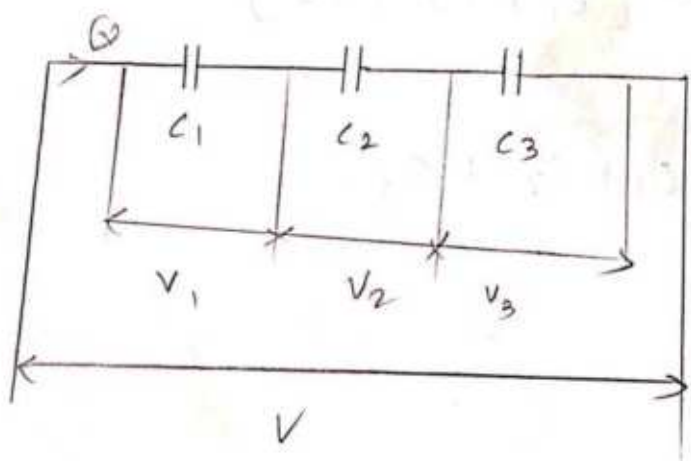


$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\frac{1}{C_T} = \frac{1}{(10 \times 10^{-6})} + \frac{1}{(25 \times 10^{-6})} + \frac{1}{(50 \times 10^{-6})}$$

$$\frac{1}{C_T} = 160,000$$

$$C_T = 6.25 \times 10^{-6} \text{ F}$$

ii) Parallel

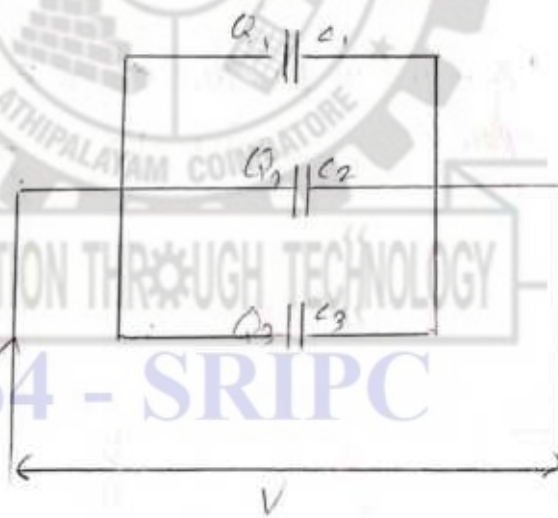

$$C = C_1 + C_2 + C_3$$

$$C = (10 \times 10^{-6}) + (25 \times 10^{-6}) + (50 \times 10^{-6})$$

$$C = 8.5 \times 10^{-5} \text{ F}$$

2) Three capacitors $23\mu\text{F}$, $31\mu\text{F}$, and $49\mu\text{F}$ are connected in a) series b) in parallel. find the equivalent capacitance in each of the cases (a) and (b) across 410V supply.

Given data.

$$\text{Capacitance } (C_1) = 23 \times 10^{-6} \text{ F}$$

$$\text{Capacitance } (C_2) = 31 \times 10^{-6} \text{ F}$$

$$\text{Capacitance } (C_3) = 49 \times 10^{-6} \text{ F}$$


$$\text{Voltage } (V) = 410 \text{ V}$$

To find

Total capacitance in parallel $C_T = ?$

Total capacitance in series $1/C_T = ?$

Series

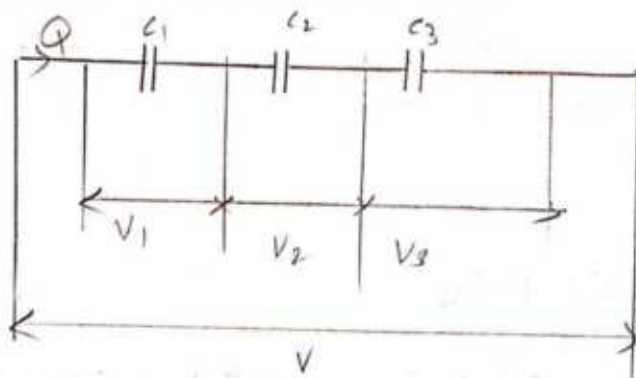

$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$


$$\frac{1}{C_T} = \frac{1}{(23 \times 10^{-6})} + \frac{1}{(31 \times 10^{-6})} + \frac{1}{(49 \times 10^{-6})}$$

$$\frac{1}{C_T} = 96,144.118$$

$$C_T = \frac{1}{96144.118}$$

$$C_T = 1.041 \text{ F}$$

2) Parallel

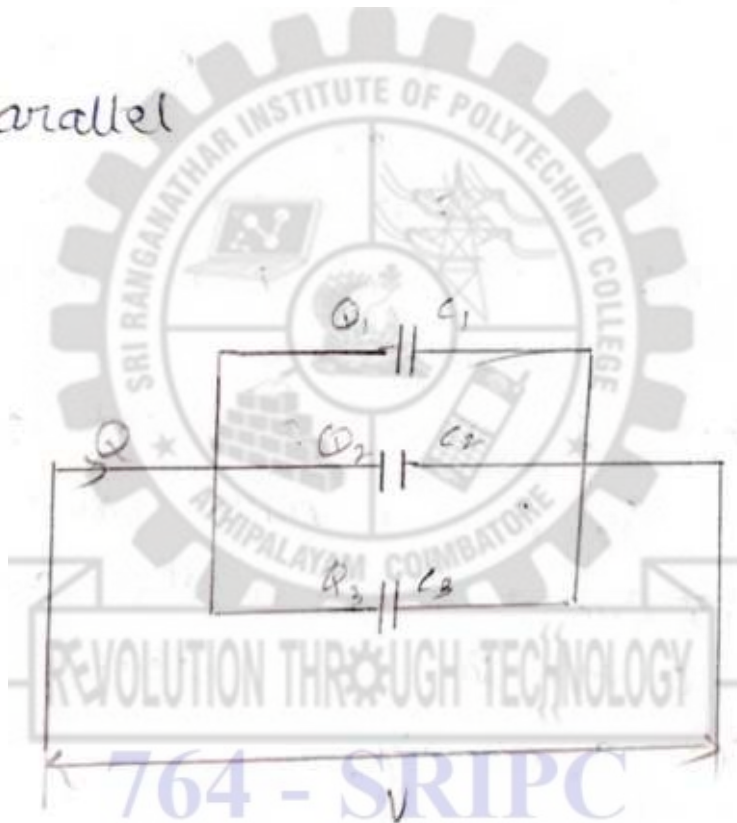

$$C = C_1 + C_2 + C_3$$

$$C = (23 \times 10^{-6}) + (31 \times 10^{-6}) + (49 \times 10^{-6})$$

$$C = 1.03 \times 10^{\text{OH}} \text{ F}$$

CIRCUIT THEOREM

Super position theorem

ഒരു രേഖീയ ബilaterൽ ഇലക്ട്രിക്കൽ സർക്യൂട്ടിൽ


ഒരു സർക്യൂട്ടിൽ n ന്റെ സോഴ്സുകൾ ഉണ്ടെങ്കിൽ ഏതെങ്കിലും ഓരോ സോഴ്സിനെയും മാത്രം സജീവമാക്കി മറ്റെല്ലാ സോഴ്സുകളെയും റിസെപ്റ്റർ സർക്യൂട്ടിന്റെ സെറിയൽ സർക്യൂട്ടിൽ ഉൾപ്പെടുത്തി സർക്യൂട്ടിലൂടെ ഒഴുകുന്ന കറന്റിന്റെ മൂല്യം കണ്ടെത്താൻ സാധിക്കും.

In a linear bilateral electrical circuit that is energised by two or more sources the current in any resistor is equal to the algebraic sum of the separate current in the resistor when each source acts separately.

Conditions for super position theorem:

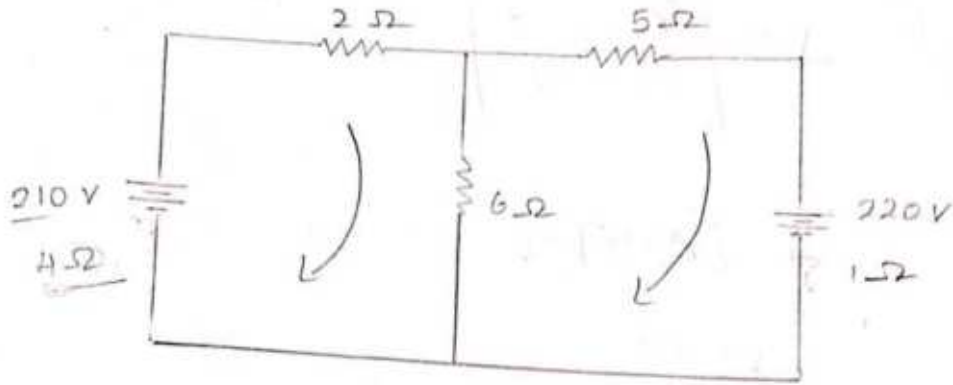1. while one source is applied the other sources are replaced by their respective internal resistance.
2. To replace the voltage sources it has to be short circuited by the internal resistance.


① Find the current through $6\text{-}\Omega$ resistor by using super position theorem



Step - 1

Soln.

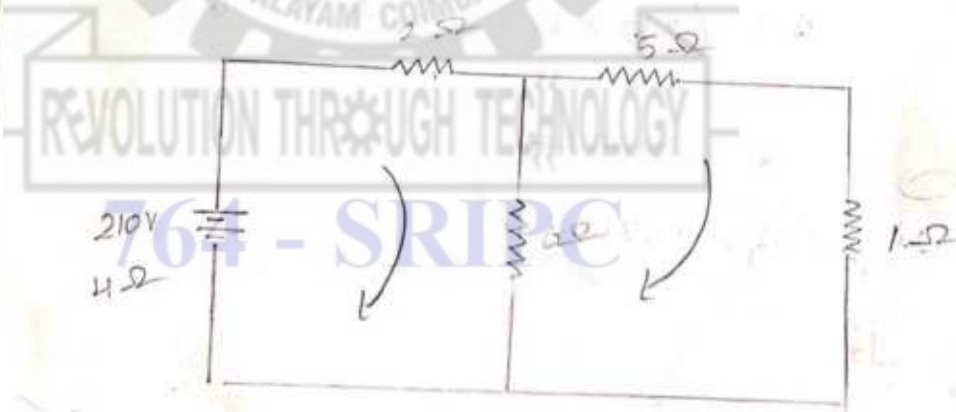210 V battery is acting alone, another 220V battery is replaced by its internal resistance.



$$\begin{bmatrix} R_{11} & R_{12} \\ R_{21} & R_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} 4 + 2 + 6 & -6 \\ -6 & 6 + 5 + 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 210 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} 12 & -6 \\ -6 & 12 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 210 \\ 0 \end{bmatrix}$$

To find Δ

$$\Delta = \begin{bmatrix} 12 & -6 \\ -6 & 12 \end{bmatrix}$$

$$\Delta = [12 \times 12] - [-6 \times -6]$$

$$\Delta = 108$$

To find Δ_1

$$\Delta_1 = \begin{bmatrix} 210 & -6 \\ 0 & 12 \end{bmatrix}$$

$$\Delta = (210 \times 12) - (0 \times -6)$$

$$\Delta = 2520$$

$$\Delta_1 = 2520$$

To find Δ_2

$$\Delta_2 = \begin{bmatrix} 12 & 210 \\ -6 & 0 \end{bmatrix}$$

$$\Delta_2 = [12 \times 0] - (-6 \times 210)$$

$$\Delta_2 = 1260$$

To find Δ

$$\Delta = \begin{bmatrix} 12 & -6 \\ -6 & 12 \end{bmatrix}$$

$$\Delta = [12 \times 12] - [-6 \times -6]$$

$$\Delta = 108$$

To find Δ_1

$$\Delta_1 = \begin{bmatrix} 210 & -6 \\ 0 & 12 \end{bmatrix}$$

$$\Delta = (210 \times 12) - (0 \times -6)$$

$$\Delta = 2520$$

$$\Delta_1 = 2520$$

To find Δ_2

$$\Delta_2 = \begin{bmatrix} 12 & 210 \\ -6 & 0 \end{bmatrix}$$

$$\Delta_2 = [12 \times 0] - (-6 \times 210)$$

$$\Delta_2 = 1260$$

To find current I_1 and I_2

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{2520}{108}$$

$$= 23.33 \text{ A}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{1260}{108}$$

$$= 11.66 \text{ A}$$

Therefore current through 6Ω Resistor by single surface acting is


$$I' = I_1 - I_2$$

$$I' = 23.33 - 11.66$$

$$I' = 11.67 \text{ A}$$

Step 2:

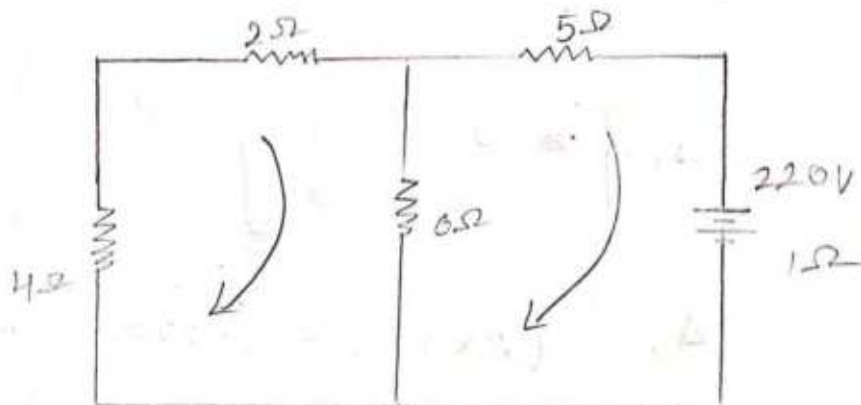220 V battery is acting alone, another 210 V battery is replaced by its internal resistance



$$\begin{bmatrix} R_{11} & R_{12} \\ R_{21} & R_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} 2+4+6 & -6 \\ -6 & 6+5+1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 0 \\ -220 \end{bmatrix}$$

$$\begin{bmatrix} 12 & -6 \\ -6 & 12 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 0 \\ -220 \end{bmatrix}$$

To find Δ

$$\Delta = \begin{bmatrix} 12 & -6 \\ -6 & 12 \end{bmatrix}$$

$$\Delta = (12 \times 12) - (-6 \times -6)$$

$$\Delta = 108$$

To find Δ_1

$$\Delta_1 = \begin{bmatrix} 0 & -6 \\ -220 & 12 \end{bmatrix}$$

$$\Delta_1 = (0 \times 12) - (-220 \times -6)$$

$$\Delta_1 = -1320$$

To find Δ_2

$$\Delta_2 = \begin{bmatrix} 12 & 0 \\ -6 & -220 \end{bmatrix}$$

$$\Delta_2 = (12 \times -220) - (-6 \times 0)$$

$$\Delta_2 = -2640$$

To find current I_1 and I_2

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{-1320}{108}$$

$$I_1 = -12.22 \text{ A}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{-2640}{108}$$

$$I_2 = -24.44 \text{ A}$$

$$I'' = I_1 - I_2$$

$$I'' = (-12.22) - (-24.44)$$

$$I'' = 12.22 \text{ A}$$

Step 3


Total current in 6Ω resistor
which two source acting together

$$I_r = I' + I''$$

$$I_T = [11.67] + [12.22]$$

$$I_T = 23.89 \text{ A}$$

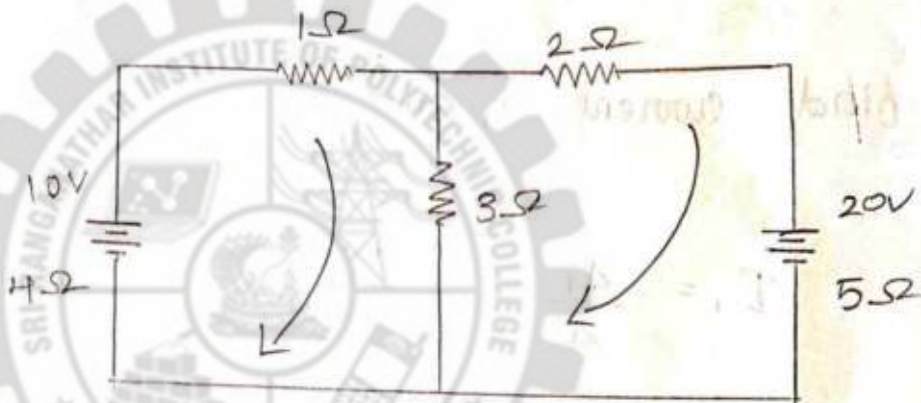- ② Find the current through 3Ω resistor by using super position theorem.




Current through 3Ω resistor. Write single source is acting.

764 - SRIPC

Step - 1

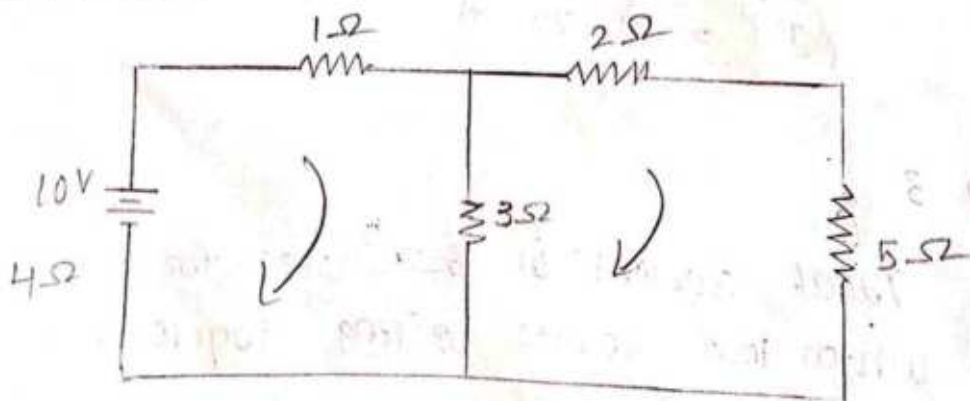10V battery is acting alone, another 20V battery is replaced by its internal resistance.



$$\begin{bmatrix} R_{11} & R_{12} \\ R_{21} & R_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} 4+1+3 & -3 \\ -3 & 3+2+5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 10 \\ 10 \end{bmatrix}$$

$$\begin{bmatrix} 8 & -3 \\ -3 & 10 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 10 \\ 10 \end{bmatrix}$$

To find Δ

$$\Delta = \begin{bmatrix} 8 & -3 \\ -3 & 10 \end{bmatrix}$$

$$\Delta = (8 \times 10) - (-3 \times -3)$$

$$\Delta = 71$$

To find Δ_1

$$\Delta_1 = \begin{bmatrix} 10 & -3 \\ 0 & 10 \end{bmatrix}$$

$$\Delta_1 = (10 \times 10) - (0 \times -3)$$

$$\Delta_1 = 100$$

To find Δ_2

$$\Delta_2 = \begin{bmatrix} 8 & 10 \\ -3 & 0 \end{bmatrix}$$

$$\Delta_2 = (8 \times 0) - (-3 \times 10)$$

$$\Delta_2 = 30$$

To find current I_1 and I_2

$$I_1 = \frac{V_1}{R_1} = \frac{100}{71}$$

$$I_1 = 1.40 \text{ A}$$

$$I_2 = \frac{V_2}{R_2} = \frac{30}{71}$$

$$I_2 = 0.42 \text{ A}$$


$$I' = I_1 - I_2$$

$$I' = 1.40 - 0.42$$

$$I' = 0.98 \text{ A}$$

Step 2 - SRIPC

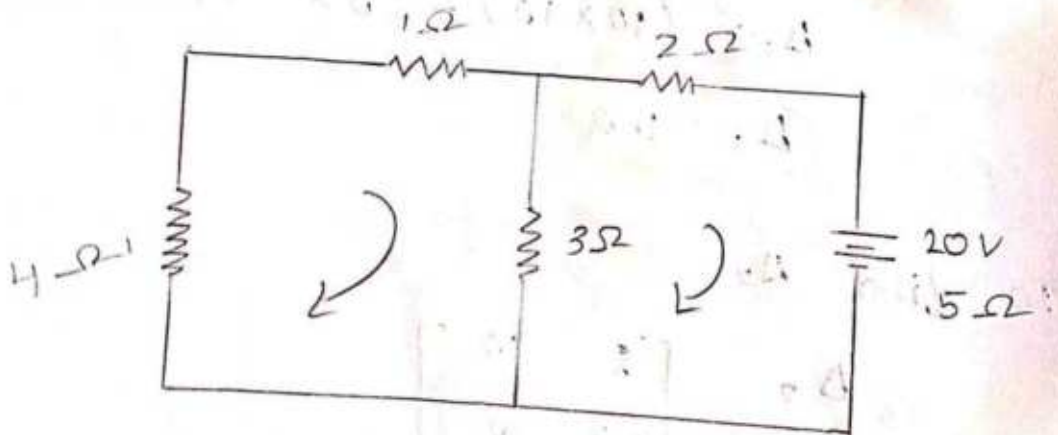20 v battery is acting alone, another 10 v battery is replaced by its internal resistance



$$\begin{bmatrix} R_{11} & R_{12} \\ R_{21} & R_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} 4+1+3 & -3 \\ -3 & 3+2+5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} 8 & -3 \\ -3 & 10 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} 8 & -3 \\ -3 & 10 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 0 \\ -20 \end{bmatrix}$$

To find Δ

$$\Delta = \begin{vmatrix} 8 & -3 \\ -3 & 10 \end{vmatrix}$$

$$\Delta = (8 \times 10) - (-3 \times -3)$$

$$\Delta = 71$$

To find Δ_1

$$\Delta_1 = \begin{vmatrix} 0 & -3 \\ -20 & 10 \end{vmatrix}$$

$$\Delta_1 = (0 \times 10) - (20 \times -3)$$

$$\Delta_1 = -60$$

To find Δ_2

$$\Delta_2 = \begin{vmatrix} 8 & 0 \\ -3 & -20 \end{vmatrix}$$

$$\Delta_2 = (8 \times -20) - (0 \times -3)$$

$$\Delta_2 = 160$$

To find current I_1 and I_2 .

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{-60}{74}$$

$$I_1 = -0.84 \text{ A}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{-160}{71}$$

$$I_2 = -2.25$$

$$I'' = I_1 + I_2$$

$$I'' = (-0.84) + (-2.25)$$

$$I'' = -3.09 \text{ A}$$

Step 3


$$I_T = I' + I''$$

$$I_T = (0.98) + (-3.09)$$

$$I_T = -2.39 \text{ A}$$

Thevenin's theorem

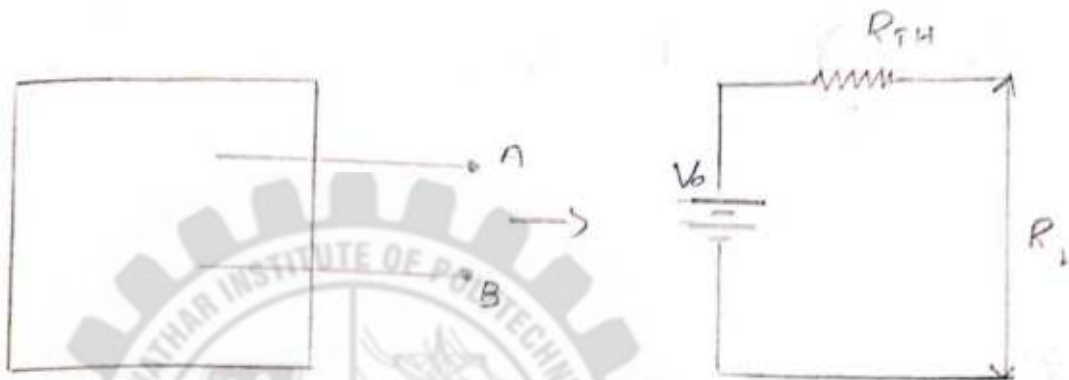A linear two terminal network can be replaced by a voltage source in series with the resistance.



$$\text{load current } I_L = \frac{V_0}{R_{Th} + R_L}$$

Where

R_{Th} - Thevenin's resistance

I_L - load current


V_0 - open source voltage

R_L - load resistance

conditions for Thevenin's theorem

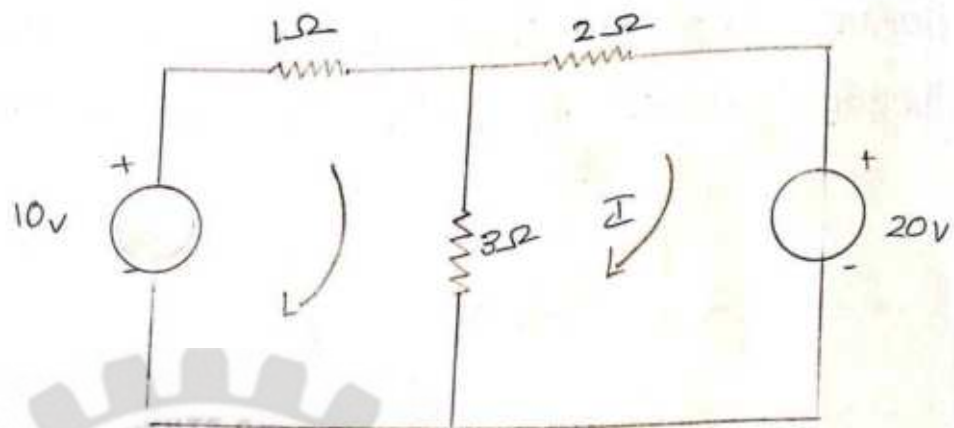1. Remove the load whose the current is required.
2. find the open circuit voltage which across the two terminals where the load is removed.
3. Determine the Thevenin's resistance.
4. find the current flowing through load resistance.


By using Thevenin's theorem. find the current through 3Ω resistor.



Soln.

Step - 1

To find V_0

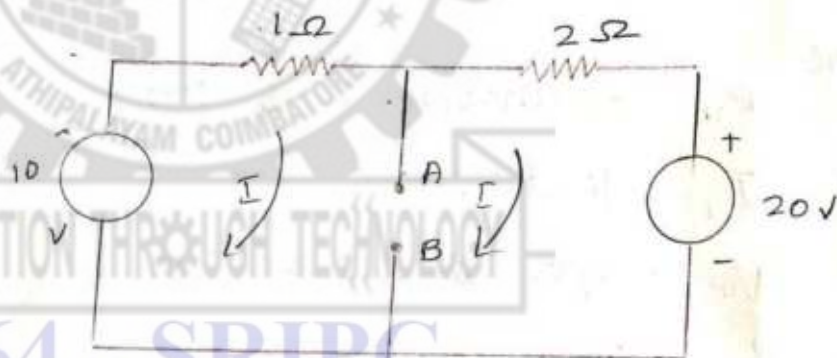

$$V_0 = V_{AB}$$

$$V_0 = 10V + \text{voltage drop } 1\Omega \text{ resistor}$$

$$V_0 = 10 + [I \times 1] \rightarrow (1)$$

To find 'I' by using KVL

$$-1I - 2I - 20 + 10 = 0$$

$$-3I - 10 = 0$$

$$-3I = 10$$

$$I = \frac{10}{-3}$$

$$I = -3.33 \text{ A}$$

[where to take current in positive
value due to open circuit voltage]

$$I' = 3.33 \text{ A}$$


Sub I' in equ (i) we get

$$V_o = 10 + [I \times 1] \rightarrow (i)$$

$$V_o = 10 + [3.33 \times 1]$$

$$V_o = 13.33 \text{ V}$$

Step 2 TO find R_{Th}

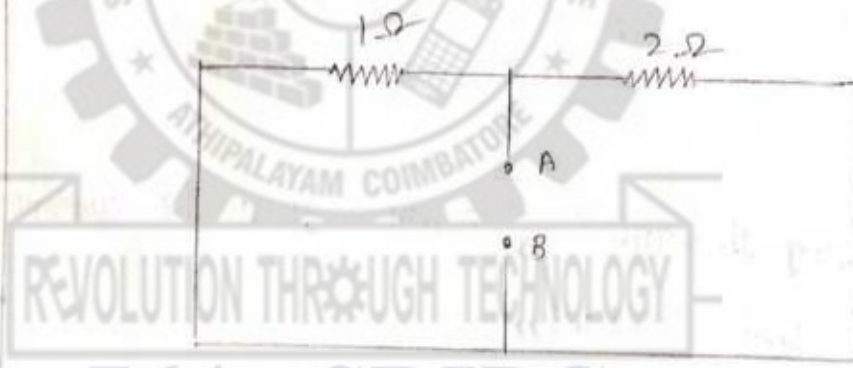

764 - SRIPC
from point A and B, Two resistance in parallel

$$\frac{1}{R_{Th}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_{Th}} = \frac{1}{1} + \frac{1}{2}$$

$$\frac{1}{R_{Th}} = 1.5$$


$$R_{Th} = \frac{1}{1.5}$$

$$R_{Th} = 0.66 \Omega$$

Step - 3

Thevanin's equivalent circuit


2x2
2x2x2x2

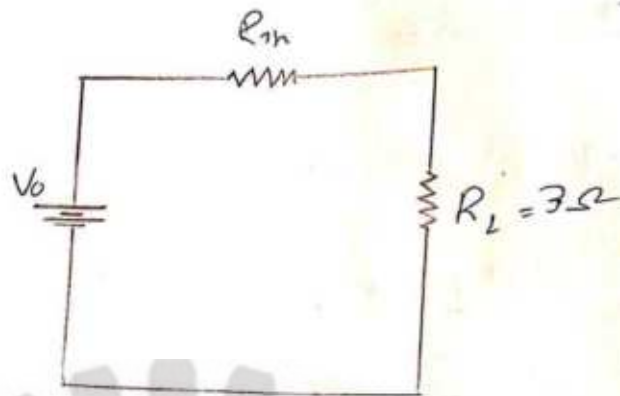

$$P_L = \frac{V_0^2}{R_{TH} + R_L} = \frac{13.33}{(0.66 + 3)}$$


$P_L = 3.64 \text{ A}$

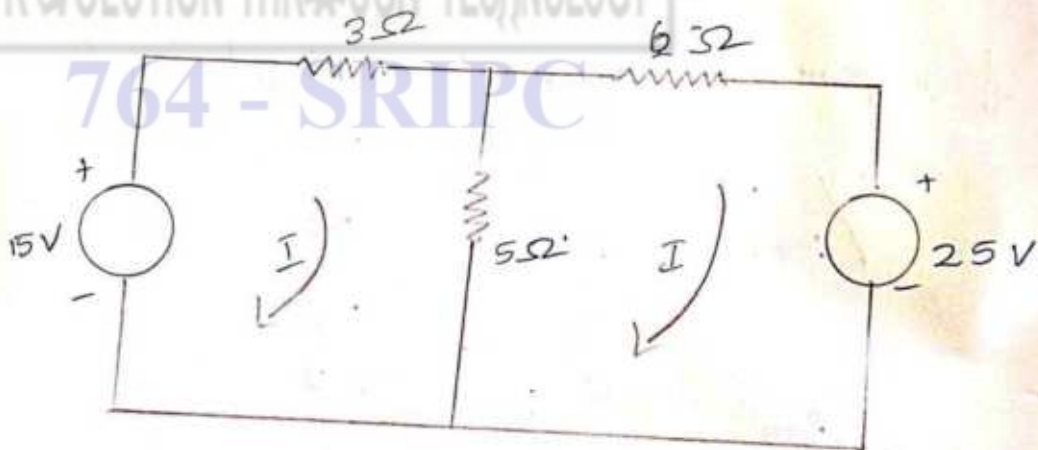By using thevanin's theorem. find the current through 5Ω resistor



Soln

Step - 1
To find V_0

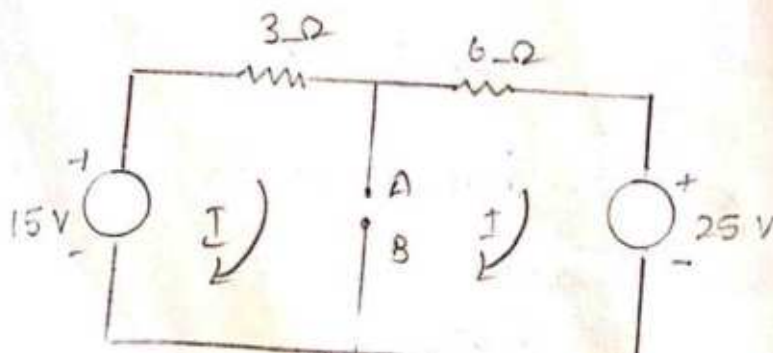

$$V_0 = V_{AB}$$

$V_0 = 15 \text{ V} +$ voltage drop across 3Ω resistor

$$V_0 = 15 + [I \times 3] \rightarrow \textcircled{1}$$

To find 'I' by using kir V 1

$$-3I - 6I - 25 + 15 = 0$$

$$-9I - 10 = 0$$

$$-9I = 10$$

$$I = 10 / -9$$

$$I = -1.11 \text{ A}$$

764 - SRIPC

$$I = 1.11 \text{ A}$$

(current in (+) value due to open circuit voltage)

sub "I" in equ $\textcircled{1}$


$$V_0 = 15 + [I \times 3] \rightarrow \textcircled{1}$$

$$V_0 = 15 + [1.11 \times 3]$$


$$V_0 = 18.33 \text{ V}$$

Step - 2

To find R_{th}

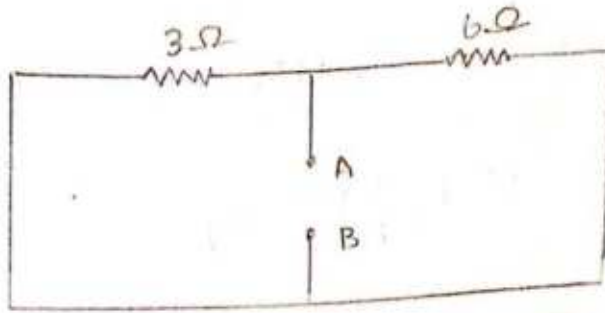

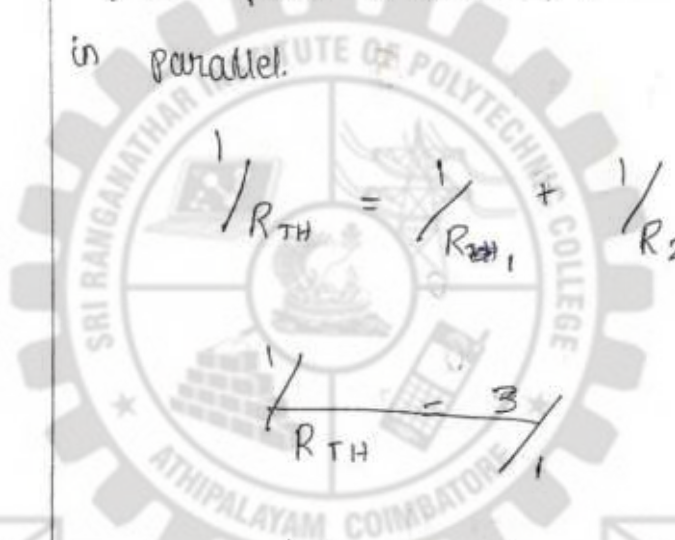from point A and B, two resistors are in parallel.



$$\frac{1}{R_{TH}} = \frac{1}{R_{TH1}} + \frac{1}{R_2}$$

$$\frac{1}{R_{TH}} = \frac{1}{3} + \frac{1}{6}$$

$$\frac{1}{R_{TH}} = \frac{1}{3} + \frac{1}{6}$$


764 - SRIPC

$$\frac{1}{R_{TH}} = 0.5$$

$$R_{TH} = \frac{1}{0.5}$$

$$R_{TH} = 2 \Omega$$

Step 3 Thevanin's equivalent circuit

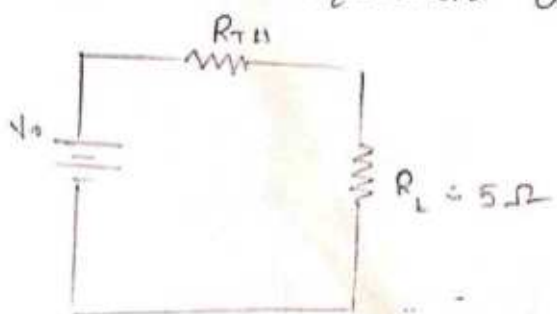


$$I_2 = \frac{V_0}{R_{TH} + R_L} = \frac{18.33}{(2 + 5)}$$

$$I_2 = 2.61 \text{ A}$$

MESH EQUATIONS

26.08.22
Friday :-

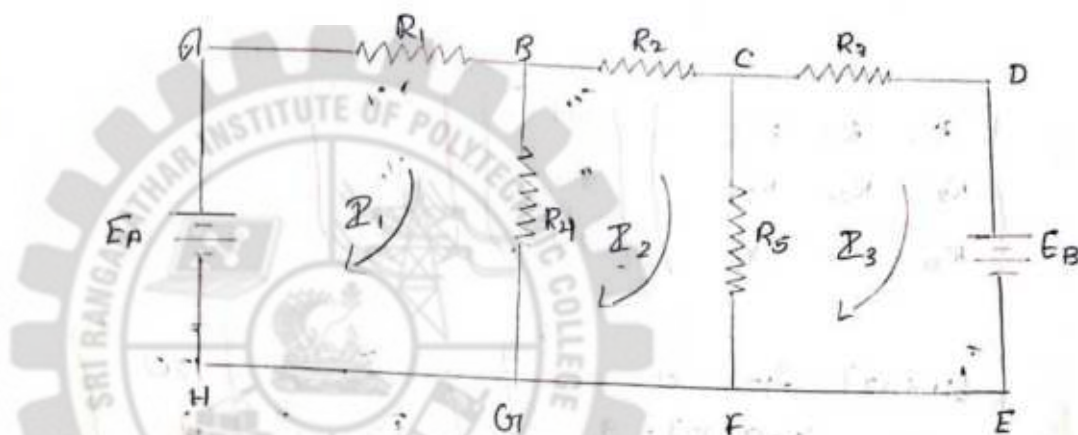

In loop ABGHA

$$-I_1 R_1 - (I_1 - I_2) R_4 + E_A = 0$$

$$-I_1 R_1 - (I_1 - I_2) R_4 = -E_A \rightarrow \textcircled{1}$$

In loop BCFCB

$$-I_1 R_2 - (I_2 - I_3) R_5 - (I_2) R_4 = 0 \rightarrow \textcircled{2}$$

In loop CDEFC


$$-I_3 R_3 - E_B - (I_3 - I_2) R_5 = 0$$

$$-I_3 R_3 - (I_3 - I_2) R_5 = E_B \rightarrow \textcircled{3}$$

final matrix method is

$$\begin{bmatrix} R_1 & R_2 & R_3 \\ R_2 & R_2 & R_3 \\ R_3 & R_3 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

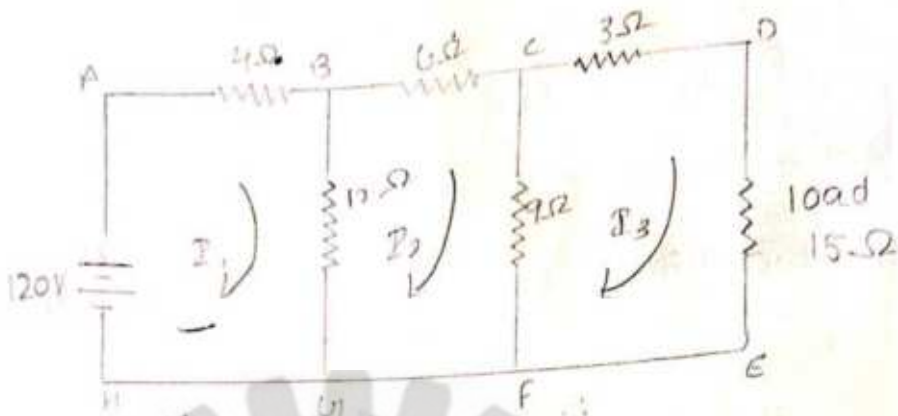from the circuit obtain the load current and power deliver to load.



$$\begin{bmatrix} R_{11} & R_{12} & R_{13} \\ R_{21} & R_{22} & R_{23} \\ R_{31} & R_{32} & R_{33} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

$$\begin{bmatrix} (4+12) & -12 & 0 \\ -12 & (6+9+12) & -9 \\ 0 & -9 & (3+15+9) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 120 \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} 16 & -12 & 0 \\ -12 & 27 & -9 \\ 0 & -9 & 27 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 120 \\ 0 \\ 0 \end{bmatrix}$$

To find Δ :

$$\Delta = \begin{vmatrix} 16 & -12 & 0 \\ -12 & 27 & -9 \\ 0 & -9 & 27 \end{vmatrix}$$

$$\Delta = 16 \begin{vmatrix} 27 & -9 \\ -9 & 27 \end{vmatrix} - (-12) \begin{vmatrix} -12 & -9 \\ 0 & 27 \end{vmatrix} + 0 \begin{vmatrix} -12 & 27 \\ 0 & -9 \end{vmatrix}$$

$$= 16 (27 \times 27) - (-9 \times (-9)) + 12 (-12 \times 27) - (-9 \times 0)$$

$$= 16 (-12 \times -9) - (27 \times 0)$$

$$\Delta = 6480$$

To find Δ_3

$$\Delta_3 = \begin{bmatrix} 16 & -12 & 120 \\ -12 & 27 & 0 \\ 0 & -9 & 0 \end{bmatrix}$$

$$\Delta_3 = \begin{vmatrix} 16 & 27 & 0 \\ -12 & 27 & 0 \\ 0 & -9 & 0 \end{vmatrix} - (-12) \begin{vmatrix} -12 & 0 \\ 0 & 0 \end{vmatrix} + 120 \begin{vmatrix} -12 & 27 \\ 0 & -9 \end{vmatrix}$$

$$\Delta_3 = 16[(27 \times 0) - (-9 \times 0)] + 12[(12 \times 0) - (0 \times 0)] + 120[(-12 \times -9) - (0 \times 27)]$$

$$\Delta_3 = 12960$$

To find I_3


$$\therefore \frac{\Delta_3}{\Delta} = \frac{12960}{6480}$$

$$I_3 = 2 \text{ A}$$

$$P = I^2 R$$
$$P = (2)^2 \times (15)$$

$$P = 60 \text{ W}$$

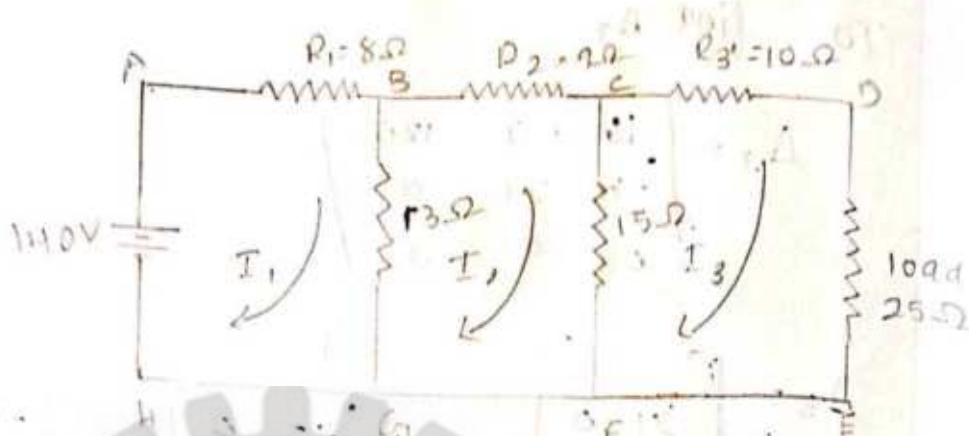from the circuit obtain the load current and power delivered to load.



$$\begin{bmatrix} R_{11} & R_{12} & R_{13} \\ R_{21} & R_{22} & R_{23} \\ R_{31} & R_{32} & R_{33} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

$$\begin{bmatrix} 8+13 & -13 & 0 \\ -13 & 13+9+15 & -15 \\ 0 & -15 & 15+10+25 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

$$\begin{bmatrix} 21 & -13 & 0 \\ -13 & 37 & -15 \\ 0 & -15 & 50 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

$$\begin{bmatrix} 21 & -13 & 0 \\ -13 & 37 & -15 \\ 0 & -15 & 50 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 140 \\ 0 \\ 0 \end{bmatrix}$$

To find Δ

$$\Delta = \begin{bmatrix} 21 & -13 & 0 \\ -13 & 37 & -15 \\ 0 & -15 & 50 \end{bmatrix}$$

$$\Delta = 21 \begin{vmatrix} 37 & -15 \\ -15 & 50 \end{vmatrix} - (-13) \begin{vmatrix} -13 & -15 \\ 0 & 50 \end{vmatrix} \\ 0 \begin{vmatrix} -13 & 37 \\ 0 & -15 \end{vmatrix}$$

$$= 21 [(37 \times 50) - (-15 \times -15)] + 13 [(-13 \times 50) - (-15 \times 0)] \\ 0 [(-13 \times -15) - (0 \times 37)]$$

$$\Delta = 25,675$$

To find Δ_3

$$\Delta_3 = \begin{bmatrix} 21 & -13 & 0 \\ -13 & 37 & 15 \\ 0 & -15 & 50 \end{bmatrix} \\ \Delta_3 = \begin{bmatrix} 21 & -13 & 140 \\ -13 & 37 & 0 \\ 0 & -15 & 0 \end{bmatrix}$$

$$\Delta_3 = 21 \begin{vmatrix} 37 & 0 \\ -15 & 0 \end{vmatrix} + 13 \begin{vmatrix} -13 & 0 \\ 0 & 0 \end{vmatrix} + 140 \begin{vmatrix} -13 & 37 \\ 0 & -15 \end{vmatrix}$$

$$21 [(37 \times 0) - (-15 \times 0)] + 13 [(-13 \times 0) - (0 \times 0)]$$

$$140 [(-13 \times -15) - (37 \times 0)]$$

$$\Delta_3 = 27300$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{27,300}{25675}$$

$$I_3 = 1.06 \text{ A}$$


To find power

$$P = I^2 R$$

$$P = (1.06)^2 \times (25)$$

$$P = 28.09 \text{ W}$$

③ from the circuit; find I_1 and I_2

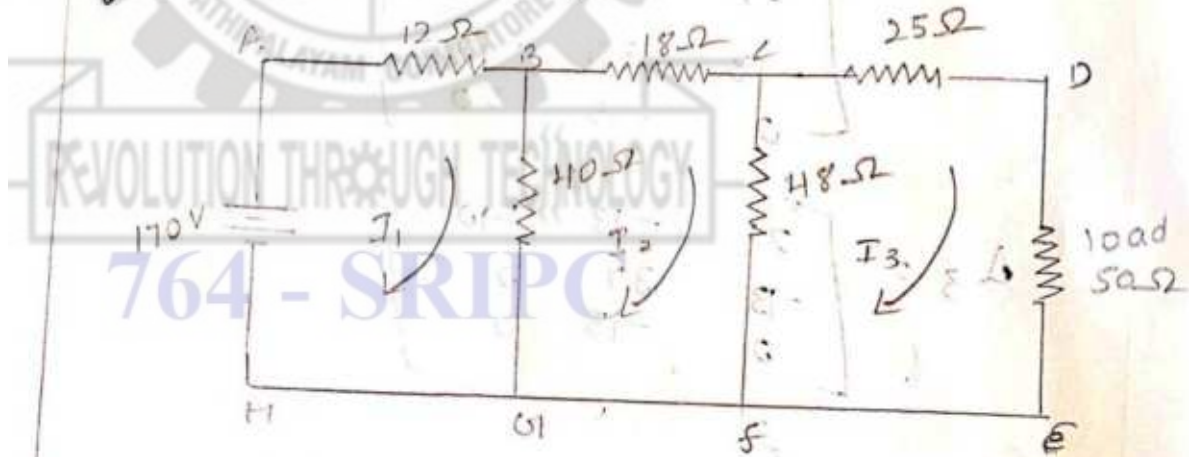

$$\begin{bmatrix} R_{11} & R_{12} & R_{13} \\ R_{21} & R_{22} & R_{23} \\ R_{31} & R_{32} & R_{33} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$


$$\begin{bmatrix} (2 + 40) & -40 & 0 \\ -40 & (40 + 18 + 48) & -48 \\ 0 & -48 & (48 + 25 + 50) \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

Norton's Theorem

Monday 30

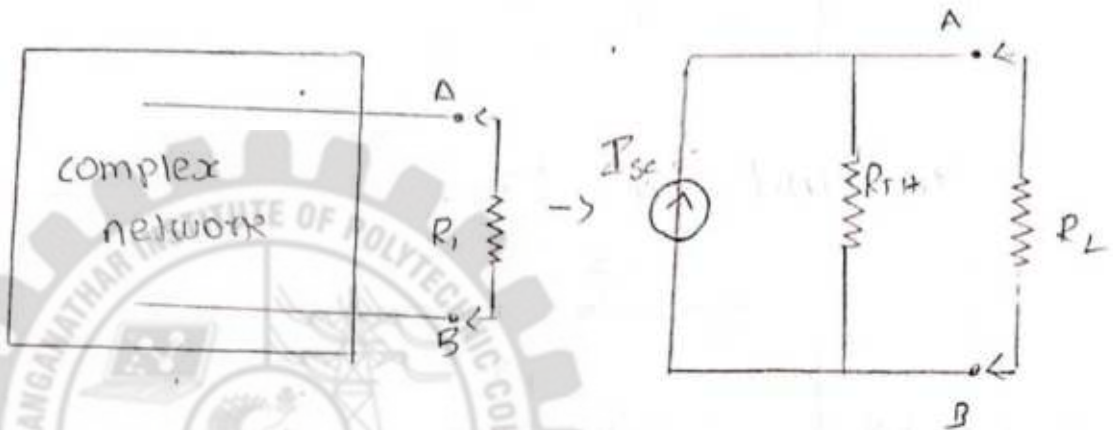Norton's theorem state that any two terminal network can be reduced to a current source in parallel with a resistor.



I_{sc} → Short circuit current

R_{TH} → Thevenin's looking back resistance


$$\text{Load current } I_L = I_{sc} \times \frac{R_{TH}}{R_{TH} + R_L}$$

Conditions for Norton's Theorem

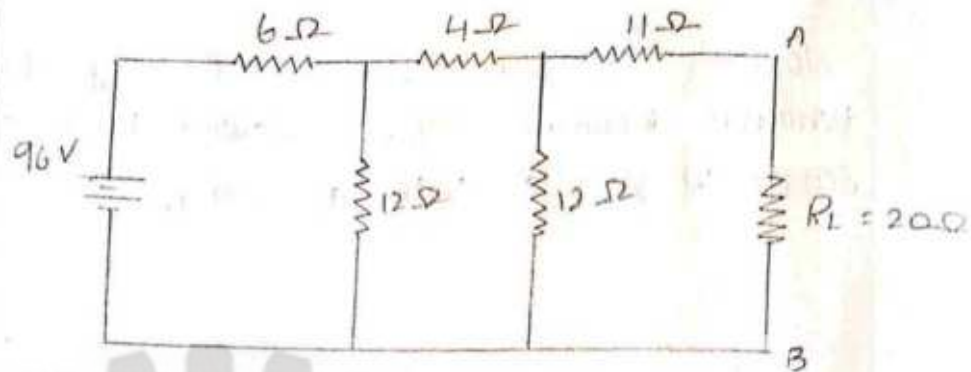
1. Remove the load resistance and put a short circuit
2. I_{sc} find the short circuit current and thevenin's looking back resistance.
3. Replace all voltage's by their internal resistance.
4. To find load current

$$\text{load current } I_L = I_{sc} \times \frac{R_{TH}}{R_{TH} + R_L}$$

① find the current through R_L by using Norton's theorem



To find $I_{sc} = I_3$

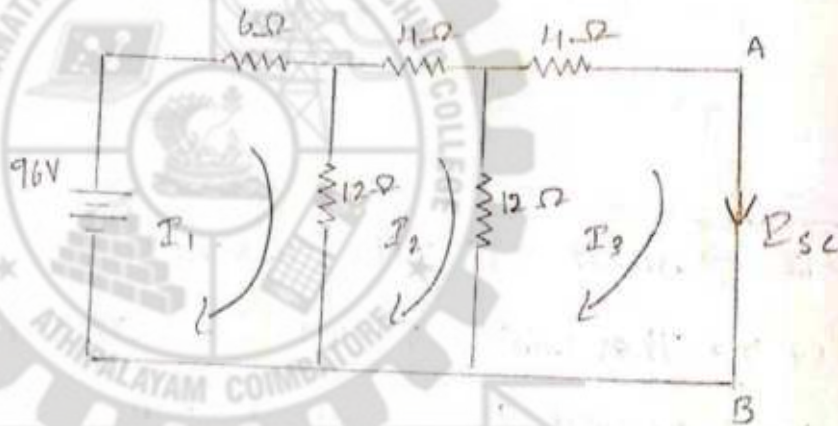

By mesh current method

$$\begin{bmatrix} R_{11} & R_{12} & R_{13} \\ R_{21} & R_{22} & R_{23} \\ R_{31} & R_{32} & R_{33} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

$$\begin{bmatrix} 6+12 & -12 & 0 \\ -12 & 12+4+12 & -12 \\ 0 & -12 & 12+11 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 96 \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} 18 & -12 & 0 \\ -12 & 28 & -12 \\ 0 & -12 & 16 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix} = \begin{bmatrix} 96 \\ 0 \\ 0 \end{bmatrix}$$

To find Δ_1

$$= 18 \begin{vmatrix} 28 & -12 \\ -12 & 16 \end{vmatrix} + 12 \begin{vmatrix} -12 & -12 \\ 0 & 16 \end{vmatrix} + 0 \begin{vmatrix} -12 & 28 \\ 0 & -12 \end{vmatrix}$$

$$= 18 [(28 \times 16) - (-12 \times -12)] + 12 [(-12 \times 16) - (-12 \times 0)]$$

$$+ 0 [(-12 \times -12) - (28 \times 0)]$$

$$= 3168$$

$$\Delta_1 = 3168$$

To find Δ_2

$$\Delta_2 = \begin{vmatrix} 18 & -12 & 96 \\ -12 & 28 & 0 \\ 0 & -12 & 0 \end{vmatrix}$$

$$\Delta_2 = 18 \begin{vmatrix} 28 & 0 \\ -12 & 0 \end{vmatrix} + 12 \begin{vmatrix} -12 & 0 \\ 0 & 0 \end{vmatrix} + 96 \begin{vmatrix} -12 & 28 \\ 0 & -12 \end{vmatrix}$$

$$\Delta_2 = 18 [(28 \times 0) - (0 \times -12)] + 12 [(-12 \times 0) - (0 \times 0)]$$

$$+ 96 [(-12 \times -12) - (28 \times 0)]$$

$$\Delta_3 = 13824$$


To find I_3

$$I_3 = \frac{\Delta_3}{\Delta}$$

$$I_3 = \frac{13824}{3168}$$

$$I_3 = 4.36 \text{ A} = I_{sc}$$

Step 2: find R_{TH}

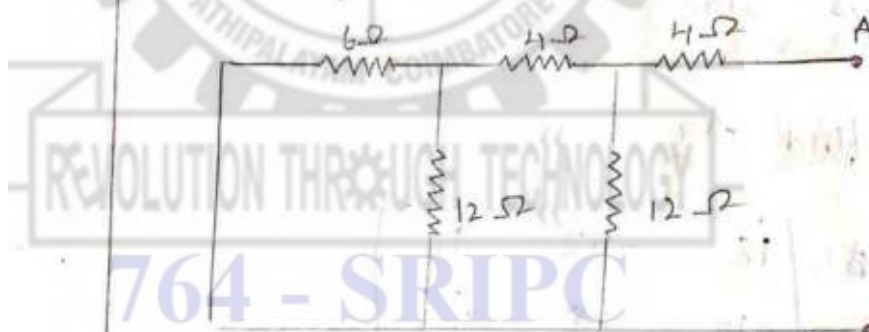


The above circuit is simplified as 6Ω and 12Ω resistances are in parallel

$$\frac{1}{R_2} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_2} = \frac{1}{6} + \frac{1}{12}$$


$$\frac{1}{R_2} = 0.25$$
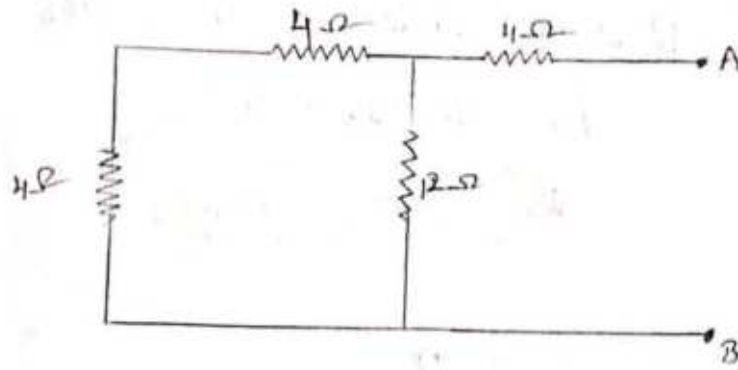
$$R_2 = \frac{1}{0.25} \quad R_2 = 4\Omega$$



4Ω and 11Ω are in series $R_{T1} = R_1 + R_2$
 $= 4 + 11 = 8\Omega$

$$R_T = 8\Omega$$

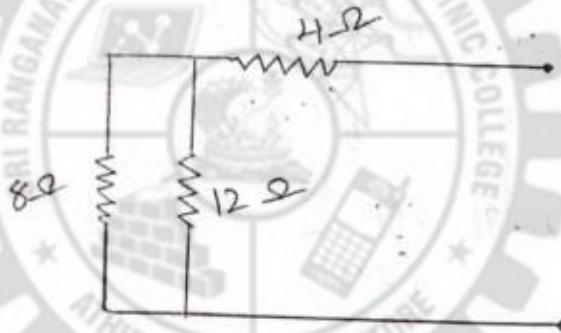

8Ω and 12Ω are in parallel


$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_T} = \frac{1}{8} + \frac{1}{12}$$

$$\frac{1}{R_T} = 0.20$$

$$R_T = \frac{1}{0.20}$$

$$R_T = 5\Omega$$

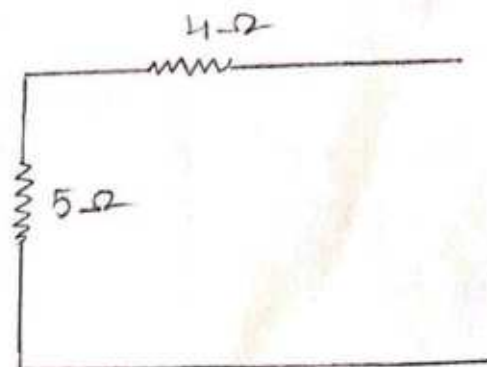

R. R_1 and 4Ω are in series

$$R_T = R_1 + R_2 = 4 + 5$$

$$R_T = 9\Omega = R_{Th}$$

Step 3: To find I_L


$$I_L = I_{SC} \times \frac{R_{Th}}{R_{Th} + R_L}$$

$$I_L = (4.36) \times \frac{(9)}{(9+20)}$$


$$I_L = 4.36 \times \frac{(9)}{(29)}$$

$$I_L = 1.35 A$$

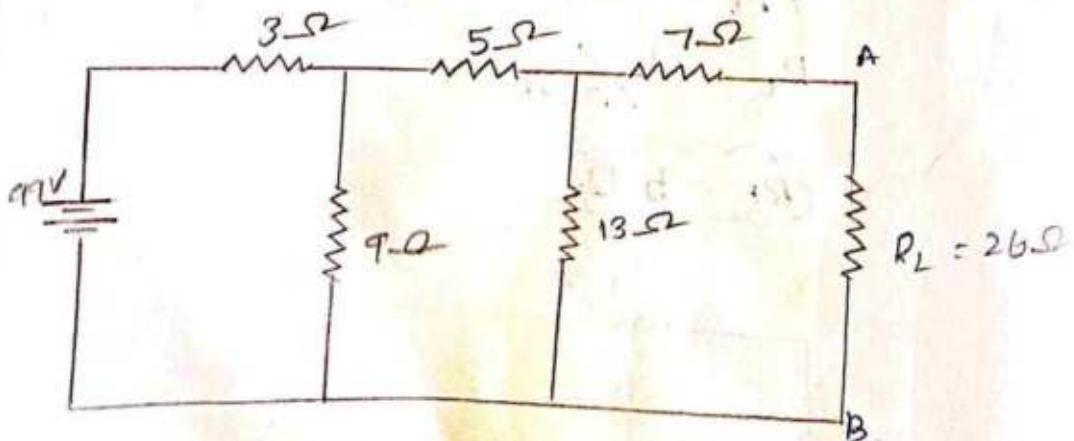② Find the current through R_L , by using Norton's theorem



To find :

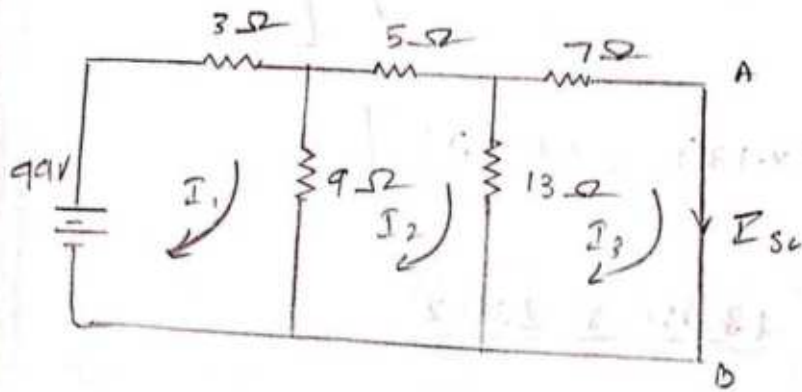

By mesh current method

$$\begin{bmatrix} R_{11} & R_{12} & R_{13} \\ R_{21} & R_{22} & R_{23} \\ R_{31} & R_{32} & R_{33} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

$$\begin{bmatrix} 3+9 & -9 & 0 \\ -9 & 9+5+13 & -13 \\ 0 & -13 & 13+7 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

$$\begin{bmatrix} 12 & -9 & 0 \\ -9 & 27 & -13 \\ 0 & -13 & 20 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 & 99 \\ V_2 & 0 \\ 0 & 0 \end{bmatrix}$$

To find delta Δ

$$\Delta = 12 \begin{vmatrix} 27 & -13 \\ -13 & 20 \end{vmatrix} + 9 \begin{vmatrix} -9 & -13 \\ 0 & 20 \end{vmatrix} + 0 \begin{vmatrix} -9 & 27 \\ 0 & -13 \end{vmatrix}$$

$$12 \left[(27 \times 20) - (-13 \times -13) \right] + 9 \left[(-9 \times 20) - (-13 \times 0) \right]$$

$$+ 0 \left[(-9 \times -13) - (27 \times 0) \right]$$

$$= \Delta = 2832$$

To find I_3

$$\Delta_3 = \begin{vmatrix} 12 & -9 & 99 \\ -9 & 27 & 0 \\ 0 & -13 & 0 \end{vmatrix}$$

$$\Delta_3 = 12 \begin{vmatrix} 27 & 0 \\ -13 & 0 \end{vmatrix} + 9 \begin{vmatrix} -9 & 0 \\ 0 & 0 \end{vmatrix} + 99 \begin{vmatrix} -9 & 27 \\ 0 & -13 \end{vmatrix}$$

$$= 12 \left[(27 \times 0) - (0 \times -13) \right] + 9 \left[(-9 \times 0) - (0 \times 0) \right]$$

$$+ 99 \left[(-9 \times -13) - (27 \times 0) \right]$$


$$\Delta_3 = 11583$$

To find I_3

$$I_3 = \frac{\Delta_3}{\Delta}$$

$$I_3 = 4.09 \text{ A} = I_{sc}$$

Step 2 find R_{TH}

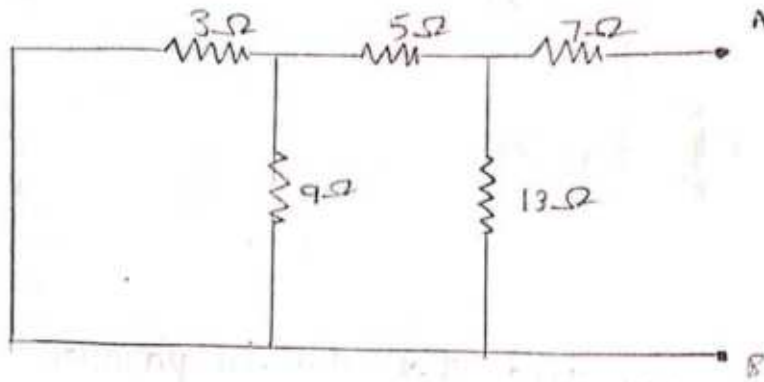

The above circuit as 3Ω and 9Ω

$$\frac{1}{R_{TH}} = \frac{1}{R_1} + \frac{1}{R_2}$$


$$\frac{1}{R_{TH}} = \frac{1}{3} + \frac{1}{9}$$

$$\frac{1}{R_{TH}} = 0.44$$

$$R_{TH} = \frac{1}{0.44}$$

$$R_{TH} = 2.27\Omega$$

764 - SRIPC

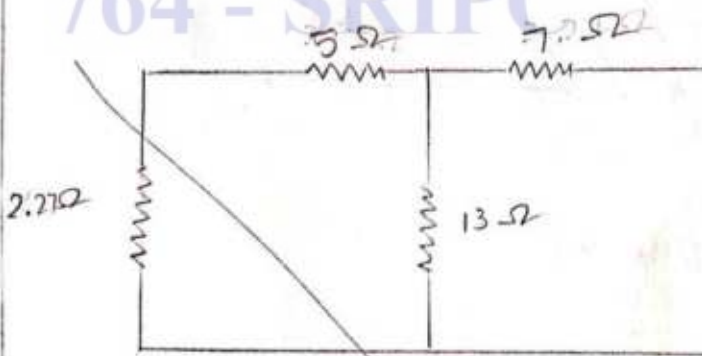


2.27Ω and 2.27Ω are in series

$$R_T = R_1 + R_2$$

$$R_T = 2.27 + 2.27$$

$$R_T = 4.54\Omega$$

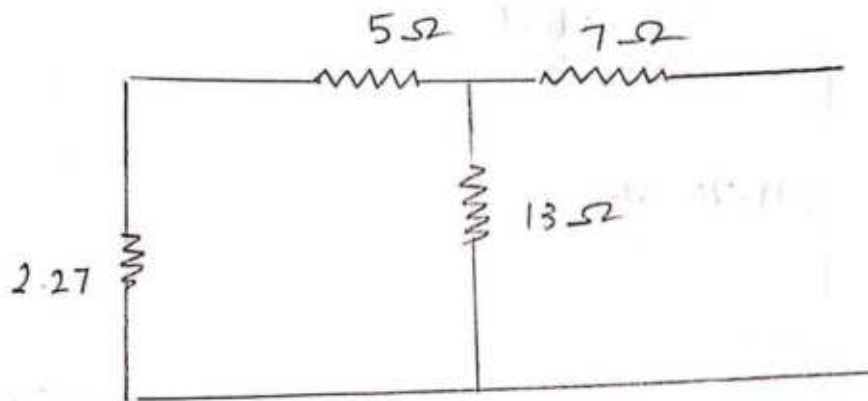


2.27 Ω and 5 Ω are in series

$$R_T = R_1 + R_2$$

$$R_T = 2.27 + 5$$

$$R_T = 7.27 \Omega$$

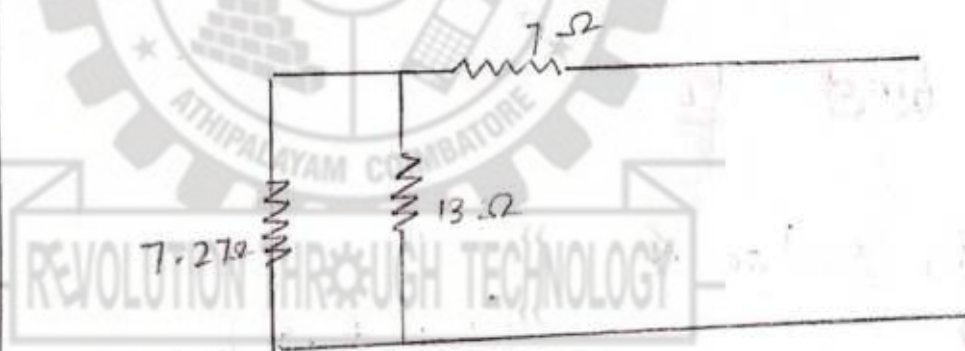

764 - SRIPC

7.27 Ω and 13 Ω are in parallel


$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_T} = \frac{1}{7.27} + \frac{1}{13}$$

$$\frac{1}{R_T} = 0.21 \Omega$$

$$R_T = \frac{1}{0.21}$$

$$R_T = 4.76 \Omega$$

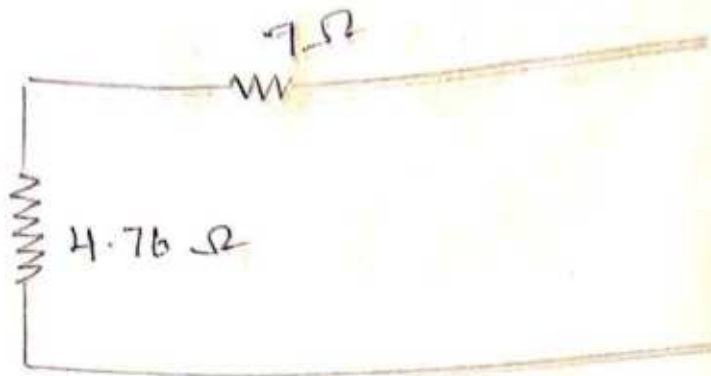

4.76Ω and 7Ω are in series

$$R_T = R_1 + R_2$$

$$R_T = 4.76 + 7$$

$$R_T = 11.76$$

To find I_L

$$I_L = I_{sc} \times \frac{R_{TH}}{(R_{TH} + R_L)}$$


$$I_L = (4.09) \times \frac{(11.76)}{(11.76 + 26)}$$

$$I_L = 1.27 A$$

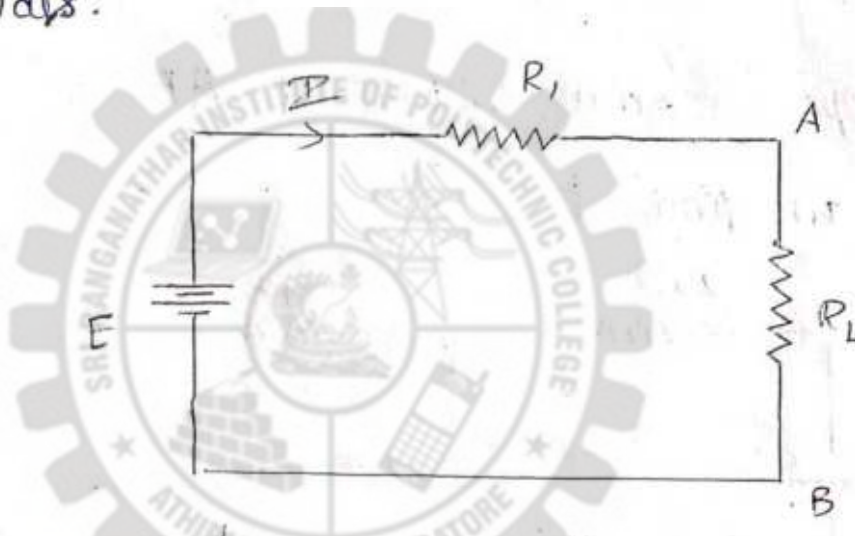01.09.2022
Thursday ☺

Maximum Power Transfer Theorem

In dc circuits maximum power is transferred from a source to load resistance is made equal to the internal resistance or looking back resistance of the network from the load terminals.




Maximum power $P_{max} = \frac{E^2}{4R_L}$ Watts

where, E^2 = Voltage

R_L = load resistance


①

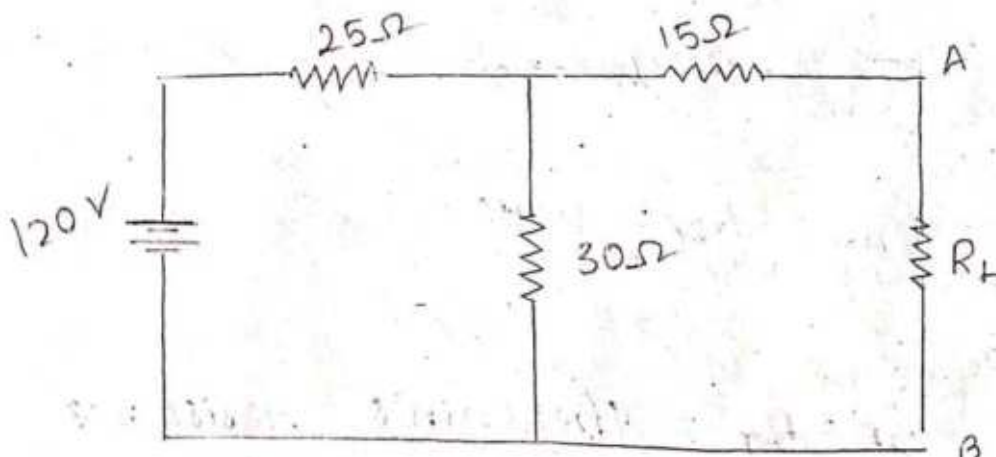calculate the value of the load resistance for maximum power transferred from the circuit. Also find the value of maximum power.




Soln

Thevenin's Equivalent circuit.

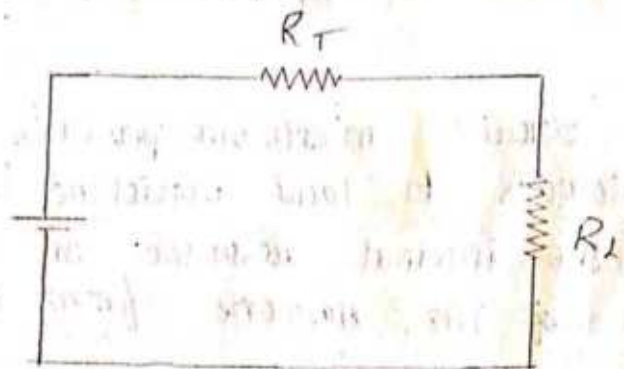

Open circuit voltage of AB

Step-1 TO find E

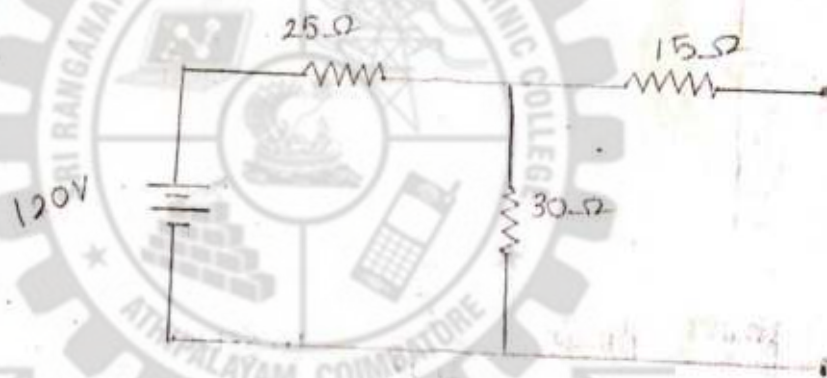

$E = V_{AB}$ = Voltage across 30Ω resistance

$$V_{AB} = I \times 30$$

$$V_{AB} = \left(\frac{V}{R} \right) \times 30 \quad \left(\begin{array}{l} \sin \theta \\ I = V/R \end{array} \right)$$


$$V_{AB} = \left[\frac{(120)}{(25 + 30)} \right] \times 30$$

$$V_{AB} = 2.18 \times 30$$

$$V_{AB} = 65.4 \text{ VOLTS} = E$$

Step 2 :

$R_L = R_T$ = Thevenin's resistance

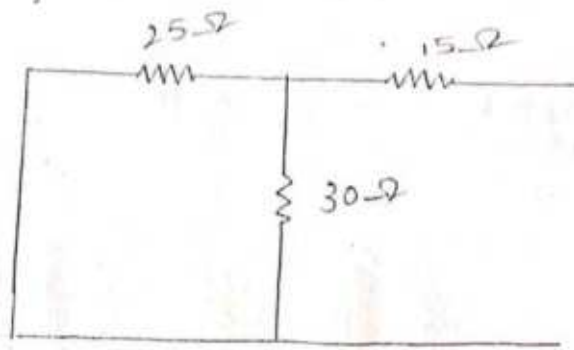


25Ω 30Ω are in parallel

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_T} = \frac{1}{25} + \frac{1}{30}$$

$$R_T = 14.28\Omega$$

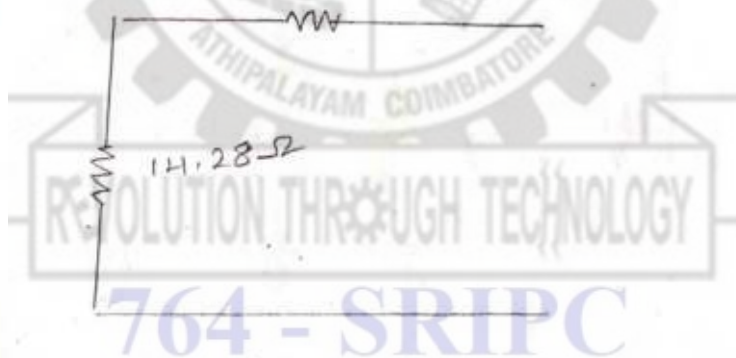

14.28Ω are in series

$$R_T = R_1 + R_2$$

$$R_T = 14.28 + 15$$

$$R_T = 29.28\Omega$$


Step 3

$$\text{maximum power } P_{\max} = \frac{E^2}{4R_2}$$

$$P_{\max} = \frac{(65.4)^2}{(4) \times (29.8)}$$

$$P_{\max} = 35.88 \text{ W}$$

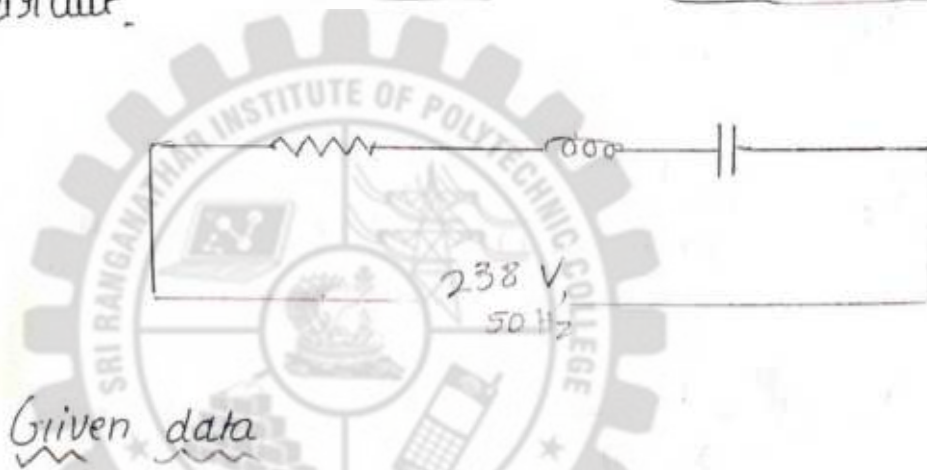A series RLC series circuit with a resistance of 72 ohm , a capacitor of 63.2 microfarad and an inductance of 0.29 H is connected across 238 V , 50 Hz supply. Determine the impedance, power factor and power consumed by the circuit.



Given data

$$\text{Resistance} = 72 \text{ ohm}$$

$$\text{capacitor} = 63.2 \text{ microfarad} \Rightarrow 63.2 \times 10^{-6}$$

$$\text{Inductance} = 0.29 \text{ H}$$

$$\text{voltage} = 238 \text{ V}$$

$$\text{frequency} = 50 \text{ Hz}$$

To find

$$\text{impedance} = ?$$

$$\text{Power factor} = ?$$

$$\text{Power consumed} = ?$$

Soln.

To find impedance?

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Where

$$X_L = 2\pi fL$$

$$X_L = (2) \times (3.14) \times (50) \times (0.29)$$

$$X_L = 91.06 \Omega$$

$$X_C = \frac{1}{2\pi fC}$$

$$X_C = \frac{1}{(2) \times (3.14) \times (50) \times (63.2 \times 10^{-6})}$$

$$X_C = \frac{1}{0.019}$$

$$X_C = 52.63 \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \sqrt{(72)^2 + (91.06 - 52.63)^2}$$

$$Z = \sqrt{(5184) + (1476.86)}$$

$$= \sqrt{6660.86}$$

$$Z = 81.61 \Omega$$

Step 2:

To find power factor ϕ

$$\cos \phi \text{ or } \frac{P}{Z}$$

$$\frac{R}{Z}$$

$$\frac{72}{81.61}$$

$$0.88$$

power factor = 0.88

Step 3

To find current = ?

$$I = \frac{V}{Z}$$

$$I = \frac{238}{81.61}$$

$$I = 2.91 \text{ A}$$

Step iv
To find power = ?

$$(\text{power } P = VI \cos \phi)$$

$$P = (238) \times (2.91) \times (0.88)$$

$$P = 609.47 \text{ watts}$$

Polar and Rectangular formsPolar form $\rightarrow 10 \angle 40^\circ$ Rectangular form $\rightarrow 10 + j 40$ ① convert the vector $10 + j 22$ into polar formAns $24.16 \angle 65.55$

①

convert the vector $23.5 + j 39.9$ into polar form $46.30 \angle 59.50$ ② convert the polar form $10 \angle 30^\circ$ into vector form $8.66 + j 5$ convert the polar form $21 \angle -45^\circ$ convert the vector $15 - j 22.3$ into polar form, $26.87 \angle 56.07$ convert the polar form $21 \angle -45^\circ$ into vector form ~~$14.84 + j 14.84$~~ $14.84 - j 14.84$

① Two impedances $Z_1 = 8 + j6$ and $Z_2 = 3 - j4$ are connected in parallel across a 230V, 50Hz supply. Calculate (a) current in each branch (b) total current of the circuit (c) power factor (d) power taken by the circuit.

Given data:

$$\text{Impedance } Z_1 = (8 + j6) \Rightarrow 10 \angle 36.86^\circ$$

$$\text{Impedance } Z_2 = (3 - j4) \Rightarrow 5 \angle -53.1^\circ$$

$$\text{Voltage } V = 230\text{V}$$

$$\text{frequency } F = 50\text{ Hz}$$

TO find:

Branch current I_1 and $I_2 = ?$

Total current $[I] = ?$

Power factor = ?

Power = ?

764 - SRIPC

Solution:

①

$$I_1 = \frac{V}{Z_1} = \frac{230 \angle 0^\circ}{10 \angle 36.86^\circ}$$

$$I_1 = 23 \angle -36.86^\circ \text{ Amps}$$

$$I_2 = \frac{V}{Z_2} = \frac{230 \angle 0^\circ}{5 \angle -53.1^\circ}$$

$$I_2 = 46 \angle 53.1^\circ \text{ Amps}$$

(ii)

Total current

Both Impedance are in parallel

$$\frac{1}{Z_T} = \frac{1}{Z_1} + \frac{1}{Z_2} \quad \text{L.C.M} \Rightarrow$$

By L.C.M

$$Z = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

$$\frac{Z_1 Z_2}{Z_1 + Z_2}$$

$$Z = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

$$Z = \frac{(8 + j6)(3 - j4)}{(8 + j6) + (3 - j4)}$$

$$Z = \frac{24 - 32j + 18j - j^2 24}{11 + j2}$$

$$Z = \frac{24 - 14j - (-1)24}{11 + j2}$$

(since $j^2 = -1$)

$$Z = \frac{24 - 14j + 24}{11 + j2}$$

$$Z = \frac{48 - 14j}{11 + j2}$$

$$Z = \frac{50 \angle -16.2^\circ}{11.1 \angle 10.3^\circ}$$

$$Z = 4.50 \angle -26.5^\circ \Omega$$

Total current

Both Impedance are in parallel

$$\frac{1}{Z_T} = \frac{1}{Z_1} + \frac{1}{Z_2} \quad \text{L.C.M} \Rightarrow$$

By L.C.M

$$Z = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

$$Z = \frac{(8 + j6) \times (3 - j4)}{(8 + j6) + (3 - j4)}$$

$$Z = \frac{24 - 32j + 18j - j^2 24}{11 + j2}$$

$$Z = \frac{24 - 14j - (-1)24}{11 + j2}$$

(since $j^2 = -1$)

$$Z = \frac{24 - 14j + 24}{11 + j2}$$

$$Z = \frac{48 - 14j}{11 + j2}$$

$$Z = \frac{50 \angle -16.2^\circ}{11.1 \angle 10.3^\circ}$$

$$Z = 4.50 \angle -26.5^\circ \Omega$$

$$Z = \frac{V}{I} = \frac{230 \angle 0^\circ}{4.5 \angle -26.5}$$

$$Z = 51.1 \angle 26.5 \text{ } \Omega$$

(iii)

Power factor

$$P.F = \cos \theta \text{ (or) } R/Z$$

$$P.F = \cos (26.5)$$

$$P.F = 0.89$$

(iv)

power

$$P = VI \cos \theta$$

$$P = 230 \times 4.5 \times 0.89$$

$$P = 10480.17 \text{ Watts}$$

764 - SRIPC

(2)

Two impedances $Z_1 = 14 + j16$ and $Z_2 = 6 - j9$ are connected in parallel across a 210V, 50 Hz supply calculate (a) current in each branch (b) total current of the circuit (c) circuit power factor (d) power taken by the circuit.

Given data

$$Z_1 = 14 + j16 \rightarrow 21.26 \angle 48.8$$

$$Z_2 = 6 - j9 \rightarrow 10.81 \angle -56.30$$

$$\text{Voltage} = 210 \text{ V}$$

$$\text{frequency} = 50 \text{ Hz}$$

To find

Branch current I_1 and $I_2 = ?$

Total current = ?

Power factor = ?

Power = ?

Soln:

i

$$I_1 = \frac{V}{Z_1} = \frac{210 \angle 0^\circ}{21.2 \angle 48.81^\circ}$$

$$I_1 = 9.90 \angle -48.81 \text{ Amps}$$

$$I_2 = \frac{V}{Z_2} = \frac{210 \angle 0^\circ}{10.8 \angle -56.30^\circ}$$

$$I_2 = 19.44 \angle 56.30 \text{ Amps}$$

(ii) Total current

both impedance are parallel

$$\frac{1}{Z_T} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

By L.C.M

$$Z = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

$$Z = \frac{(14 + j16)(6 - j9)}{(14 + j16) + (6 - j9)}$$

$$Z = \frac{84 - 126j + 96j - j^2 144}{20 + 7j}$$

$$Z = \frac{84 - 30j - (-1) 144}{20 + 7j}$$

$$Z = \frac{84 - 30j + 144}{20 + 7j}$$

$$Z = \frac{228 - 30j}{20 + 7j}$$

$$Z = \frac{229.96 \angle -7.49^\circ}{21.18 \angle 19.29^\circ}$$

$$Z = 10.8 \angle -26.78^\circ \Omega$$

$$I = \frac{V}{Z} = \frac{210 \angle 0^\circ}{10.8 \angle -26.78^\circ}$$

$$I = 19.4 \angle 26.78^\circ \text{ Amps}$$

(iii)

Power factor = ?

$$P.F = \cos \theta \text{ (or) } \frac{R}{Z}$$

$$P.F = \cos (26.78)$$

$$P.F = 0.89$$

Power

$$P = VI \cos \theta$$

$$P = 210 \times 19.4 \times 0.89$$

$$P = 3625.86 \text{ watts}$$

REVOLUTION THROUGH TECHNOLOGY

764 - SRIPC

Resonance

R.L.C series resonance


An R.L.C series circuit is said to be in resonance when circuit power factor is unity.

At resonance $X_L = X_C$

X_L = Inductive reactance

X_C = Capacitive reactance

15. 09, 2022
Thursday ☺

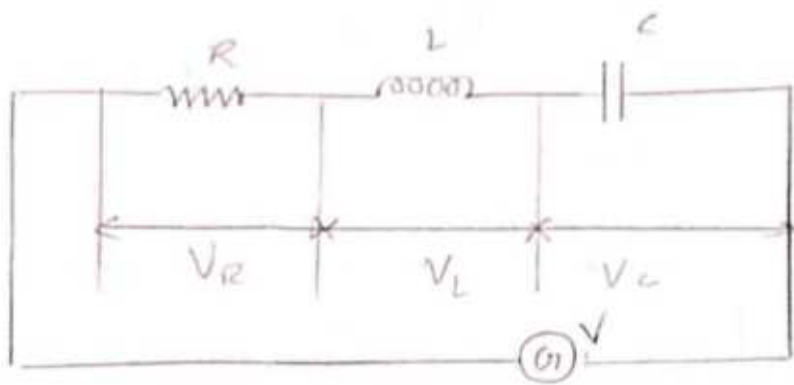

$$\text{Resonance frequency } (F_R) = \frac{1}{2\pi\sqrt{LC}}$$

L - Inductor
C - capacitor

16.09.2022
Friday :-

Effect of Series Resonance

1. When series resonance occurs the inductive reactance X_L and capacitive reactance are equal and opposite and cancel each other.
2. The impedance of the circuit is minimum and equal to the resistance of the circuit.
3. The current in the circuit maximum.
4. The power factor of the circuit is Unity.
5. The voltage drop across L and C is very large.


Quality factors of series resonant circuit

At series resonance the voltage across L and C is many times greater than the applied voltage.

Q - factor = $\frac{\text{Voltage drop across L or C}}{\text{Applied Voltage}}$

$$Q - \text{factor} = \frac{1}{R} \frac{L}{C}$$

Parallel resonance

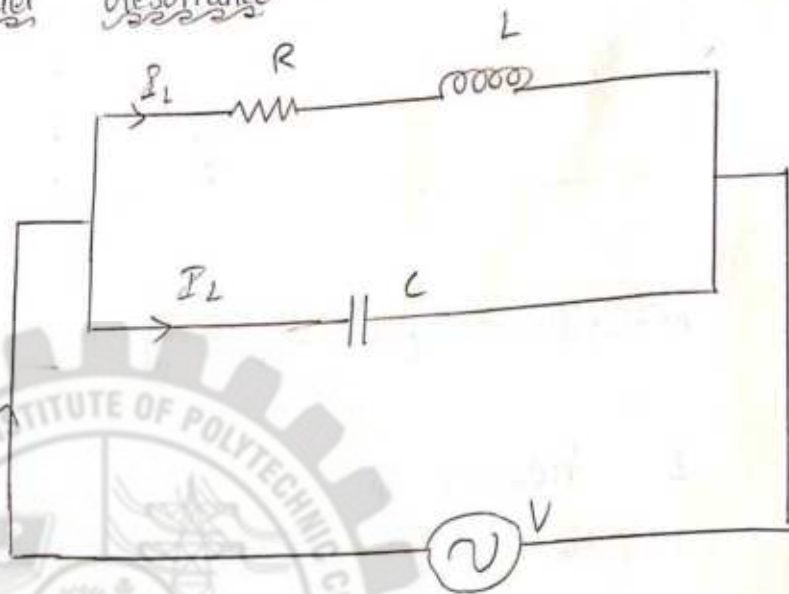

At resonance $I_C = I_L$

$$\text{Resonant frequency } F_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \left[\frac{R}{L}\right]^2}$$

Dynamic resistance at series

When the series resonance occur the inductive reactance X_L and capacitive reactance are equal and opposite and cancel each other.

$$\text{Dynamic resistance} = "R"$$

Dynamic resistance at parallel

$\frac{L}{CR}$ is known as the impedance at parallel resonance or dynamic impedance or dynamic resistance

$$\text{Dynamic resistance} = \frac{L}{CR}$$

Q - factor for parallel circuit

At parallel resonance the circulating current between the two branches is many times greater than the supply current.

Q - factor = $\frac{\text{circulating current between L and C}}{\text{Supply current}}$

$$Q - \text{factor} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

Comparison of series and parallel resonance

S.No	Particulars	Series circuit	Parallel circuit
1.	Impedance at resonance	Minimum	Maximum
2.	Current at resonance	Maximum	Minimum
3.	Dynamic resistance	R	$\frac{R L}{C R}$
4.	Power factor at resonance	Unity	Unity
5.	frequency at resonance	$f_r = \frac{1}{2\pi \sqrt{LC}}$	$f_r = \frac{1}{2\pi \sqrt{LC - \left[\frac{R^2}{L}\right]}}$
6.	It magnifies	Voltage	Current
7.	Q - factor	$\frac{1}{R} \sqrt{\frac{L}{C}}$	$\frac{1}{R} \sqrt{\frac{L}{C}}$

Application of Resonance


1. Resonance circuit can be employed to maintain AC circuit oscillations at a constant frequency.
2. It is used in tuning circuit.
3. It is used in filter circuits to block a particular frequency or a range of frequencies.
4. It is used in radio transmitter and receivers.
5. It is used in TV transmitter and receiver.

19.09.2022
Monday

UNIT - 4

THREE PHASE CIRCUITS


Star connection

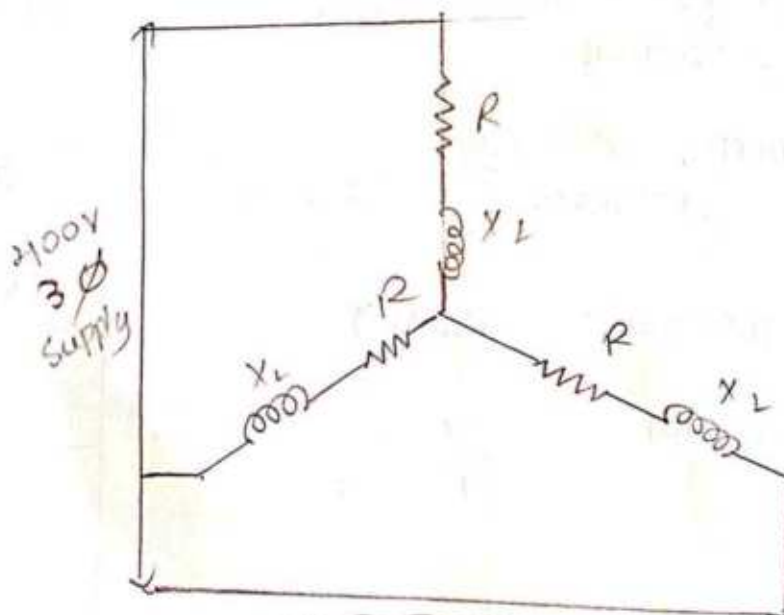

$$I_L = I_{ph}$$

$$V_L = \sqrt{3} V_{ph}$$

Delta connection

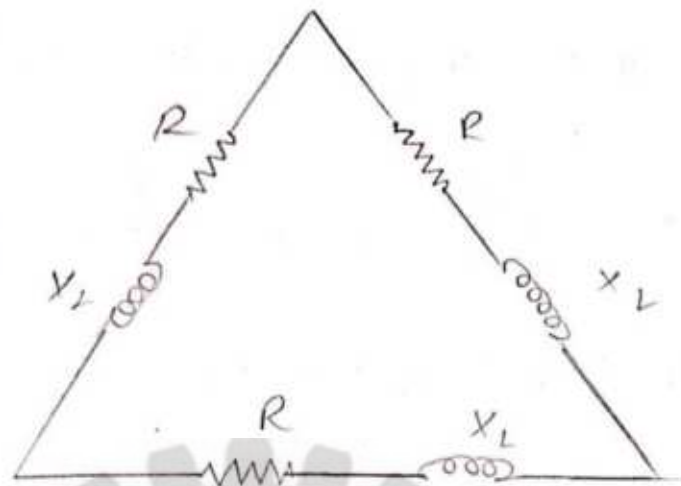

$$P_L = \sqrt{3} I_{ph}$$

$$V_L = V_{ph}$$

Three identical coils with resistance of 15Ω and Reactance of 15Ω are connected in Delta across $400V, 50Hz$ supply. find

- i) line current
- ii) power factor
- iii) power draw from the supply

Given data:

$$\text{Resistance } R = 15\Omega$$

$$\text{Inductive Reactance } X_L = 15\Omega$$

$$\text{line voltage } V_L = 400V = V_{ph}$$

To find:

- i) line current (I_L) = ?
- ii) power factor = ?
- iii) power draw from the supply = ?

Soln.

line current (I_L)

$$I_L = \sqrt{3} I_{ph} \text{ [Delta connection]} \rightarrow (1)$$

$$\therefore I_{ph} = \frac{V_{ph}}{Z_{ph}} \text{ [since } V = IZ \text{]}$$

$$\text{and } Z_{ph} = \sqrt{R^2 + X_L^2}$$

To find Z_{ph}

$$Z_{ph} = \sqrt{(15)^2 + (8)^2}$$

$$Z_{ph} = \sqrt{21.21 \Omega}$$

$$Z_{ph} = 21.21 \Omega$$

$$\therefore I_{ph} = \frac{V_{ph}}{Z_{ph}} \text{ [since } V = IZ \text{]}$$

$$\text{and } Z_{ph} = \sqrt{R^2 + X}$$

To find I_{ph}

$$I_{ph} = \frac{V_{ph}}{Z_{ph}}$$

$$I_{ph} = \frac{400}{21.21}$$

Delta connection

$$V_{ph} = V_L$$

$$I_{ph} = 18.85 \text{ A}$$

Sub I_{ph} value in equ (1)

$$I_L = \sqrt{3} I_{ph} \longrightarrow (1)$$

$$I_L = \sqrt{3 \times 18.85}$$

$$I_L = 32.64 \text{ A}$$

ii) power factor

$$P.F = \cos \theta \text{ (or) } R/Z$$

$$P.F = R/Z = \frac{15}{21.21} = 0.70$$

$$P.F = 0.70$$

iii) power drawn from the supply

$$P = \sqrt{3} \cdot V_L \cdot I_L \cdot \cos \theta$$

$$P = \sqrt{3} \times 400 \times 32.64 \times 0.70$$

$$\text{Power} = 15829.55 \text{ Watts}$$

② Three identical coil with resistance of 20Ω and reactance of 25Ω are connected in delta across 420 V , 50 Hz supply. find i) line current ii) power factor iii) power drawn from the supply.

Given data:

$$\text{Resistance} = 20 \Omega$$

$$\text{Inductive reactance } (X_L) = 25 \Omega$$

$$\text{Line voltage } (V_L) = 420 \text{ V} = V_{ph}$$

To find

- i) line current (I_L) = ?
- ii) power factor = ?
- iii) power drawn from the supply = ?

Soln

line current (I_L) = ?

$$I_L = \sqrt{3} I_{ph} \text{ (delta connection)} \rightarrow (1)$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} \quad (V = IZ)$$

$$\text{and } Z_{ph} = \sqrt{R^2 + X_L^2}$$

To find Z_{ph}

$$Z_{ph} = \sqrt{(20)^2 + (25)^2}$$

$$Z_{ph} = 32.01 \Omega$$

To find I_{ph}

$$I_{ph} = \frac{V_{ph}}{Z_{ph}}$$

$$I_{ph} = \frac{420}{32.01} \quad [V_{ph} = V_L]$$

$$I_{ph} = 13.12 \text{ A}$$

sub I_{ph} Value in equ (1)

$$I_L = \sqrt{3} I_{ph} \rightarrow (1)$$

$$I_L = \sqrt{3} \times 13.12$$

$$I_L = 22.72 \text{ A}$$

39.36

6.27

22.7

ii) power factor

$$P.F = \cos \theta \text{ or } R/Z$$

$$P.F = R/Z = \frac{20}{39.01}$$

$$P.F = 0.62$$

iii) power drawn from the supply

$$P = \sqrt{3} V_L I_L \cos \theta$$

$$P = \sqrt{3} \times 420 \times 22.72 \times 0.62$$

$$P = 10247.31 \text{ watts}$$

Three identical coils with resistance $20\ \Omega$ and reactance of $15\ \Omega$ are connected in star across 400V , 50Hz supply. Find i) line current ii) power factor iii) power drawn from the supply.

Given data:

$$\text{Resistance } R = 20\ \Omega$$

$$\text{Inductive reactance } X_L = 15\ \Omega$$

$$\text{Line voltage } V_L = 400\text{V}$$

To find

i) line current (I_L) = ?

ii) power factor $\cos \phi$ = ?

iii) power drawn from the supply = ?

Solve

i) line current (I_L)

$$I_L = I_{ph} \quad [\text{star connection}] \rightarrow \textcircled{1}$$

$$\therefore I_{ph} = \frac{V_{ph}}{Z_{ph}} \rightarrow \textcircled{A}$$

To find $V_{ph} = \frac{V_L}{\sqrt{3}} \rightarrow \textcircled{B}$ [since $V_L = \sqrt{3} V_{ph}$]

$$Z_{ph} = \sqrt{R^2 + X_L^2} \rightarrow \textcircled{C}$$

To find Z_{ph}

$$\text{Impedance } Z_{ph} = \sqrt{R^2 + X_L^2}$$

$$Z_{ph} = \sqrt{20^2 + 15^2}$$

$$Z_{ph} = 25 \Omega$$

To find V_{ph}

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}}$$

$$V_{ph} = 230.94 \text{ V}$$

To find I_{ph}

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{230.94}{25}$$

$$I_{ph} = 9.24 \text{ A}$$

Sub I_{ph} value in equ (1)

$$I_L = I_{ph} = 9.24 \text{ A} \quad [\text{star connection}]$$

ii) Power factor

$$P.F = \cos \theta = \frac{R}{Z}$$

$$\frac{R}{Z} = \frac{20}{25}$$

$$P.F = 0.8$$

iii) Power drawn from the supply

$$P = \sqrt{3} V_L I_L \cos \theta$$

$$P = \sqrt{3} \times 400 \times 9.24 \times 0.8$$

$$P = 5121.32 \text{ Watts}$$

Three identical coils with resistance of $32\ \Omega$ and reactance of $29\ \Omega$ are connected in star across 415V, 50Hz supply. find i) line current ii) power factor
iii) power drawn from the supply.

Given data

$$\text{Resistance } (R) = 32\ \Omega$$

$$\text{Inductive reactance } (X_L) = 29\ \Omega$$

$$\text{line Voltage } (V_L) = 415\ \text{V}$$

To find

i) line current $(I_L) = ?$

ii) power factor = ?

iii) power drawn from the supply = ?

Soln.

i) To find line current $(I_L) = ?$

$$I_L = I_{ph} \text{ (star connection)} \rightarrow \textcircled{1}$$

$$\therefore I_{ph} = \frac{V_{ph}}{Z_{ph}} \rightarrow \textcircled{A}$$

To find V_{ph}

$$V_{ph} = \frac{V_L}{\sqrt{3}} \rightarrow \textcircled{B} \quad (V_L = \sqrt{3}V_{ph})$$

$$Z_{ph} = \sqrt{R^2 + X_L^2} \rightarrow \textcircled{C}$$

To find Z_{ph}

$$\text{impedance } Z_{ph} = \sqrt{R^2 + X_L^2}$$

$$Z_{ph} = \sqrt{(32)^2 + (29)^2}$$

$$Z_{ph} = 43.18 \Omega$$

To find V_{ph}

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{415}{\sqrt{3}}$$

$$V_{ph} = 239.60 \text{ V}$$

To find I_{ph}

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{239.60}{43.18}$$

$$I_{ph} = 5.54 \text{ A}$$

Sub value in eqn ①

$$I_L = I_{ph} = 5.54 \text{ A}$$

ii) power factor

$$P.F = \cos \theta \text{ or } R/Z$$

$$P.F = \frac{R}{Z} = \frac{32}{43.18}$$

$$P.F = 0.74$$

Power drawn from the supply

$$P = \sqrt{3} V_L I_L \cos \theta$$

$$P = \sqrt{3} \times 415 \times 5.54 \times 0.74$$

$$P = 2946.79 \text{ Watts}$$

21.09.2022

Wednesday

- ① A 415V, 3 phase voltage is applied to a balanced delta connected load of phase impedance $(27 + j43) \Omega$. Find the line current, power factor and power consumed by circuit.

Given data:

(R) Resistance = 27Ω

(X_L) Inductive reactance = 43Ω

(V_L) Voltage = $415 \text{ V} = V_{ph}$

To find

- i) line current = ?
- ii) power factor = ?
- iii) power consumed by circuit = ?

Solution

line current (I_L) = ?

$$I_L = \sqrt{3} I_{ph} \text{ (delta connection)} \rightarrow \textcircled{1}$$

$$\therefore I_{ph} = \frac{V_{ph}}{Z_{ph}} \quad (V = 82)$$

10 find $Z_{ph} =$

$$Z_{ph} = \sqrt{R^2 + X_L^2}$$

$$Z_{ph} = \sqrt{(27)^2 + (113)^2}$$

$$Z_{ph} = 50.77 \Omega$$

TO

find I_{ph}

$$I_{ph} = \frac{V_{ph}}{Z_{ph}}$$

$$I_{ph} = \frac{415}{50.77}$$

$$(V_{ph} = V_L)$$

$$I_{ph} = 8.17 \text{ A}$$

Sub I_{ph} value in equ (1)

$$I_L = \sqrt{3} I_{ph} \rightarrow C$$

$$I_L = \sqrt{3} \times 8.17$$

$$I_L = 14.15 \text{ A}$$

ii) power factor

$$P.F = \cos \theta \text{ or } \frac{R}{Z}$$

$$P.F = R/Z$$

$$\frac{27}{50.71}$$

$$P.F = 0.53$$

iii) power consumed by the circuit

$$P = \sqrt{3} V_L I_L \cos \theta$$


764 - SRIPC

$$P = \sqrt{3} \times 415 \times 14.15 \times 0.53$$

$$P = 5390.64 \text{ watts}$$

Diff. questions model sem with same answer

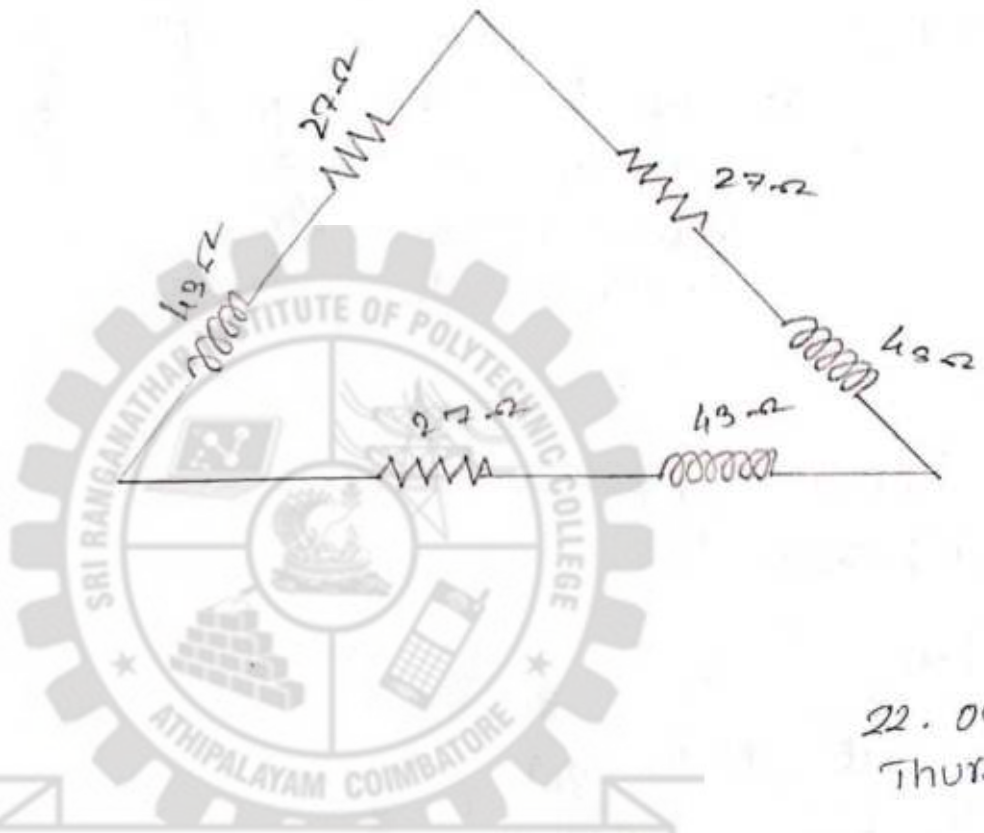A 415V, 3 phase voltage is connected in a balanced delta connection as shown in the fig. find the line current, power factor and power drawn from the circuit.



22.09.2022
Thursday

A 410V, 3 phase voltage is applied to a balanced star connected load of phase impedance $(24 + j42)$. find the current, power factor and power consumed by the circuit.

A 410V, 3 phase voltage is connected in a star connection as shown in the diagram. find the current, power factor and power drawn from the supply.

1) The power input of 400V, 3 ϕ 50 Hz motor is measured by two wattmeter, which indicates 2500W and 500W respectively. find the power and power factor of the circuit.

Given data:

$$\text{Voltage (V)} = 400\text{V}$$

$$\text{frequency (f)} = 50\text{ Hz}$$

$$\text{Wattmeter (W}_1\text{)} = 2500\text{W}$$

$$\text{Wattmeter (W}_2\text{)} = 500\text{W}$$

To find

i) power (P) = ?

ii) power factor = ?

i) power (P)

$$\text{Total power} = W_1 + W_2$$

$$\text{Power} = 2500 + 500$$

$$\text{Power} = 3000\text{W}$$

764 - SRIPC

iii) power factor:

$$\text{Power factor} = \cos \theta \text{ or } P/Z$$

To find $\cos \theta$

$$\tan \theta = \sqrt{3} \left[\frac{W_2 - W_1}{W_1 + W_2} \right]$$

$$\tan \theta = \sqrt{3} \left[\frac{500 - 2500}{2500 + 500} \right]$$

$$\tan \theta = \sqrt{3} [-0.66]$$

$$\tan \theta = -1.14$$

$$\theta = \tan^{-1}[-1.14]$$

$$\theta = -48.74$$

Sub θ value in power factor formula

$$\text{power factor} = \cos \theta$$

$$P.F. = \cos(-48.74)$$

$$\text{power factor} = 0.65$$

power input of a 4125 V, 3 ϕ 50 Hz motor is measured by two wattmeter, which indicates 3199 W and 619 W respectively. find the power and power factor of the circuit.

Given data

$$\text{Voltage (V)} = 4125 \text{ V}$$

$$\text{frequency (F)} = 50 \text{ Hz}$$

$$\text{wattmeter (W}_1\text{)} = 3199 \text{ W}$$

$$\text{wattmeter (W}_2\text{)} = 619 \text{ W}$$

to find

$$\text{power} = ?$$

$$\text{Power factor of the circuit} = ?$$

Soln/..

i) power

$$\text{Total power} = w_1 + w_2 \\ = 3499 + 649$$

$$\text{power} = 4148 \text{ W}$$

ii) power factor = ?

power factor $\leq \cos \theta$ or P/Z

To find $\cos \theta$

$$\tan \theta = \sqrt{3} \left[\frac{w_2 - w_1}{w_1 + w_2} \right]$$

$$\tan \theta = \sqrt{3} \left[\frac{649 - 3499}{3499 + 649} \right]$$

$$\tan \theta = \sqrt{3} \left[\frac{-2850}{4148} \right]$$

$$\tan \theta = \sqrt{3} (-0.68)$$

$$\tan \theta = -1.17$$

$$\theta = \tan^{-1} (-1.17)$$

$$\theta = -49.47$$

Sub θ value in power factor formula

$$P.F = \cos \theta$$

$$P.F = \cos (-119.47)$$

$$P.F = 0.64$$

26.09.2022

Monday 😊❤️

UNIT - V

STORAGE BATTERY

Battery

Battery is an electrochemical device which delivers electric energy by chemical reaction.

Classification of cells

1. Primary cell


A cell which cannot be recharged is known as primary cell. ex: dry cell, voltaic cell.

2. Secondary cell

The cell which can be recharged and brought to the original state is known as secondary cell. ex: lead acid cell, alkaline cells.


$$R_1 = \frac{R_{31} R_{12}}{R_{12} + R_{23} + R_{31}}$$

LEAD ACID BATTERY

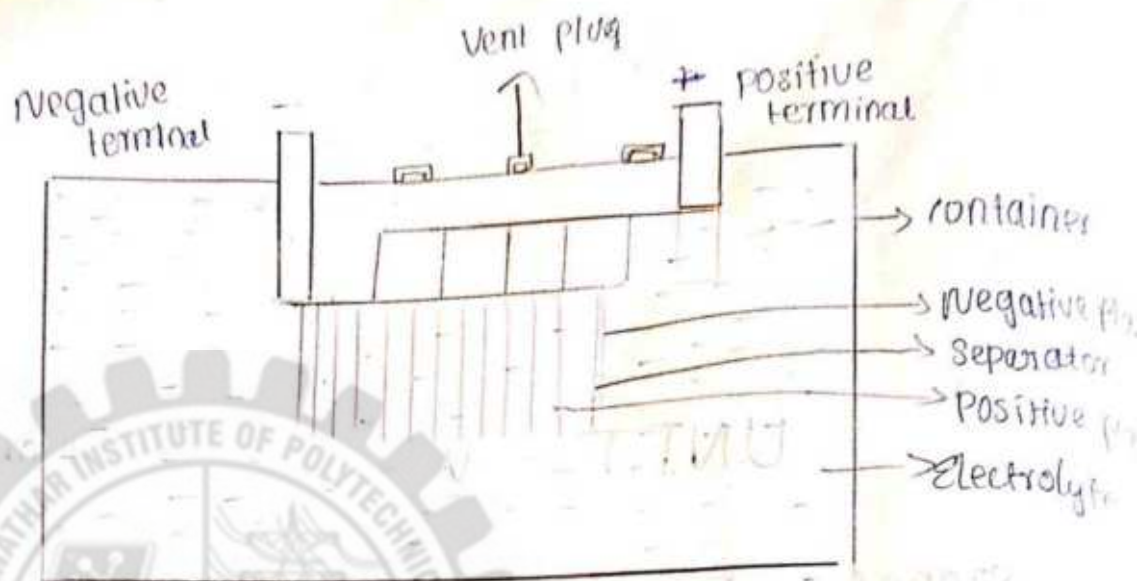


1. container
2. Positive plate - Anode - lead peroxide (PbO_2)
3. Negative plate - cathode - spongy lead (Pb)
4. Separator.
5. Electrolyte - Sulphuric acid (H_2SO_4)
6. cell covers - Vent plug
7. cell connector
8. Battery terminal

Chemical reaction during discharging

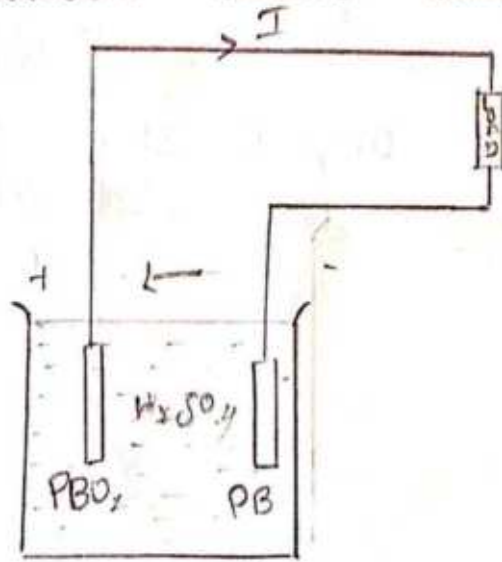

Chemical reaction during charging

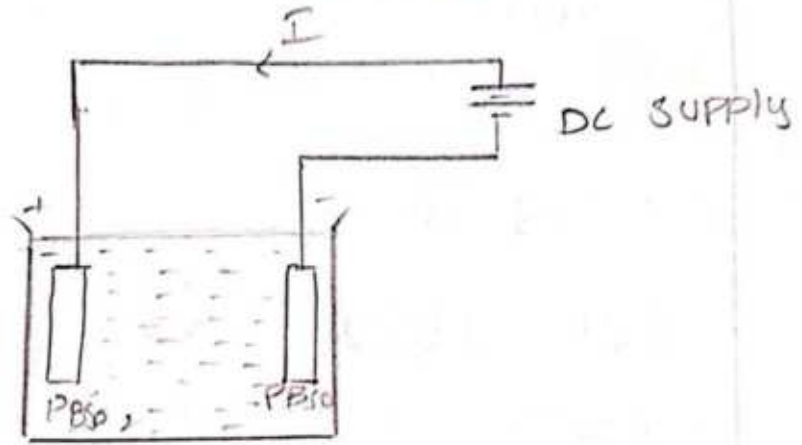

Alkaline cells


1. Nickel - Iron cell
2. Nickel - cadmium cell

Nickel - Iron cell

Positive plate - Nickel hydroxide $[Ni(OH)_2]$

Negative plate - Iron $[Fe]$


Electrolyte - potassium hydroxide (KOH)

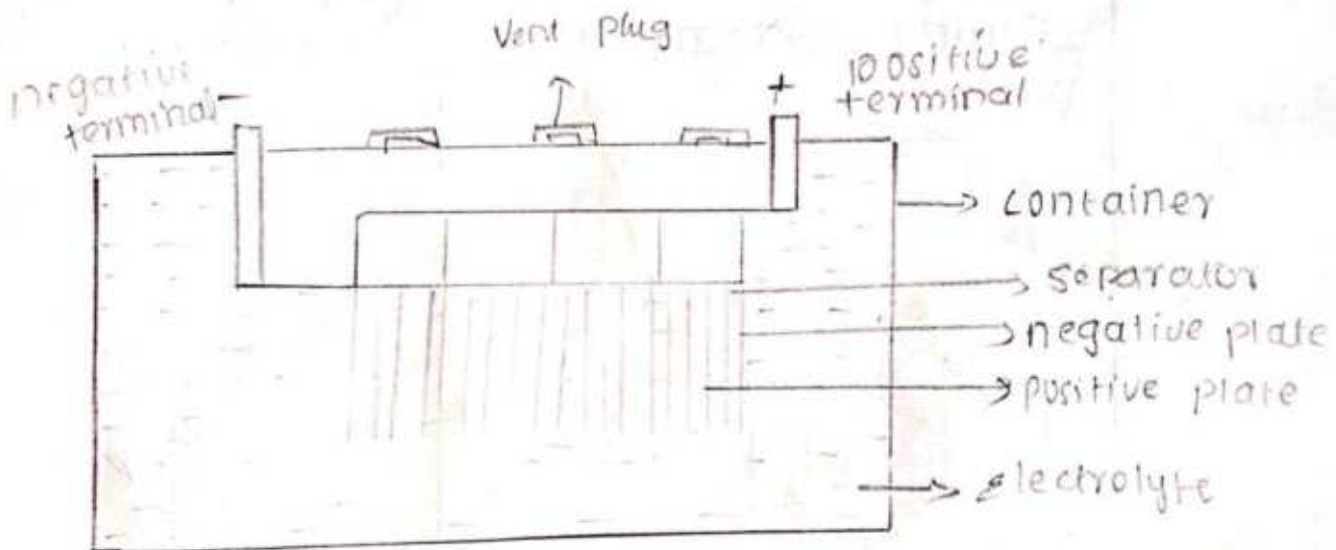

4. Separator
5. container
6. cell covers - Vent plug
7. cell connectors
8. Battery terminals

Nickel cadmium cell

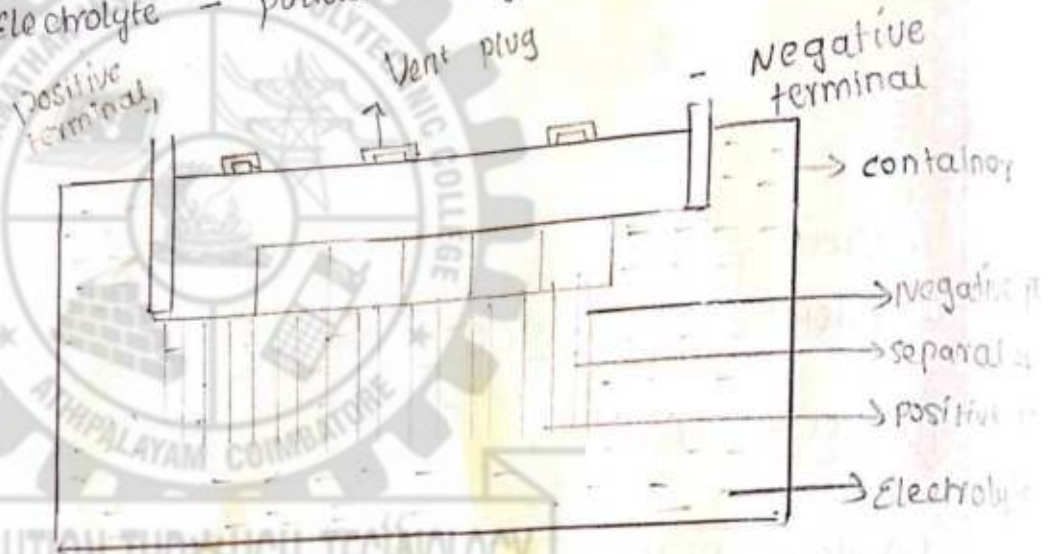1. positive plate - Nickel hydroxide $[Ni(OH)_2]$
2. Negative plate - cadmium (C_2)
3. Electrolyte - potassium hydroxide (KOH)





764 - Nickel Iron cell

28. 09. 22

Wednesday:

During discharging

During charging

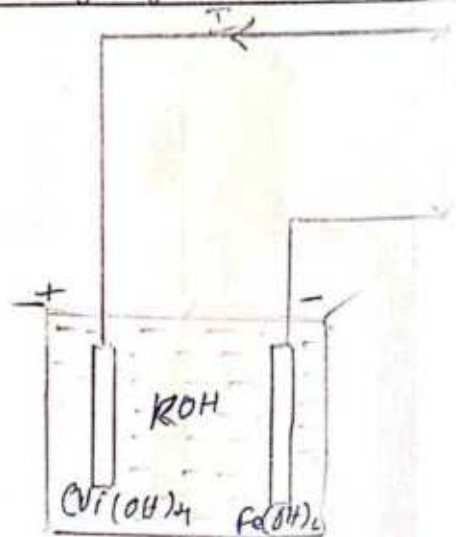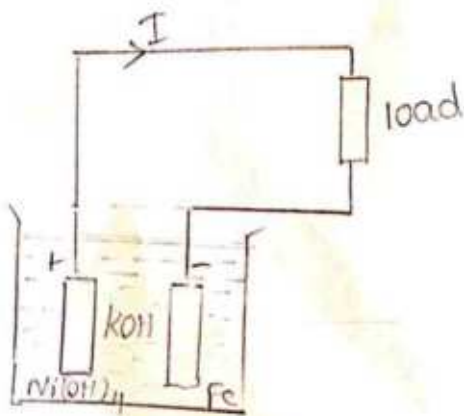


$Ni(OH)_2$ - Nickel hydroxide
 Fe - Iron

KOH - potassium hydroxide


Nickel cadmium cell

during discharging

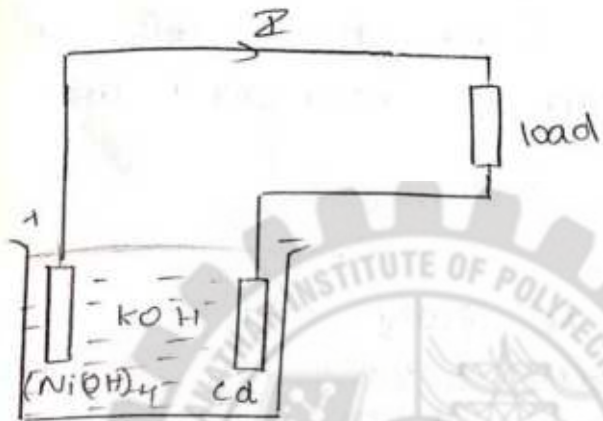

Ni(OH)_2 - Nickel hydroxide
 Cd - Cadmium
 KOH - potassium hydroxide

during charge

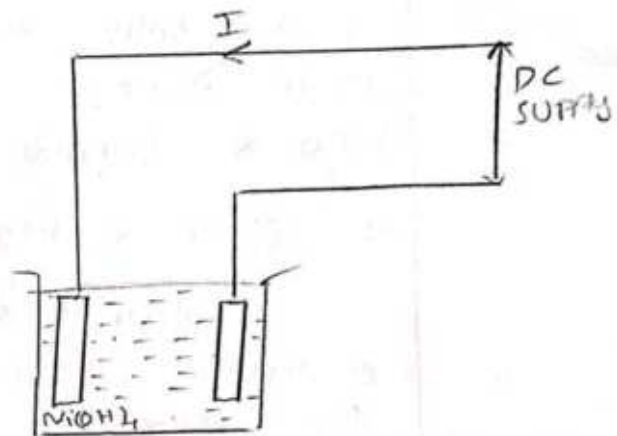

Indication of fully charged cell

1. Voltage
2. Gassing
3. Specific gravity of the electrolyte
4. Colour of the plates

1. Voltage

• During charging the terminal voltage of a cell increases. The voltage per cell is 2.1 volts. This can be checked with the help of cell tester.

2. Gassing

When the cell is fully charged it freely gives off hydrogen at cathode and oxygen at anode.

3. Specific gravity of the electrolyte:

The specific gravity of the electrolyte of a fully charged lead acid cell is about 1.28. This can be measured with the help of hydrometer.

4. Colour of plate

When the cell is fully charged the colour of positive plate becomes dark brown and the negative plate is grey.

Defects and their remedies in lead acid battery.

1. Sulphation
2. buckling
3. Internal short circuit
4. Sedimentation

1. Sulphation

If the discharged battery is not charged immediately or over discharged the sulphate deposit on the plates will become crystal.

To prevent this carbonate of soda and charging the battery at low rate for a long time.

2. buckling

buckling - means bending of battery plates to rectify this replace the buckling

plates.

Internal Short circuit:

The short circuit may occur with damage of separator. To rectify this replace the separators.

4. Sedimentation

due to charging and discharging small amount of active materials deposit in the container. or electrolyte. To rectify this replace the electrolyte and clean the bottom surface.

29.09.2022

Thursday :-

Battery capacity

The capacity of battery is expressed in "Ampere - hours".

It depend upon

1. Size number of plates
2. Quantity of electrolyte
3. Specific gravity of electrolyte
4. Rate of discharging.
5. Temperature.

Efficiency:

1) Ampere - hour efficiency


$$\text{A.H. efficiency} = \frac{\text{Ampere hour output}}{\text{Ampere hour Input}} \times 100$$

2) Watts hour efficiency


$$\text{Wh efficiency} = \frac{\text{Watts hour output}}{\text{Watts hour input}} \times 100$$

Methods of charging


① constant current method :

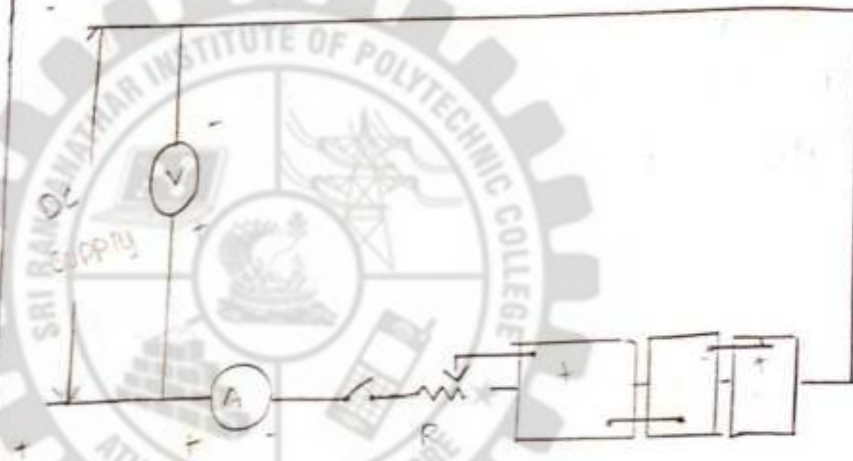

② constant voltage method

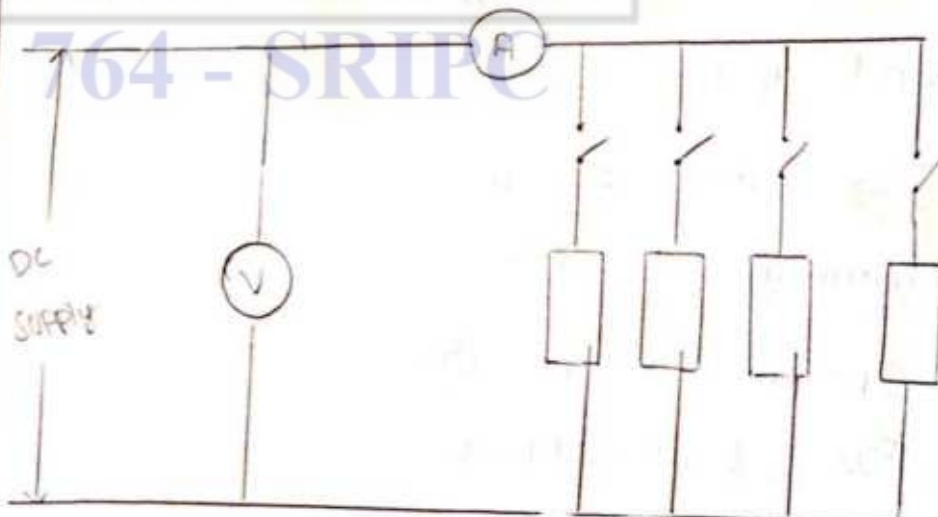

Lithium Ion cell

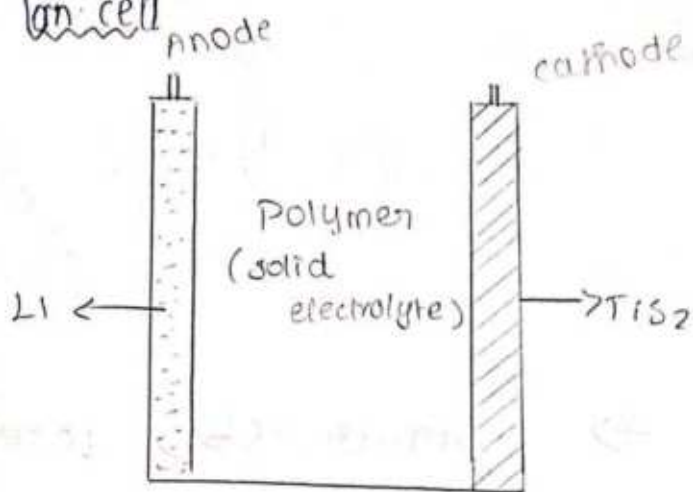

Types

1. Lithium cobalt oxide battery
2. Lithium iron phosphate battery.
3. Lithium manganese oxide battery.
4. Lithium nickel cobalt aluminium oxide battery.
5. Lithium Nickel manganese cobalt oxide battery
6. Lithium titanate oxide battery.

Anode - Lithium - Li

Cathode - Titanate sulphide [TiS₂]

Electrolyte - polymer

Separator

MERCURY CELL

30.09.2022

